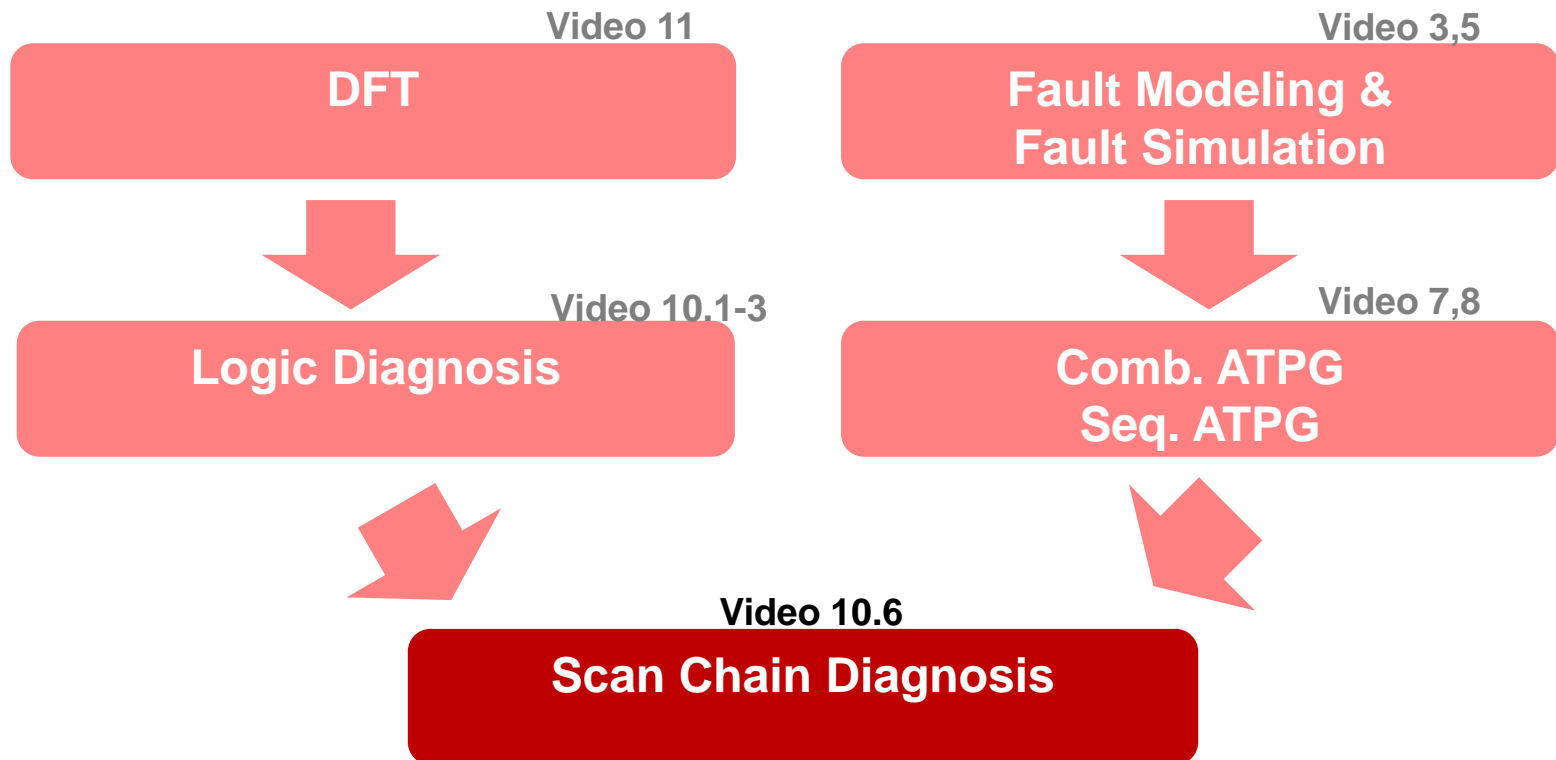


# Diagnosis

- Introduction
- Logic Diagnosis
- Scan Chain Diagnosis
  - ◆ Fault models
  - ◆ Sequential ATPG diagnosis [Kundu 93]
  - ◆ Simulation-based diagnosis
    - \* X simulation [Guo 01]
    - \* Single excitation pattern [Li 05]
- Failure Analysis
- Conclusions




# Course Roadmap for This Video


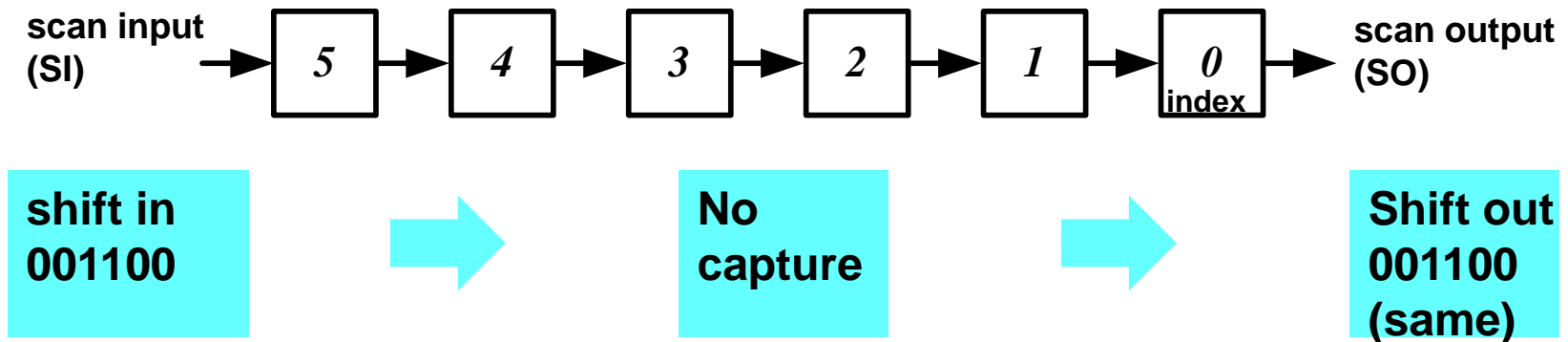
# Testing Scan Chains


- Scan chains occupies **5%~10%** silicon area
  - ♦ **~30%** scan chain failure reported [Guo 01]
- Testing (and diagnosis) of scan chains is important
- **Scan chain integrity test** (aka **flush test**) applied before testing CUT
  - ♦ Shift in **00110011...** alternating test patterns
  - ♦ **NO capture.** Directly shift out. Expect same outputs
  - ♦ All four transitions are covered  $1 \rightarrow 1$ ;  $1 \rightarrow 0$ ;  $0 \rightarrow 1$ ;  $0 \rightarrow 0$



**Flush Test Needed for Scan Chains**
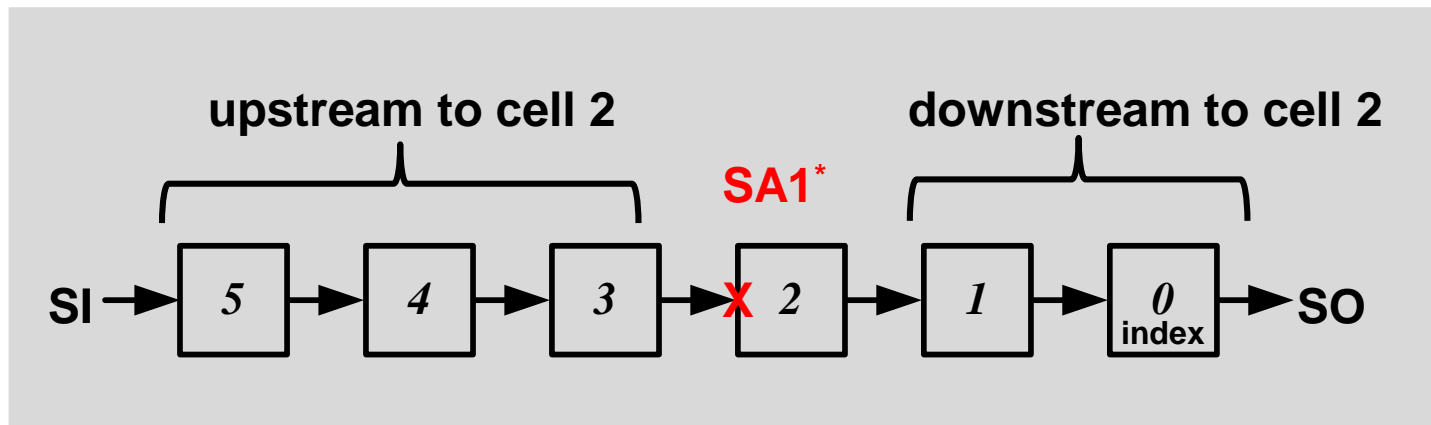
# Scan Chain Fault Effects

- Scan cells are indexed from **SO** to **SI**, in increasing order
- Assume cell 2 is stuck-at one
  - ♦ cells 1,2 are **downstream** to cell 2
  - ♦ cells 3,4,5 are **upstream** to cell 2



before shift in  
001100

after shift in  
001111

after shift out  
111111

all **downstream** 0's  
are flipped to one

all **upstream** 0's  
are flipped to one

\*NOTE: this fault located at  
scan input, not data input, of cell 2

# Scan Chain Fault Models

- Stuck-at one (**SA1**)
- Stuck-at zero (**SA0**)
- Slow-to-Rise (**STR**)
  - ♦ one cycle later
- Slow-to-Fall (**STF**)
  - ♦ one cycle later
- Setup Time (**ST**)
  - ♦ STR+STF
- Fast-to-rise (**FTR**)
  - ♦ one cycle earlier
- Fast-to-Fall (**FTF**)
  - ♦ on cycle earlier
- Hold-time (**HT**)
  - ♦ FTR+FTF

	flush test outputs*
Expected SO	11001100
Faulty SO ( <b>SA1</b> )	11 <u>11</u> 11 <u>11</u>
Faulty SO ( <b>SA0</b> )	<u>00</u> 00 <u>00</u> 00
Faulty SO ( <b>STR</b> )	1 <u>0</u> 001 <u>0</u> 00
Faulty SO ( <b>STF</b> )	110 <u>1</u> 1100
Faulty SO ( <b>ST</b> )	1 <u>00</u> 1 <u>100</u>
Faulty SO ( <b>FTR</b> )	11 <u>1</u> 011 <u>1</u> 0
Faulty SO ( <b>FTF</b> )	1100 <u>0</u> 100
Faulty SO ( <b>HT</b> )	11 <u>1</u> 0 <u>0</u> 1 <u>1</u> 0

\* assume single *permanent fault*,  
which always happens consistently

# Quiz

Q: We apply flush test to a scan chain. Please identify which fault is this?

(Hint: *Intermittent fault* means a fault not always happen)

ANS:

	flush test outputs
Expected SO	11001100
Observed SO	1100 <u>0</u> 1 <u>1</u> 0


# Diagnosis

- Introduction
- Logic Diagnosis
- Scan Chain Diagnosis
  - ◆ Fault models
  - ◆ Sequential ATPG diagnosis [Kundu 93]
  - ◆ Simulation-based diagnosis
    - \* X-simulation [Guo 01]
    - \* Single excitation pattern [Li 05]
- Failure Analysis
- Conclusions


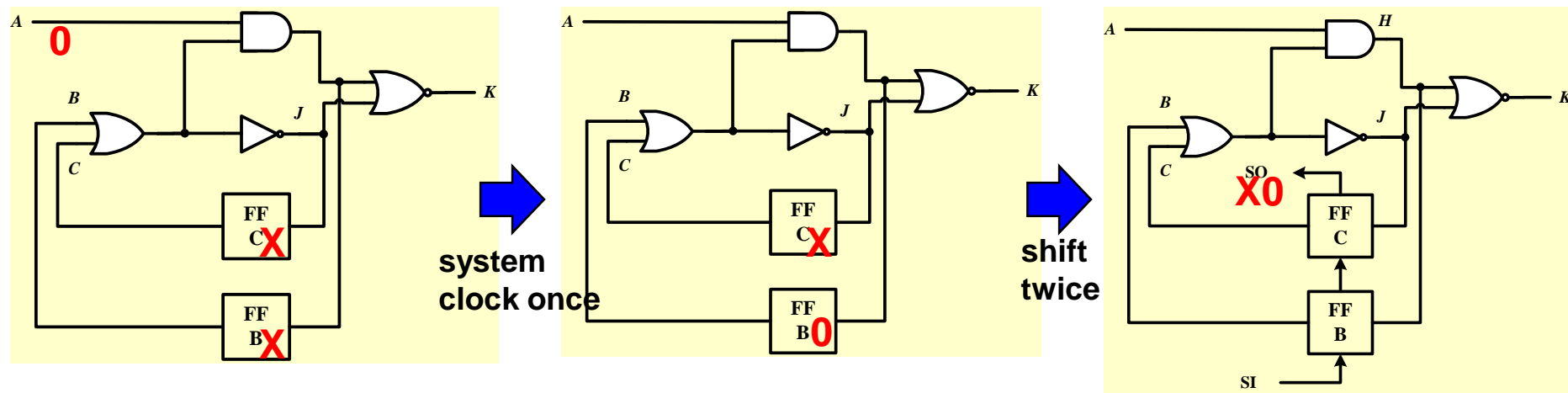
# Sequential ATPG [Kundu 93]

- Idea: use PI, not scan, to control FF
  - ① control FF to desired value by sequential ATPG
  - ② shift out scan chain and check its value
- Example:  $FF_B$  SA1
  - ♦  $A=0$ , system clock once. Shift out 2 cycles
  - ♦ If  $FF_B=0$ , there is **NO SA1** downstream to  $FF_B$ ;
  - ♦ If  $FF_B=1$ , there is **SA1** downstream to  $FF_B$ .




**Repeat this to Every Cell in Chain to Locate Fault**


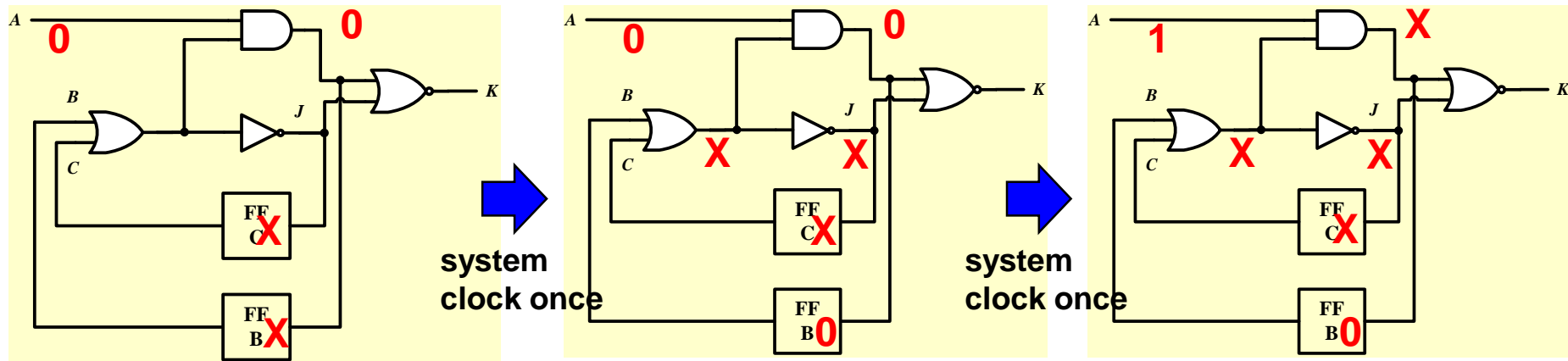
# Sequential ATPG (2)

- Another example: FF<sub>B</sub> SA0
  - ♦ Fail to generate patterns
  - ♦ Unable to diagnose SA0 downstream to FF<sub>B</sub>




**Sequential ATPG is Ineffective**

# Quiz

**Q: John has a smart idea. Since we know there is no SA1 in scan chain, we can first shift in two zeros into the chain.**

**Given the initial state 00 ,use sequential ATPG to diagnose if there is SA0 downstream to  $FF_B$ ? (that is, control  $FF_B = \text{one}$ )**

**ANS:**

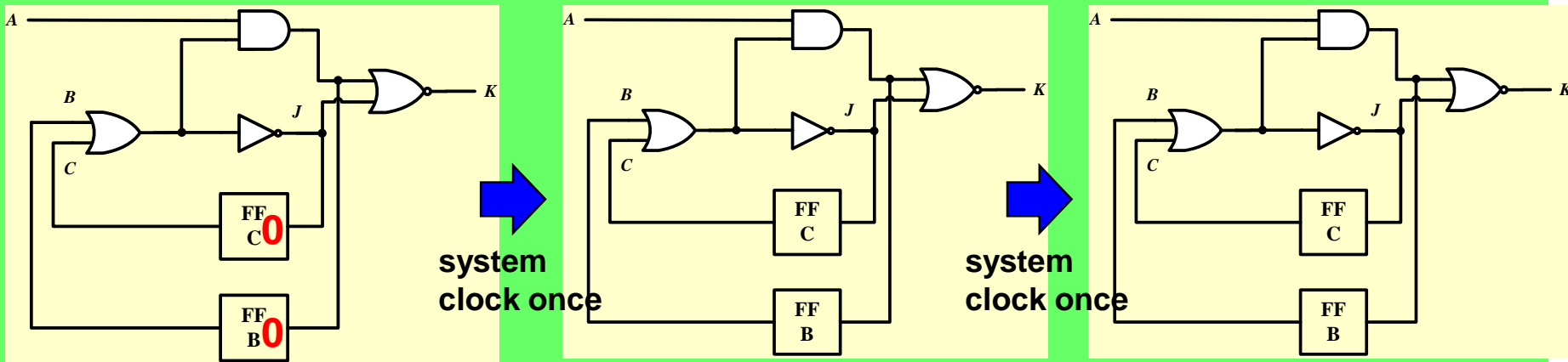

# Diagnosis


- Introduction
- Logic Diagnosis
- Scan Chain Diagnosis
  - ◆ Fault models
  - ◆ Sequential ATPG diagnosis [Kundu 93]
  - ◆ Simulation-based diagnosis
    - \* X simulation [Guo 01]
    - \* Single Excitation pattern [Li 05]
- Failure Analysis
- Conclusions



# UB/LB by Simulation [Guo 01]

- Faulty SC and fault model is already known by flush test
- Simulate circuit with faulty SC values changed to X
  - ♦ to obtain **simulated values**
- Test CUT to obtain **observed values**
- **Lower bound** = max-index where obs. = sim. values  $\neq$  stuck values
  - ♦ NOTE: X NOT considered
- **Upper bound** = mini-index where obs.  $\neq$  sim. values


SA1

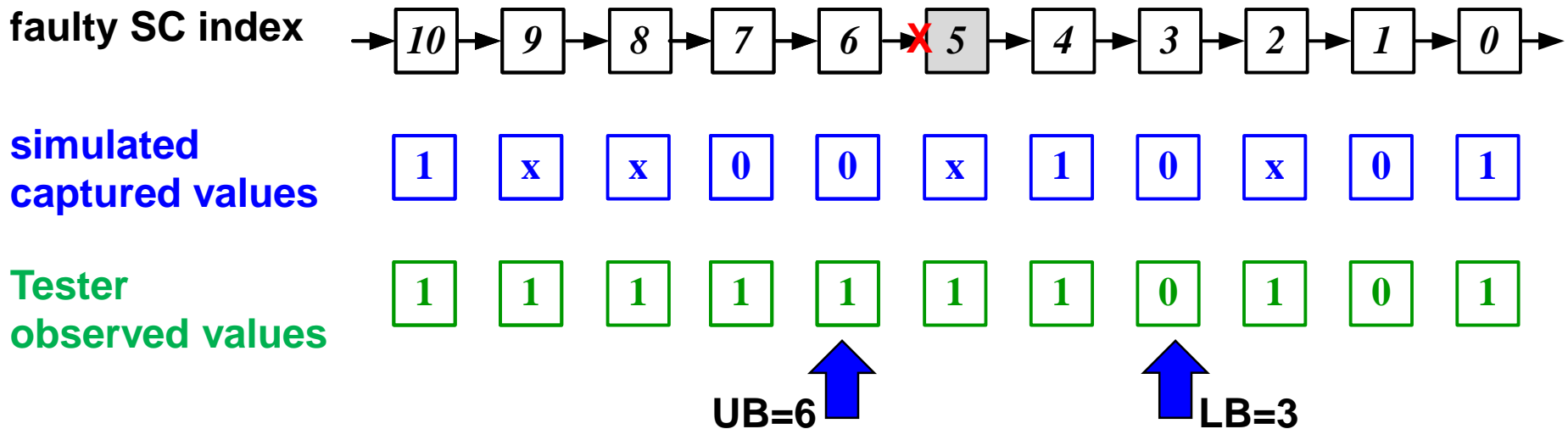

# Quiz

**Q: Given a SA0 fault. Given the following simulated output and observed output, what are the UB and LB?**

**ANS:**

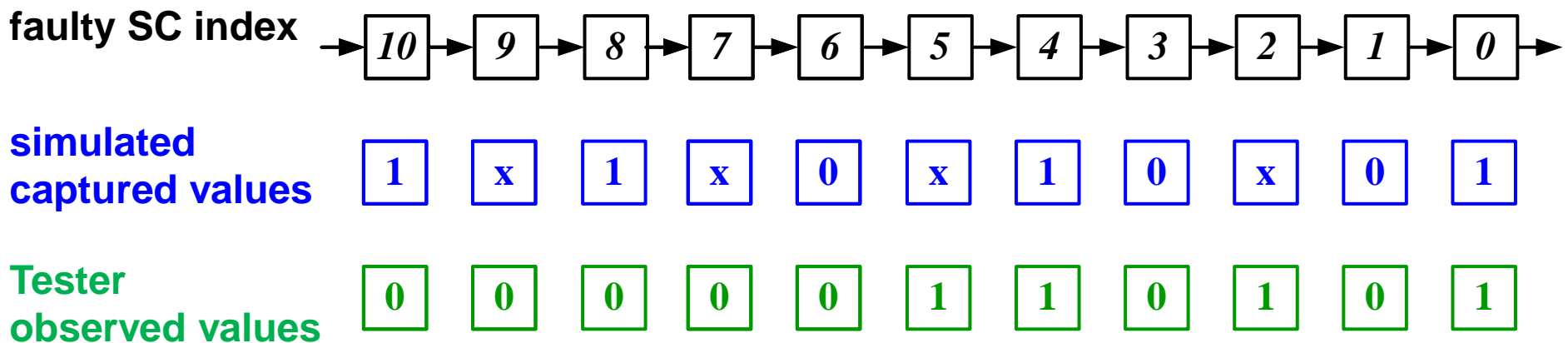


# Diagnosis

- Introduction
- Logic Diagnosis
- Scan Chain Diagnosis
  - ◆ Fault models
  - ◆ Sequential ATPG diagnosis [Kundu 93]
  - ◆ Simulation-based diagnosis
    - \* X simulation [Guo 01]
    - \* Single Excitation pattern [Li 05]
- Failure Analysis
- Conclusions





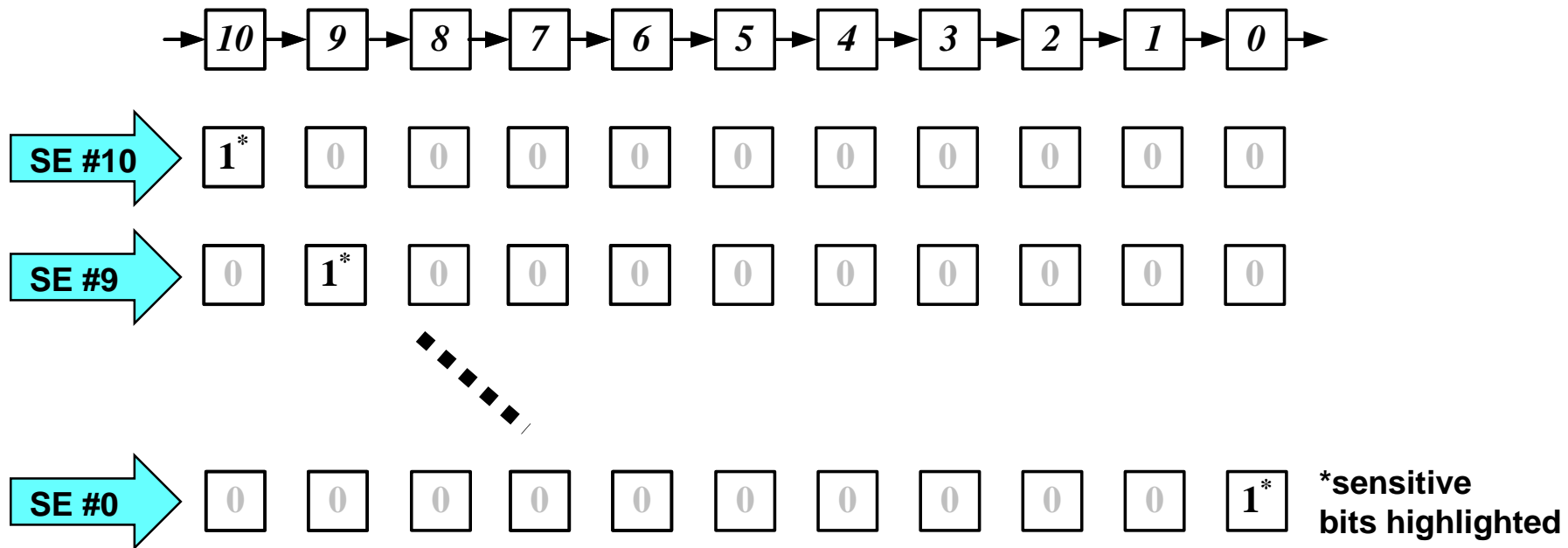
# Single-Excitation Patterns [Li 05]

- Assume: faulty SC and fault model is already known by flush test
- Load **single-excitation (SE)** patterns to faulty SC
  - ♦ SE pattern has only one **sensitive-bit** can be flipped by fault
  - ♦ Generate test pattern to detect SA fault at sensitive bit
- Example: SE patterns for **SA0**



**Turn Diagnosis into SSF ATPG Problem**

# Diagnosis Resolution

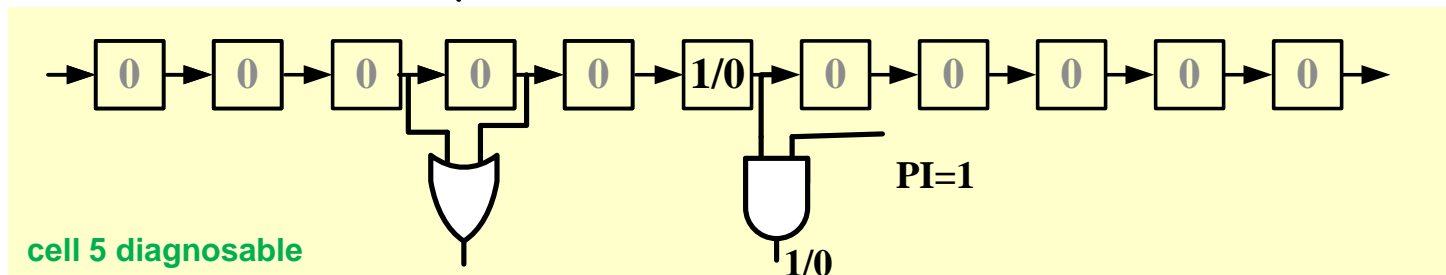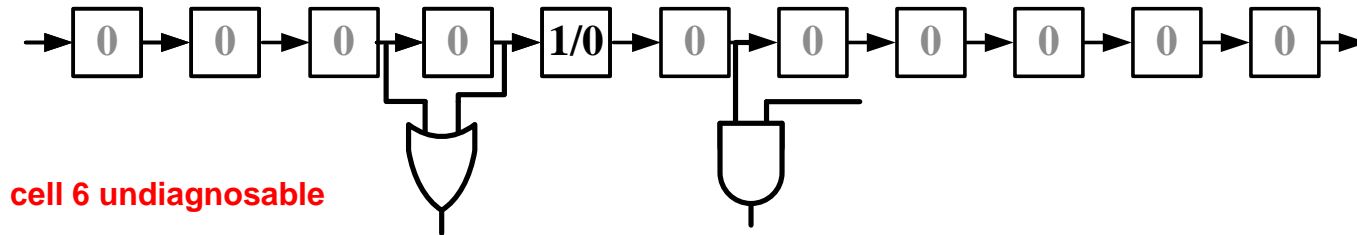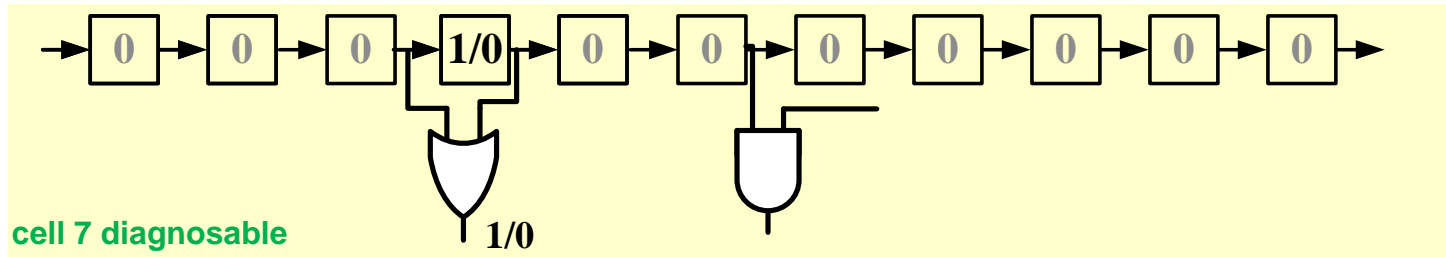

$$\text{DiagnosisResolution} = \frac{\text{total number of cells}}{\text{number of diagnosable cells}} = \frac{11}{5} = 2.2$$




# Summary

- Scan chains occupies **5%~10%** silicon area
  - ♦ **Scan chain faults** occur in scan chains, not logic
  - ♦ Testing (and diagnosis) of scan chain faults is important
- **Scan chain integrity test (flush test)**
  - ♦ Shift in **00110011...** alternating test patterns. No capture
- Diagnosis techniques
  - ① Sequential ATPG (Not practical)
  - ② Simulation-based
    - \* X simulation: determine **UB** and **LB** (useful for large ckt)
    - \* **Single excitation** pattern (solvable by SSF ATPG)

# FFT

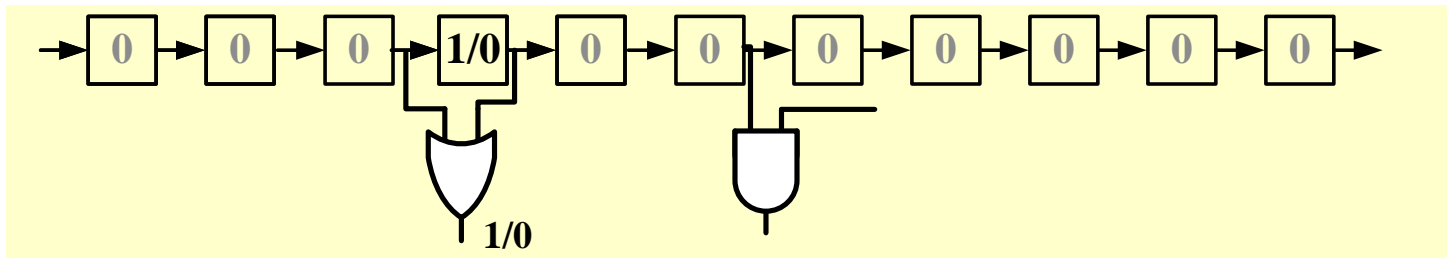- Q1: Since scan chain faults do not effect logic operation, why bother to test them?
- Q2: If scan cell has SA fault, can we detect by regular logic testing?
  - ◆ why bother to generate single excitation pattern?
  - ◆ e.g. this fault can be detected by regular ATPG for OR gate



# Quiz

**Q: Given the same circuit. Use Sequential ATPG, to diagnose if there is SA0 downstream to  $FF_0$ ?**

**ANS:**

