


# Combinational ATPG

- Introduction
- Deterministic Test Pattern Generation
  - ◆ Boolean difference \*
  - ◆ Path sensitization \*\*
  - ◆ D-Algorithm\*\*
  - ◆ PODEM\*\*
  - ◆ FAN\*\*
  - ◆ SAT-based \*
- Acceleration Techniques
- Concluding Remarks

**Two ATPG categories:**


**\*Boolean-based methods**

**\*\*Path-based methods**

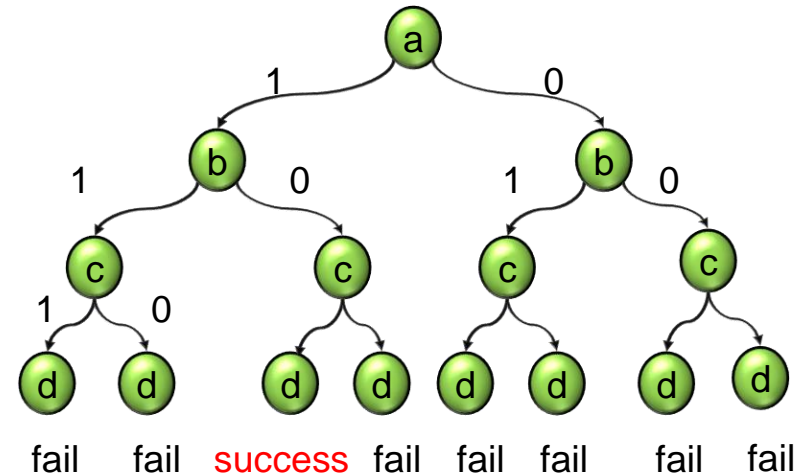

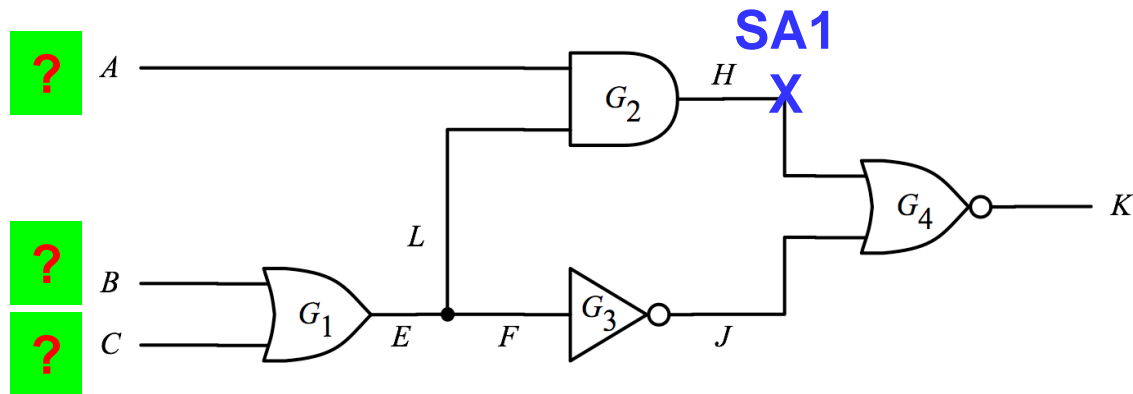
# Motivating Problem

- **We do not need to know Boolean expression**
  - ◆ **we can just find a test from circuit netlist**


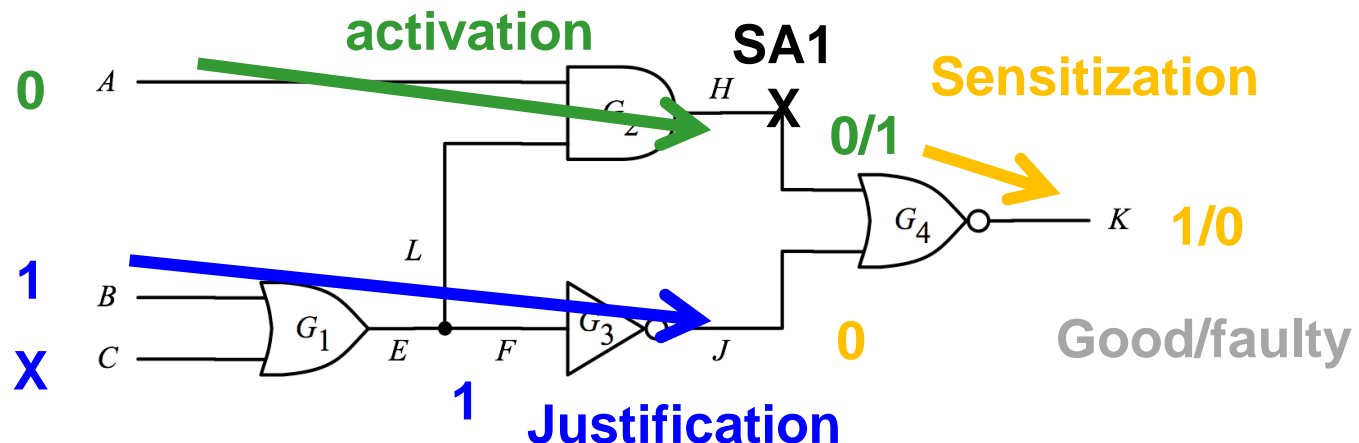
# Let's Analyze What We Did

- **Fault activation:** Assign gate inputs to generate appropriate value at fault site ( $H$ )
  - ♦  $A=0$
- **Sensitization:** Assign side-inputs to non-controlling value to propagate fault effect forward
  - ♦  $J=0$
- **Justification:** Assign primary inputs to achieve desired values
  - ♦  $B=1$



# Single Path Sensitization

- Single path sensitization (SPS) Algorithm:

- ① ***Fault activation*** (aka. ***Fault excitation***)

Assign gate inputs to generate value at fault site

Desired value opposite to the faulty value (e.g. 0 for SA1)

- ② ***Fault effect propagation***:

Select **one single path** from fault site to an output

Assign side inputs to sensitize fault effect along the path


- ③ ***Justification***:

Assign primary inputs to justify desired values assigned in

①&②

If justification fails, **backtrack**.

# Example

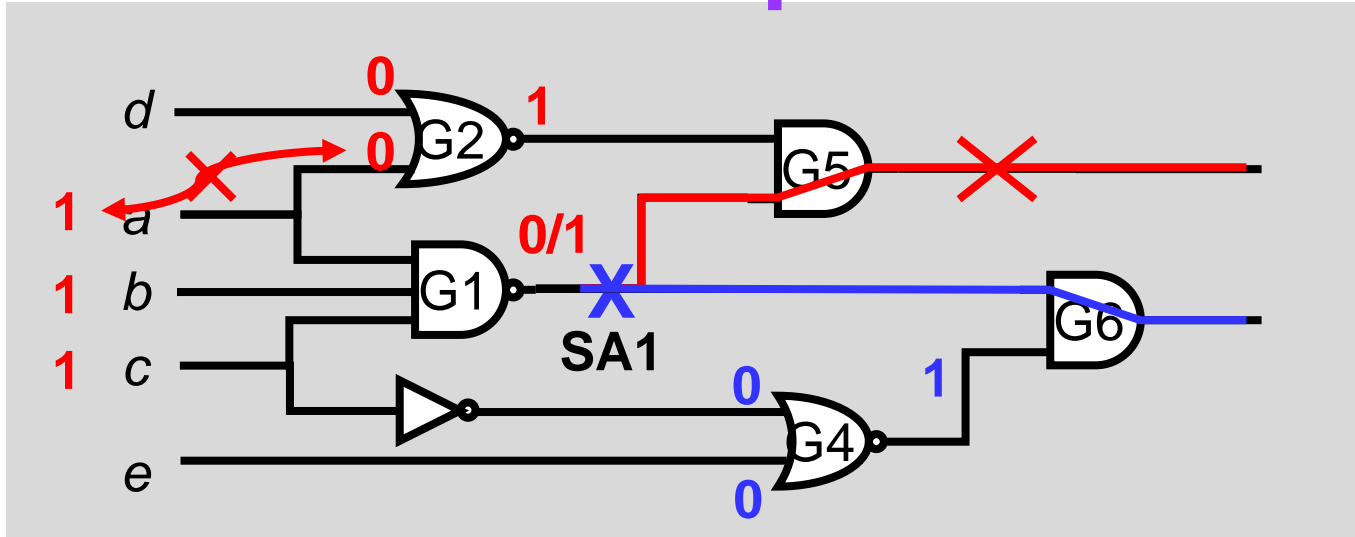

Consider stuck-at-1 fault

① Fault activation

♦  $a = b = c = 1$

② Fault effect propagation: two propagation paths

♦ Choose path {G5}. Want  $G2 = 1$

③  $a = d = 0 \rightarrow$  justification fails!

② Backtrack! Choose another path {G6}. Want  $G4 = 1$

③  $c = 1, e = 0 \rightarrow$  justification succeeds

♦ test pattern:  $abce'$  generated


# Quiz

Q1: Generate a test pattern for *E* SA1 fault. Choose path **ELHK**.

A:

Q2: (Cont'd) Backtrack to another path **EFJK**.


A:

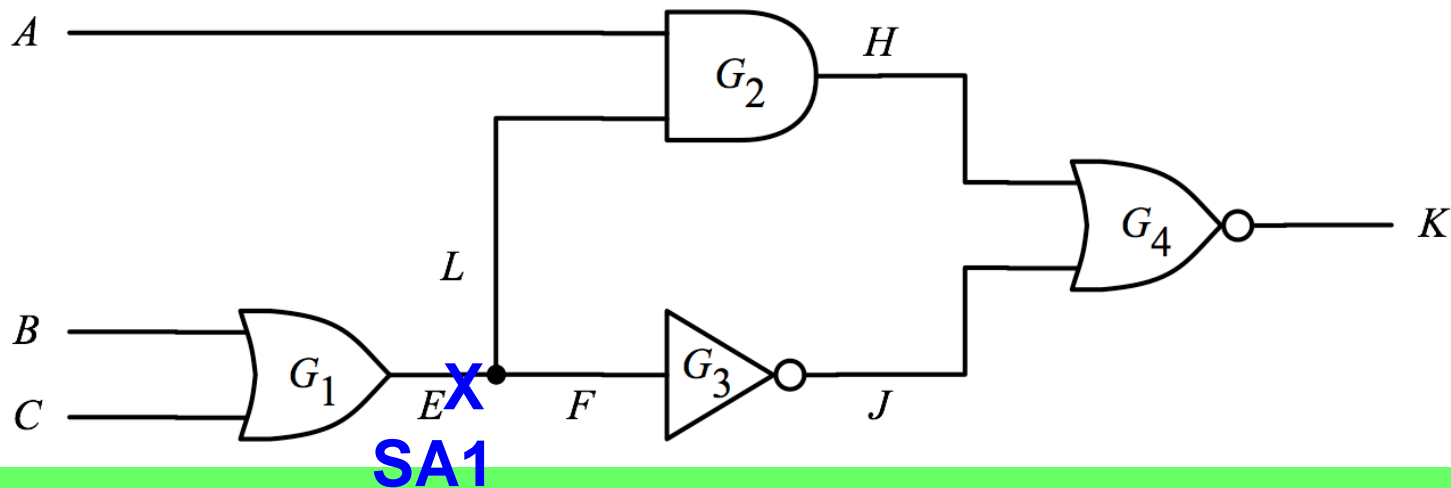

**Important to Choose Correct Path**


But it is difficult...

# Backtrack

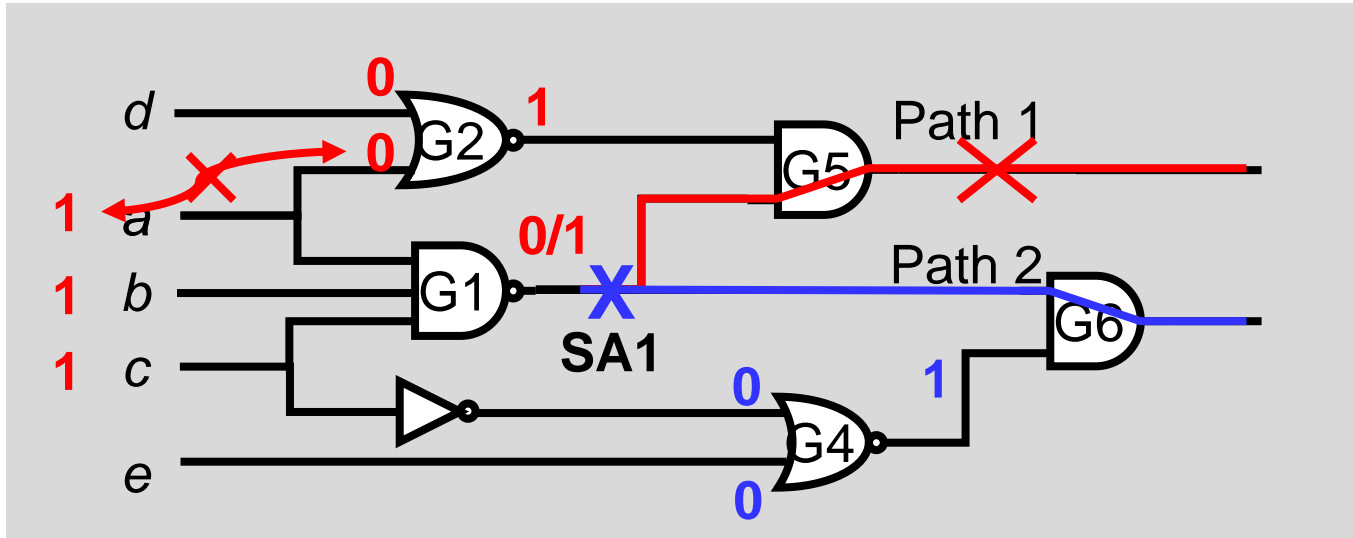

- When we made a mistake in decision tree, **conflict** occurs

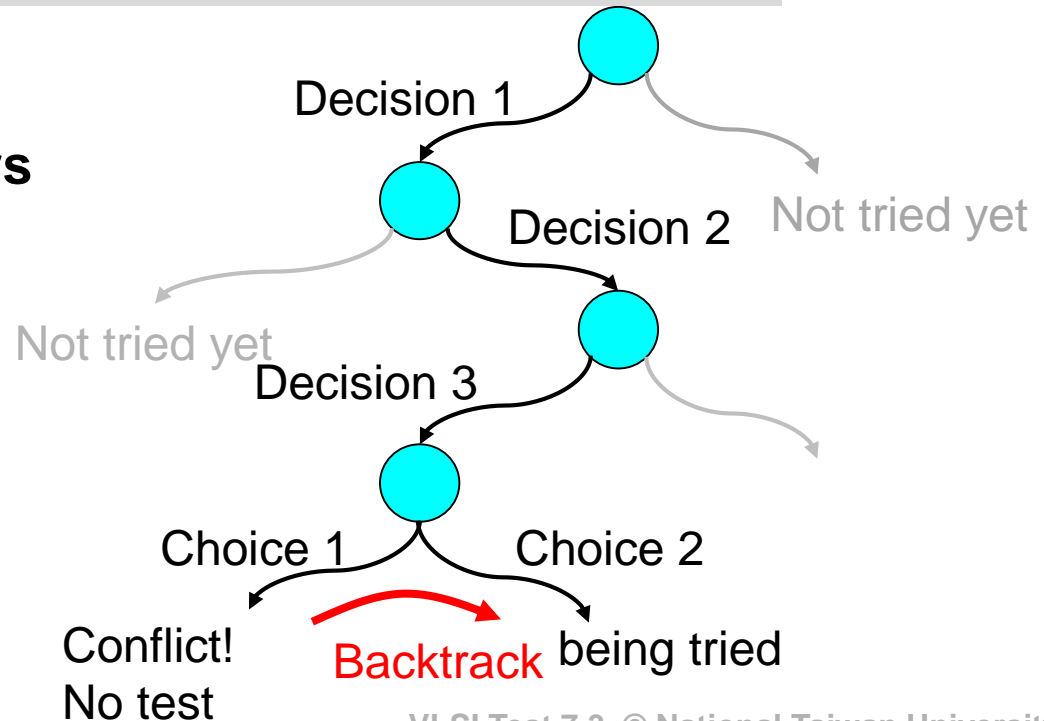- Go back to a previous decision point
- Change decision
- Redo the rest



# Pros and Cons

## 😊 Pros

- ◆ Easy to implement
- ◆ No Boolean equation needed

## 😞 Cons


- ◆ Q1: Too many paths to choose, which one is correct?
- ◆ Q2: Single-path sensitization not enough to detect all faults

- Single path sensitization (SPS) Algorithm:
  - ① **Fault activation** (aka. **Fault excitation**)  
Assign internal signals to generate value at fault site  
Desired value opposite to the faulty value
  - ② **Fault effect propagation**:  
Select **one single path** from fault site to an output  
Assign internal signals to sensitize fault effect along the path
  - ③ **Justification**:  
Assign primary inputs to justify signal values assigned in ①&②  
If justification fails, **backtrack**.


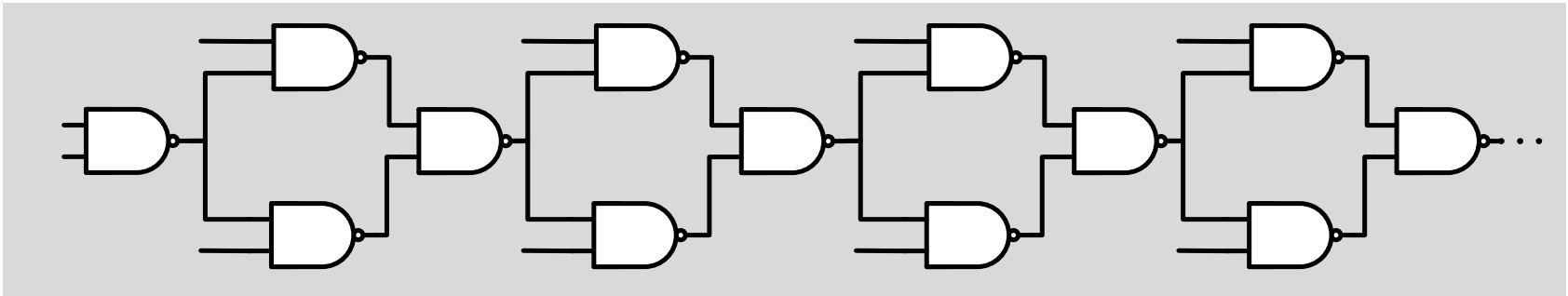
# Q1: Too Many Paths !

- How to choose correct path?
  - ♦ No smart algorithm
  - ♦ Simple idea: exhaustively try all paths
- How many paths in a circuit?
  - ♦ Worst case example:  $3n$  gates,  $2^n$  paths! ( $n = \#$  of stages)




**# of Paths is Exponential to Circuit Size!**  
**Impossible to Try All**

## Q2: Single Path Not Enough

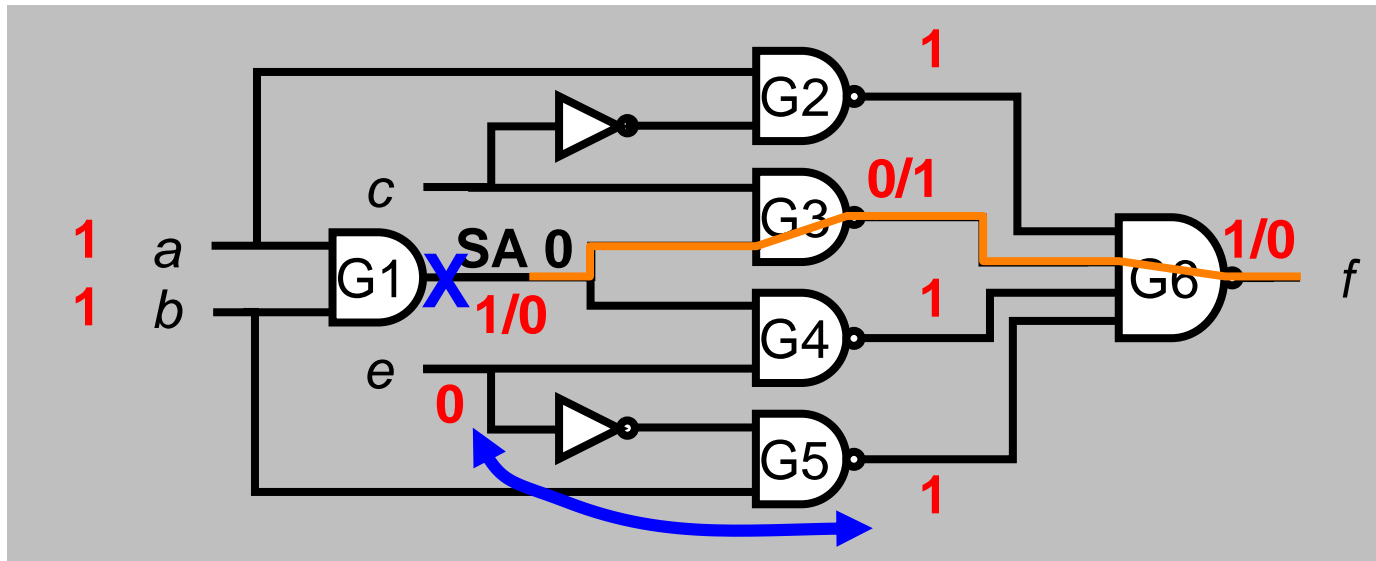- Example


- ① Fault activation:  $a = b = 1$
  - ② Fault propagation: Choose path **{G3-G6}**. want  $G2 = G4 = G5 = 1$
  - ③  $G4 = 1 \rightarrow e = 0 \rightarrow G5 = 0 \rightarrow$  justification fails
  - ② Choose another path **{G4-G6}**. Justification also fails.
- ◆ SPS algorithm fails



**This Fault Is Actually Testable. Why SPS Fail?**

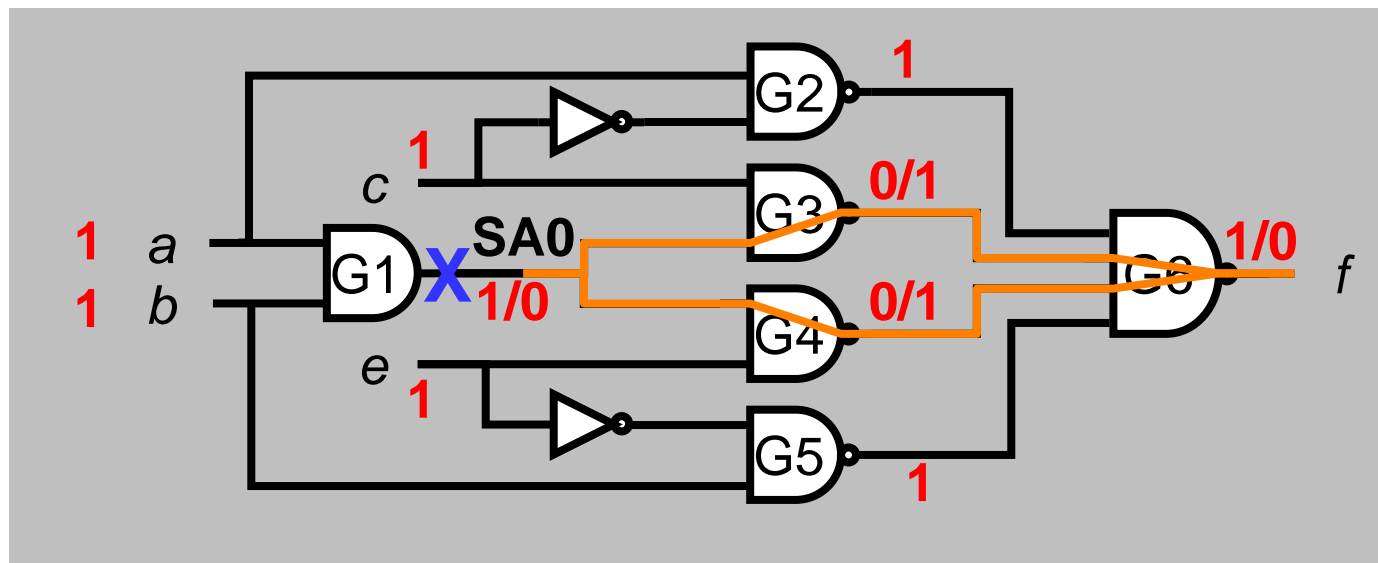
# Solution: Multiple Path Sensitization

- This fault requires *multiple path sensitization*
- Both two paths {G3-G6} and {G4-G6} are sensitized
  - ♦ Error is propagated along both paths simultaneously
  - ♦  $G2 = G5 = 1$  ,  $c = e = 1$
  - ♦ Test generated successfully
- FFT: can we extend 1-path to 2, 3, 4, 5...path sensitization?


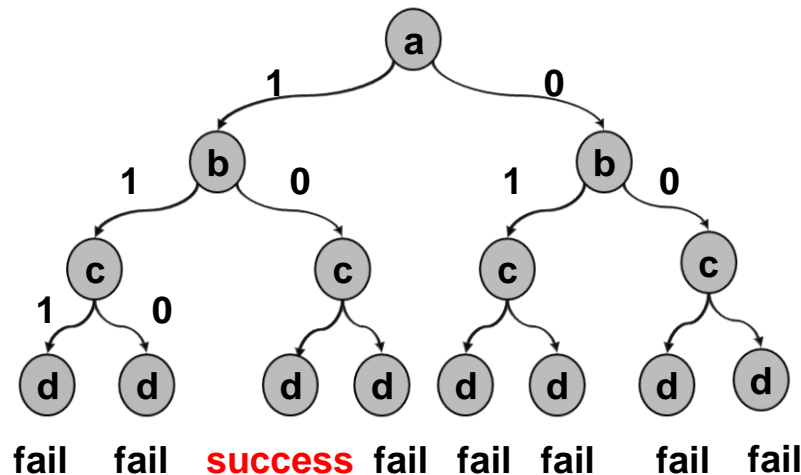
# Complete ATPG Algorithm

- A **complete** ATPG exhausts the whole input space ( $2^n$ )
  - ♦ If a test pattern exists, complete ATPG will find it **for sure**
- An **incomplete** ATPG does **NOT** exhaust the whole input space
  - ♦ ATPG may fail even though a test pattern **DOES** exist




**Complete ATPG Guarantees to Find Solution  
if it exists**

# Quiz

Q: Is Single Path Sensitization a **complete ATPG algorithm**?


Hint: recall this example

- Single path sensitization (SPS) Algorithm:
  - ① **Fault activation** (aka. **Fault excitation**)  
Assign internal signals to generate value at fault site  
Desired value opposite to the faulty value
  - ② **Fault effect propagation**:  
Select **one single path** from fault site to an output  
Assign internal signals to sensitize fault effect along the path
  - ③ **Justification**:  
Assign primary inputs to justify signal values assigned in ①&②  
If justification fails, **backtrack**.

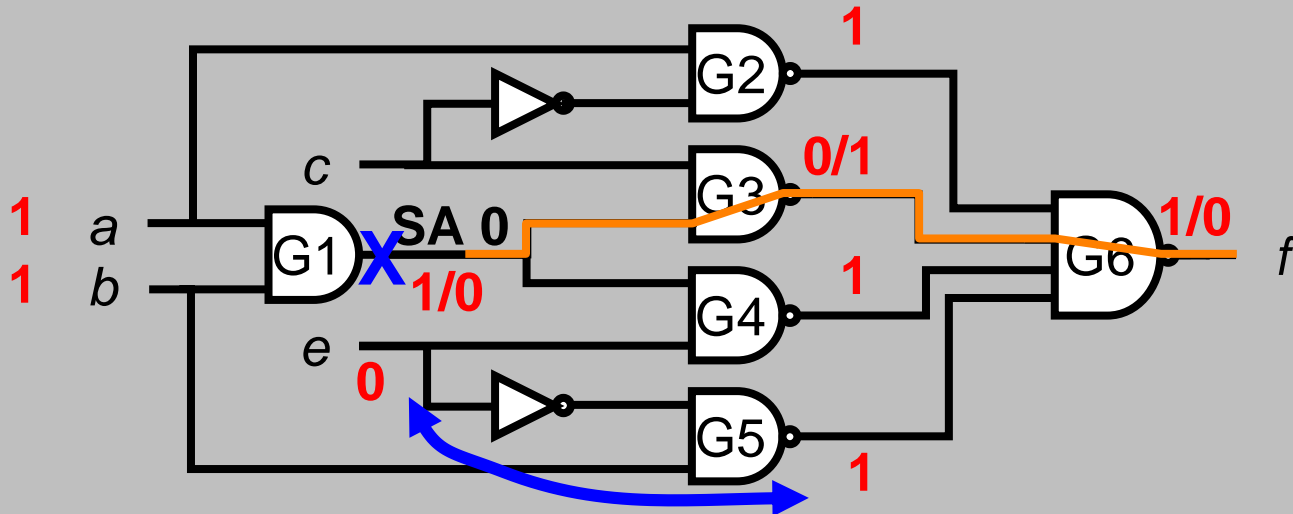
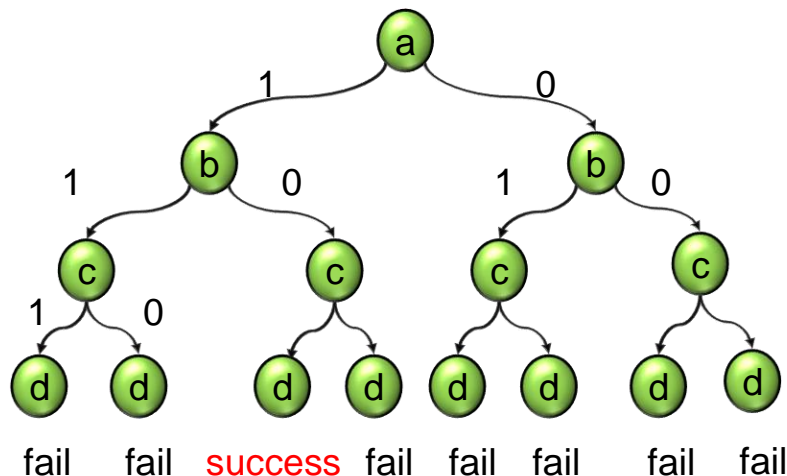
# Summary

- **Single Path Sensitization Algorithm**
  - ① **Fault activation**
  - ② **Fault effect propagation**
  - ③ **Justification**
- **Complete ATPG**: guarantee to find solution if one exists
- **Disadvantages of SPS algorithm**
  - ♦ Number of paths is **exponential** to circuit size. Too many!
  - ♦ Single path sensitization is **incomplete** ATPG



# FFT

- Q1: If SPS fails, can we extend 1-path to 2, 3, 4, 5... paths?
  - ♦ What is the problem for multiple path sensitization algorithm?
- Q2: Pros and Cons of complete ATPG algorithm?
  - ♦ in terms of run time and fault coverage

