



VLSI Testing

積體電路測試

Design For Testability

Part 2: External Scan (JTAG)


Professor James Chien-Mo Li 李建模

Lab. of Dependable Systems

Graduate Institute of Electronics Engineering


National Taiwan University

Course Roadmap (Design Topics)

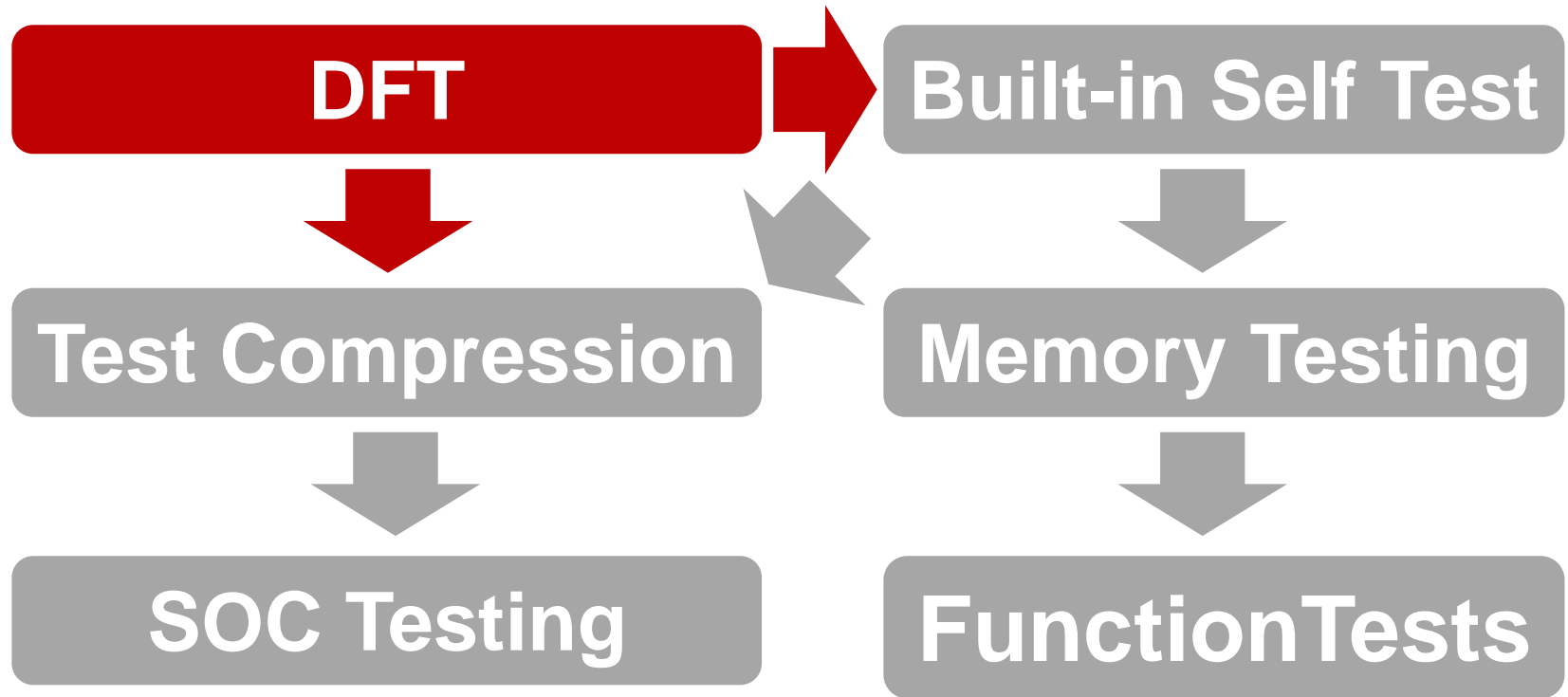

Motivating Problem

 - You buy 6 chips and assemble a board
 - ◆ Your manager asks you to test the board and chips, how?



Why Am I Learning This?


- This chapter allows us to understand
 - ◆ JTAG, IEEE 1149.1 standard
 - ◆ board-level testing

*“In school we learn things then take the test,
In life we take the test then learn things.”*

(Admon Israel)


DFT – Part 2

 - Introduction
- JTAG Architecture and Components
- JTAG Instructions
- Conclusion



What is External Scan ?

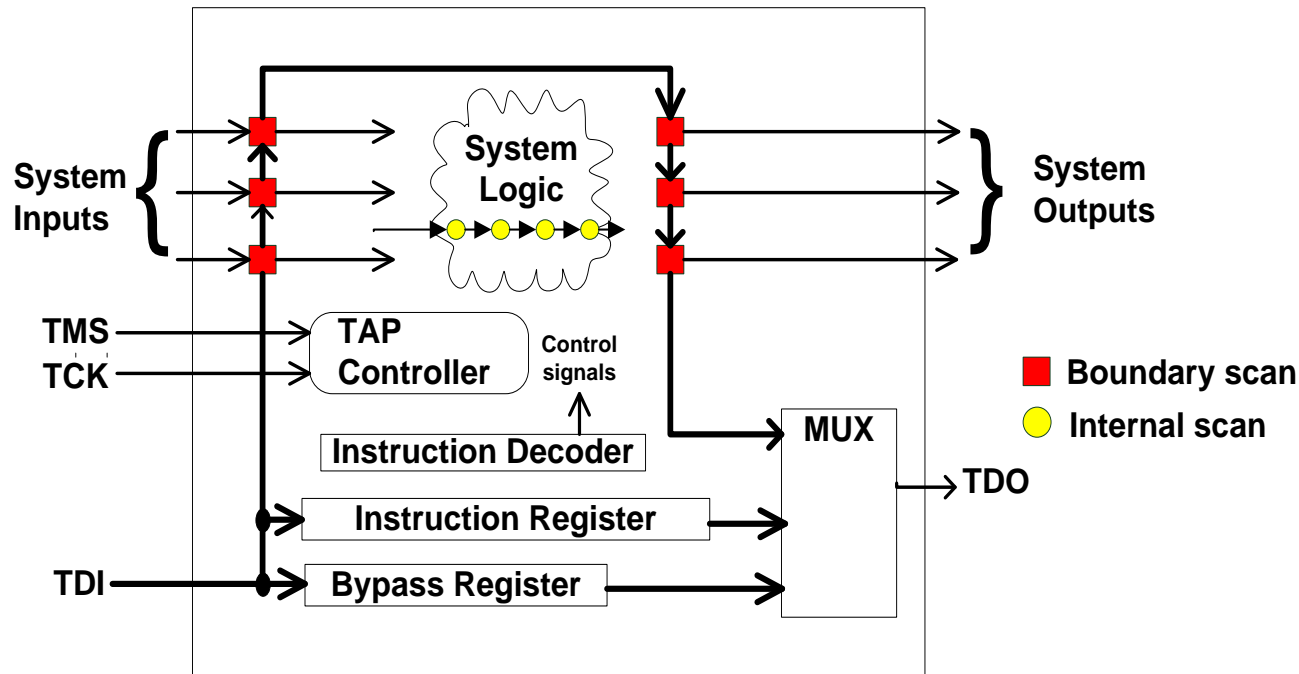- **External scan**
 - ♦ Stitch **system input/output pins** into a shift register
 - * as opposed to *internal scan*
 - ♦ also known as **boundary scan**




Boundary Scan


- Boundary scan standard is needed
 - ◆ Allow chips from **different vendors** to be tested together
- **IEEE 1149.1-1990**
 - ◆ **Boundary scan** standard
 - ◆ aka **JTAG**
- Why use boundary scan?
 - ◆ 1. **Board-level** test and diagnosis
 - ◆ 2. Test on-board **interconnect** among chips
 - ◆ 3. Test on-chip **system logic**

Board Level Test and Diagnosis

 - All chips are stitched into **one JTAG scan chain**
- Off-line testing and on-line debug are supported



Test On-board Wires Among Chips

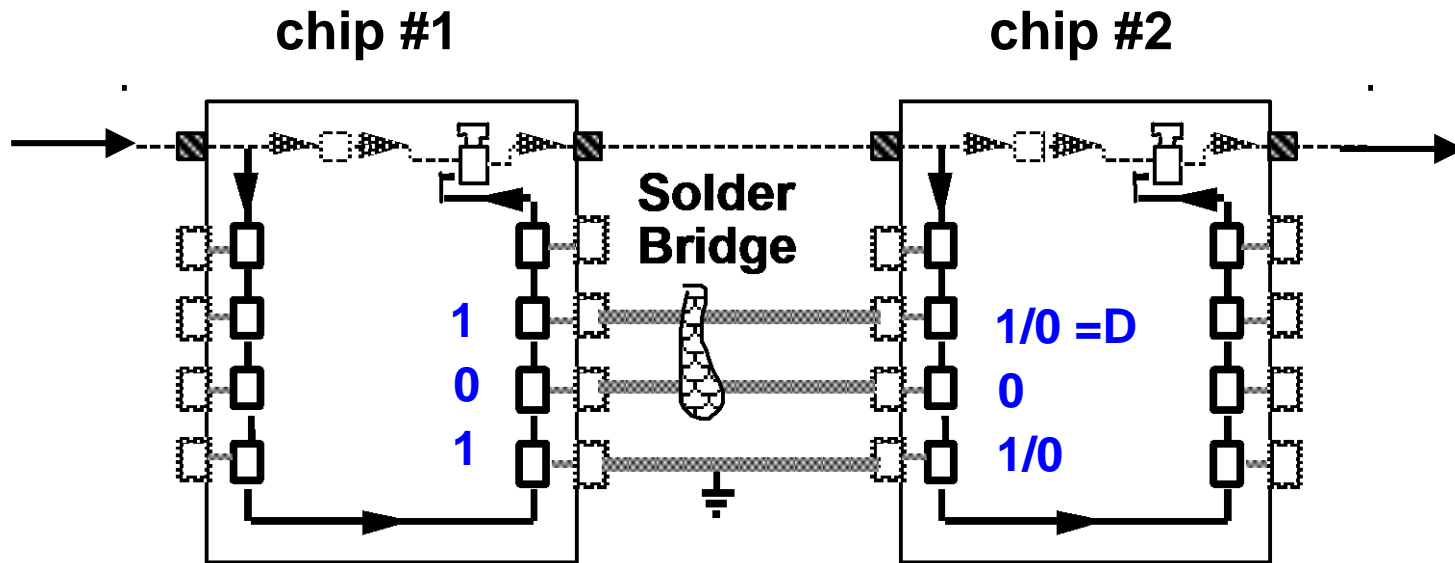


Input: X X X X 1 0 1 X X X X X X X X X ←First scan in
Output: X X X X X X X X X D 0 D X X X X ←First scan out

*assume wired-AND fault model

Test On-chip System Logic

 - How to test a chip already assembled on board. Cannot use ATE



								First scan out									
								First scan in									
							↓									↓	
Input:	X	1	1	X	X	X	X	Good	Output:	X	X	X	X	X	X	1	X
Input:	X	0	1	X	X	X	X	Good	Output:	X	X	X	X	X	X	0	X
Input:	X	1	0	X	X	X	X	Good	Output:	X	X	X	X	X	X	0	X

Quiz


Q: Which of the following is NOT true about boundary scan?

- A. Boundary scan enables board-level testing**
- B. Requires standard because chips are from different vendors**
- C. Boundary scan can replace internal scan**

ANS:

DFT – Part 2

 - Introduction
- JTAG Architecture and Components
 - ◆ TAP
 - ◆ TAP controller
 - ◆ Registers
 - ◆ Instruction Decoder
- JTAG Instructions
- Conclusion



JTAG Architecture

- JTAG Components


- ◆ 1. Test Access Port (TAP)

- ◆ 2. TAP controller

- ◆ 3. Registers


- * Instruction Register, Boundary Scan Register, Bypass Register...

- ◆ 4. Instruction Decoder

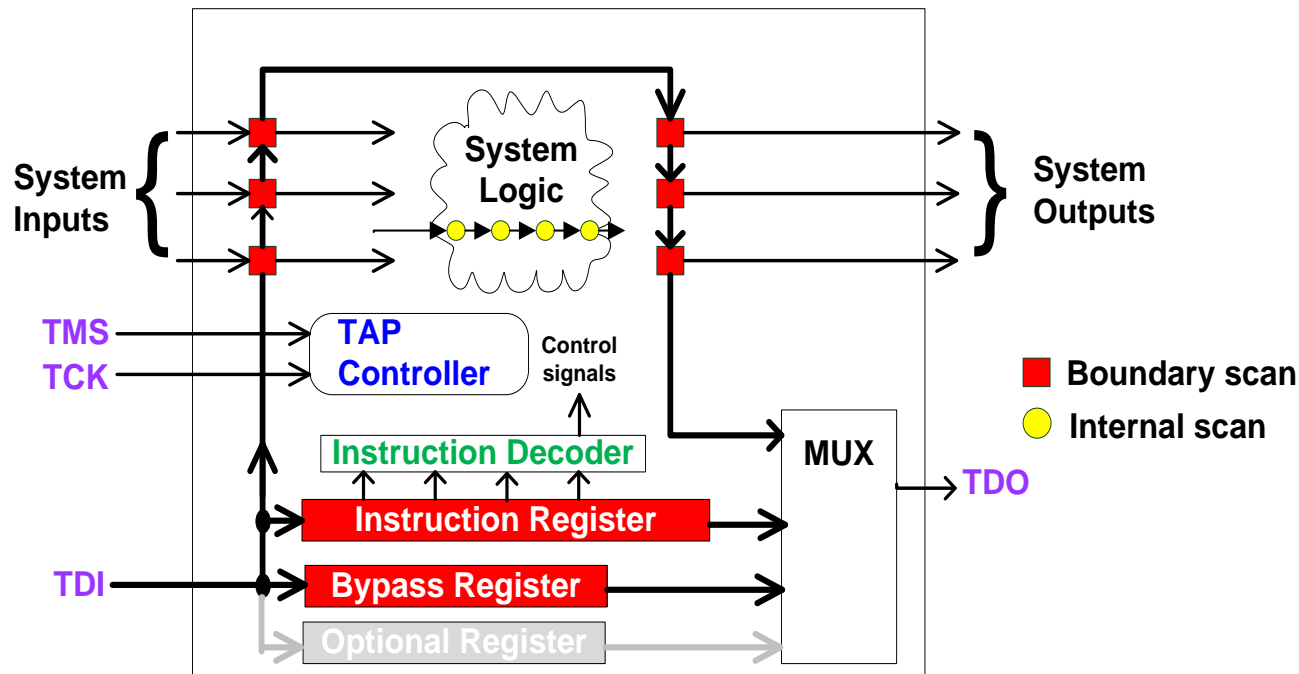

Test Access Port, TAP


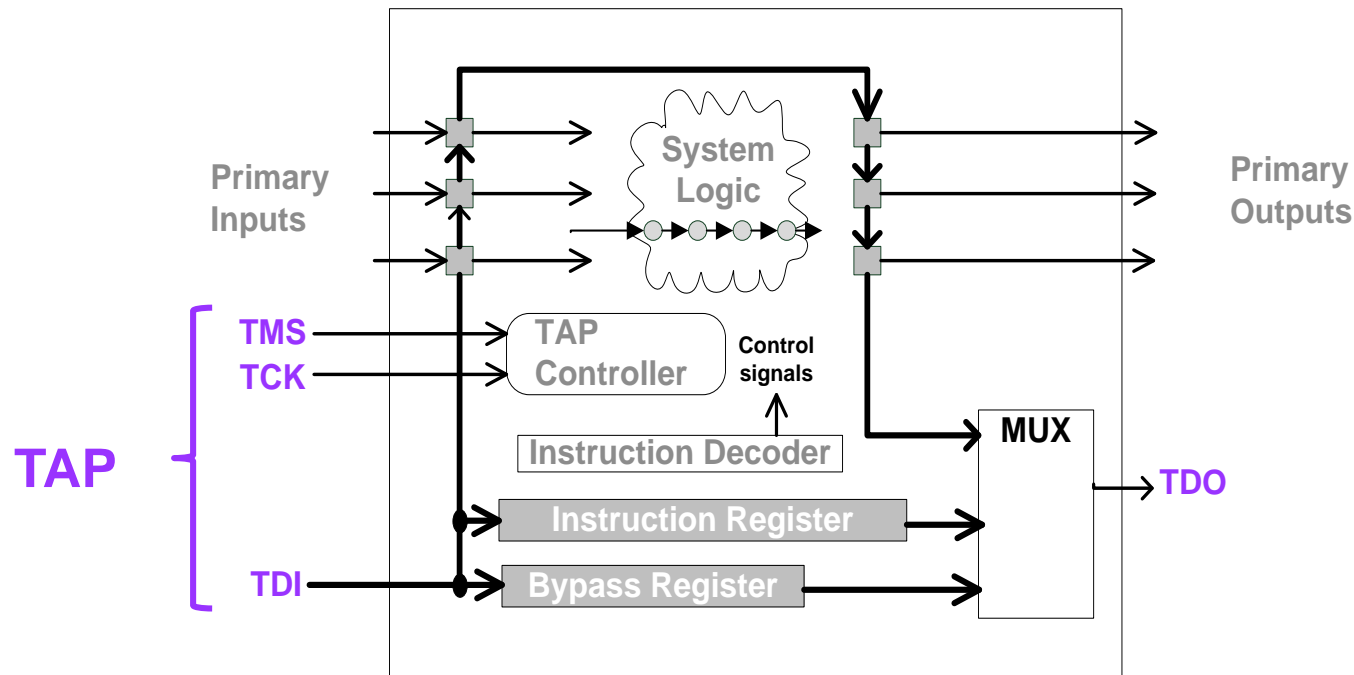
- 4 mandatory TAP
 - ♦ **TDI**, Test Data Input
 - ♦ **TDO**, Test Data Output
 - ♦ **TCK**, Test Clock
 - ♦ **TMS**, Test Mode Select
- 1 optional TAP
 - ♦ **TRST**, Reset of Test Logic (Active Low)



TAP Controller

- Control JTAG operation
- 16-state Finite State Machine
 - ◆ Clock is TCK
 - ◆ Input is TMS
- Test-Logic-Reset
 - ◆ Reset JTAG Circuits
 - ◆ How to reset JTAG?
 - * TMS=111..., or
 - * TRST = 0

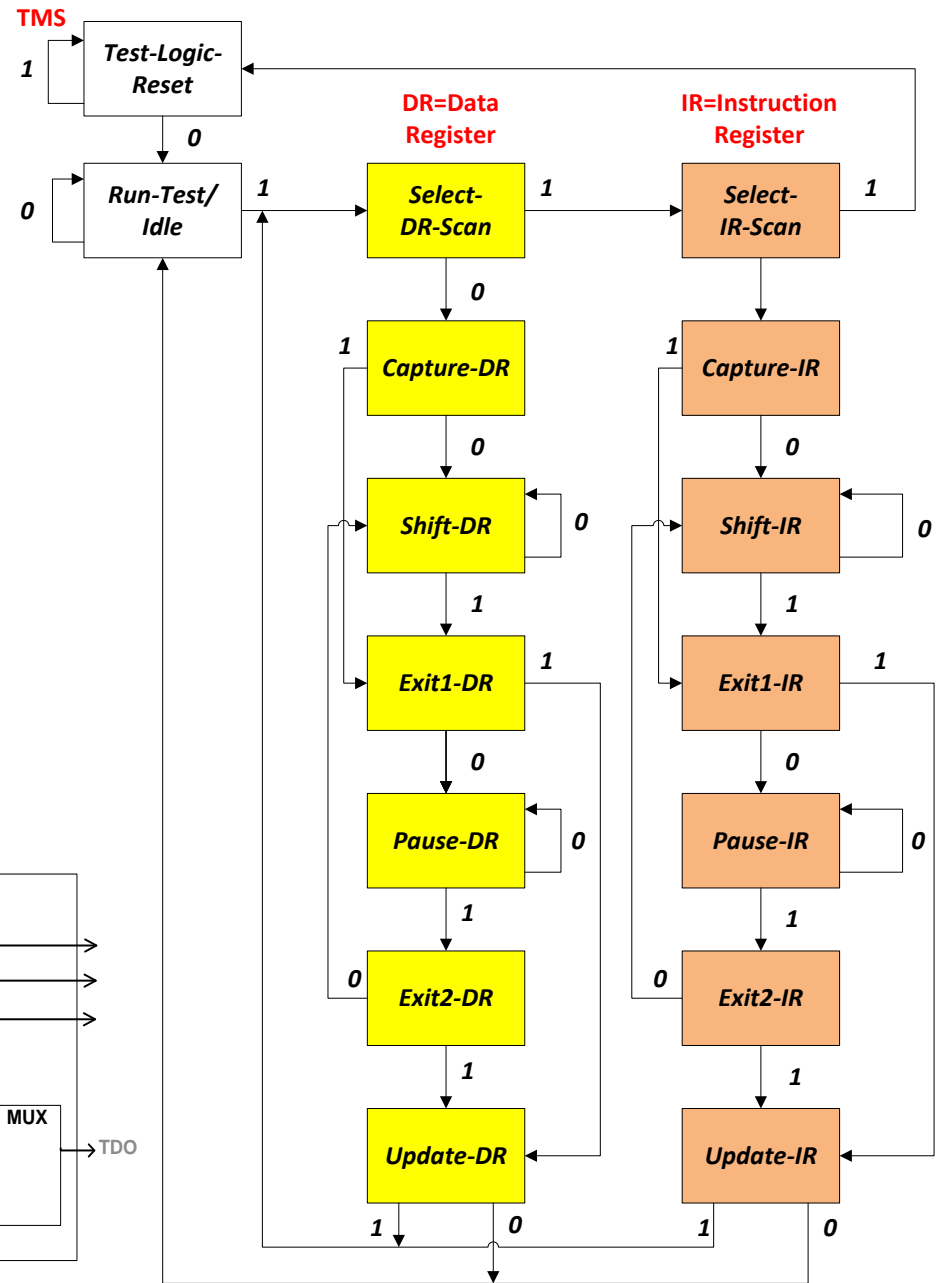 Note:
State transition
occurs at rising
edge of TCK



Summary

- **IEEE 1149.1-1990**
 - ♦ **Boundary scan** standard
 - ♦ aka **JTAG** (*Joint Test Action Group*)
- Why use boundary scan?
 - ♦ **Board-level, interconnect, system logic**
- JTAG components
 - ♦ 1. **Test Access Port (TAP)**
 - ♦ 2. **TAP controller** (16-state FSM)
 - ♦ 3. Registers
 - ♦ 4. Instruction Decoder

FFT

- Q: What is mini number of 1's needed to initialize JTAG?
Regardless of initial state.

- ◆ TMS=111...

