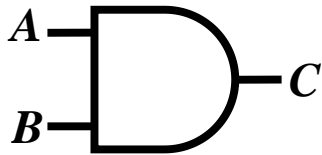


# Fault Collapsing


- Introduction
- Equivalence Fault Collapsing
  - ◆ Fanout-free circuits
  - ◆ Circuits with fanouts
- Dominance Fault Collapsing
  - ◆ Fanout-free circuits
  - ◆ Circuits with fanouts
- Checkpoint Theorem (1976)
- Conclusion

# Fault Dominance

- **Detecting set of fault  $f$  ( $T_f$ )** = set of all test patterns that detect fault  $f$
- Fault  $f$  **dominates** fault  $g$  if the detecting set of  $f$  contains that of  $g$ 
  - ♦  $T_f \supseteq T_g$
- Example: **C/1 fault dominates A/1 fault**
  - ♦ C/1 detecting set {00, 01, 10} contains A/1 detecting set {01}
  - ♦ C/1 is **dominating fault**; A/1 is **dominated fault**



Input		Output						
A	B	good	A/0	C/0	B/0	A/1	C/1	B/1
0	0	0	0	0	0	0	<u>1</u>	0
0	1	0	0	0	0	<u>1</u>	<u>1</u>	0
1	0	0	0	0	0	0	<u>1</u>	<u>1</u>
1	1	1	<u>0</u>	<u>0</u>	<u>0</u>	1	1	1

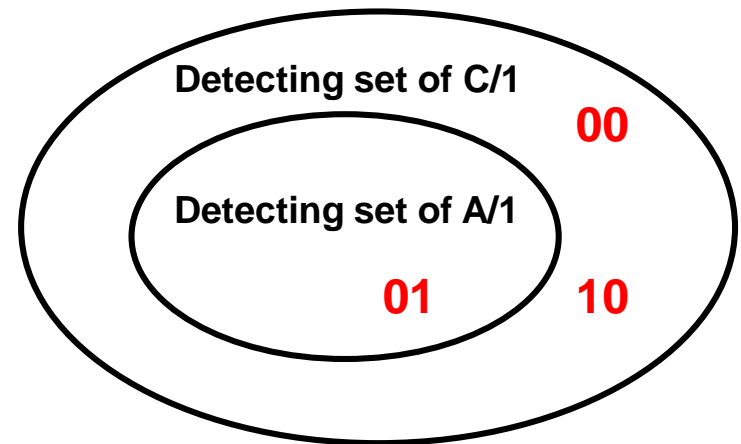

# Quiz

Q: Is dominance relation transitive?

if  $f$  dominates  $g$ , and  $g$  dominates  $h$ , then  $f$  dominates  $h$ ?


A:

Q: Is dominance relation symmetric?

if  $f$  dominates  $g$ , then  $g$  dominates  $f$ ?

A:

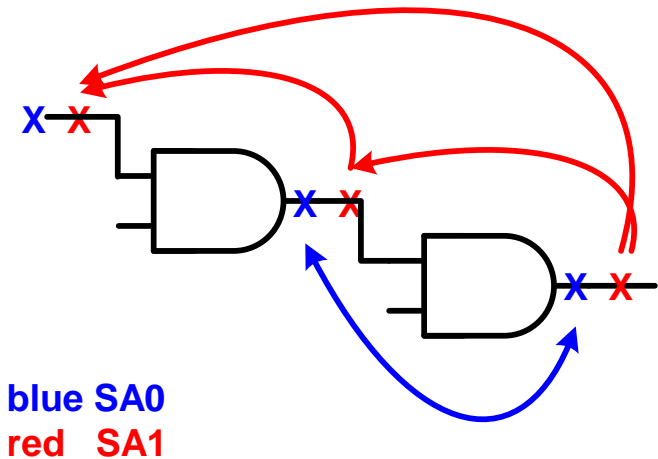
$f \leftrightarrow g$ : equivalence  
 $f \rightarrow g$ : dominance



# Dominance Fault Collapsing, DFC

- DFC reduces fault list using fault dominance relation
  - ♦ If a test pattern detects a *dominated fault*, then it must detect its *dominating fault*. So **dominating faults can be removed** for ATPG
- Example:
  - ♦ **C/1** fault can be removed. Similarly, **A/0**, **B/0** also removed
  - ♦ Minimum {A/1, B/1, C/0} 3 faults remains after DFC


Input		Output						
A	B	Good	A/0	C/0	B/0	A/1	C/1	B/1
0	0	0	0	0	0	0	<u>1</u>	0
0	1	0	0	0	0	<u>1</u>	<u>1</u>	0
1	0	0	0	0	0	0	<u>1</u>	<u>1</u>
1	1	1	<u>0</u>	<u>0</u>	<u>0</u>	1	1	1

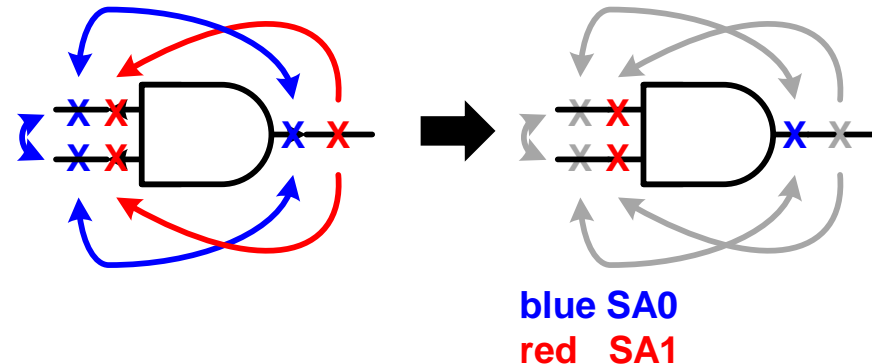


**Minimum 3 faults after DFC**
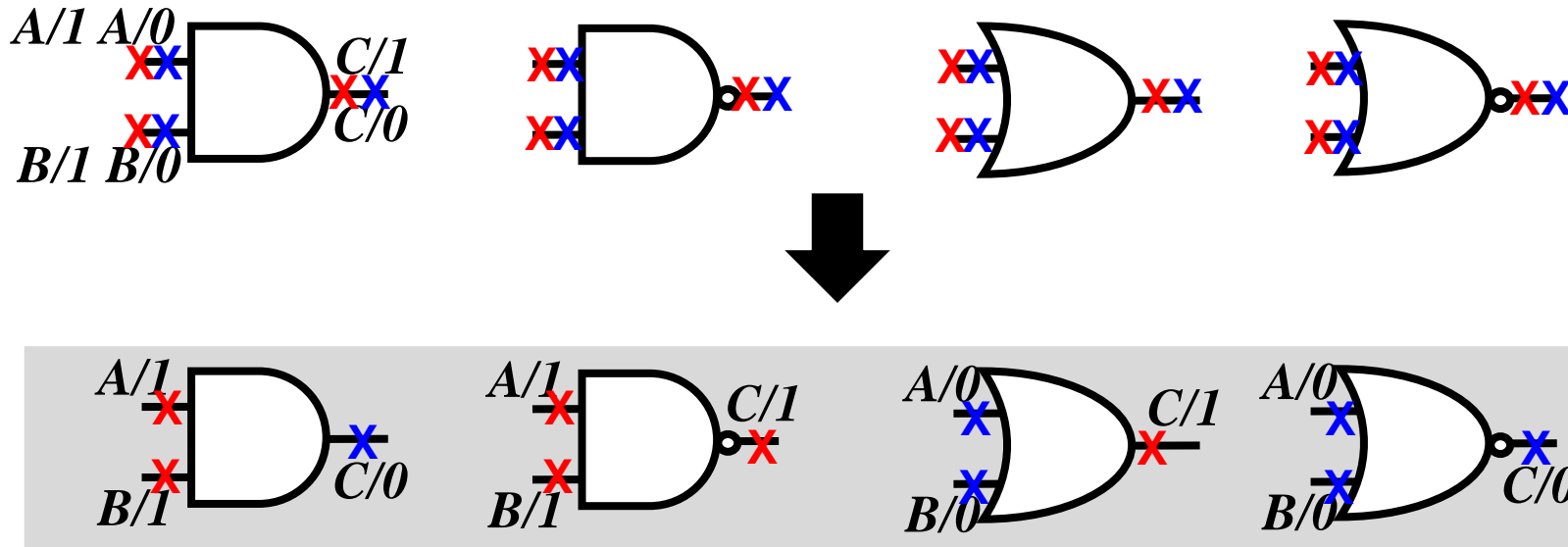
# DFC on Elementary Gates

- 2-input AND/OR/NAND/NOR elementary gates
  - ♦ Originally 6 faults  $\rightarrow$  4 faults after EFC  $\rightarrow$  3 faults after DFC
- For  $n$ -input elementary gate,
  - ♦  $n+1$  stuck-at faults after DFC





# DFC on Fanout-free Circuits

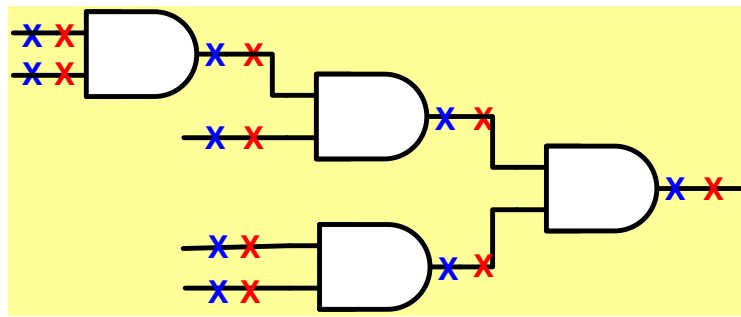


blue SA0  
red SA1

push to PI

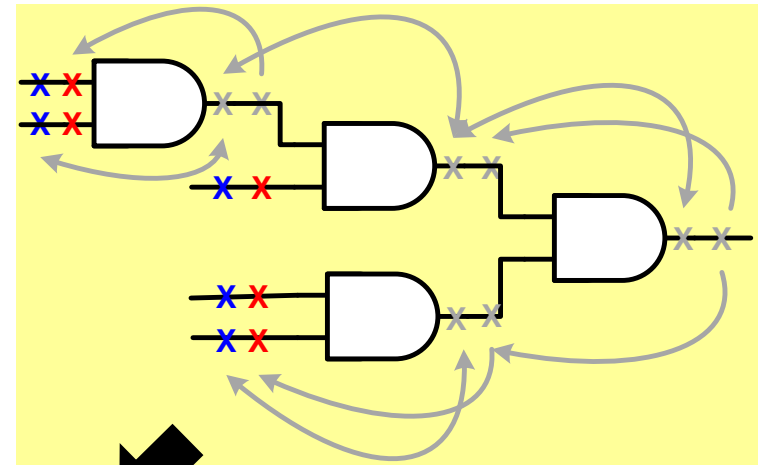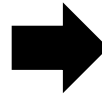

all-PI gates reduce further

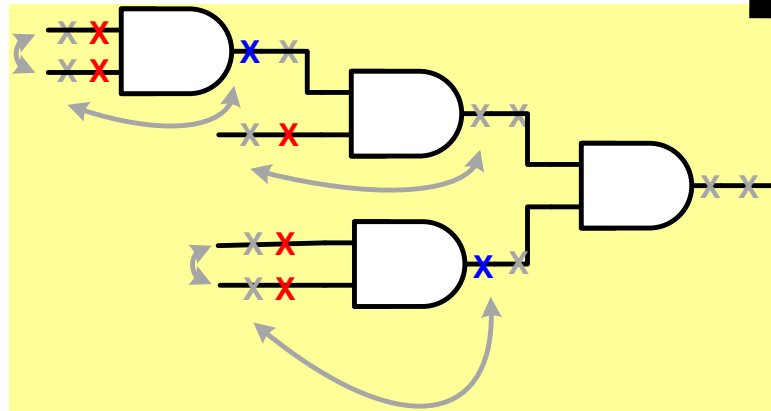


- Two observations:
  - ① All gate input faults removed; except **primary inputs**
  - ② All gate output faults removed; except **all-PI gates**
- This is also applicable to other elementary gates. Why? FFT

# DFC Rules for Fanout-free Circuits

## DFC Rules


- (1) **one** DFC collapsed fault for **every primary input**
- (2) **one** DFC collapsed fault for each **all-PI gate output\***

\*all-PI gate = gate inputs are all PI

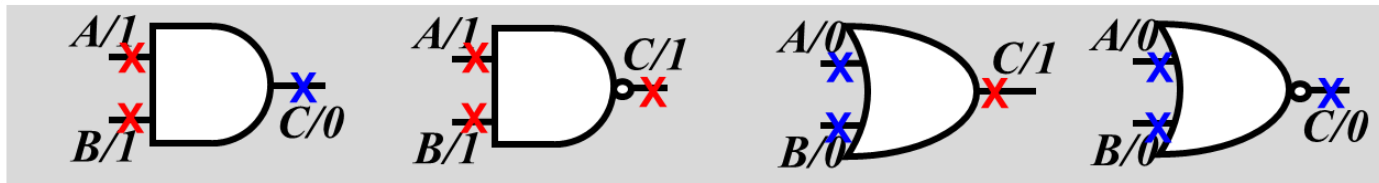





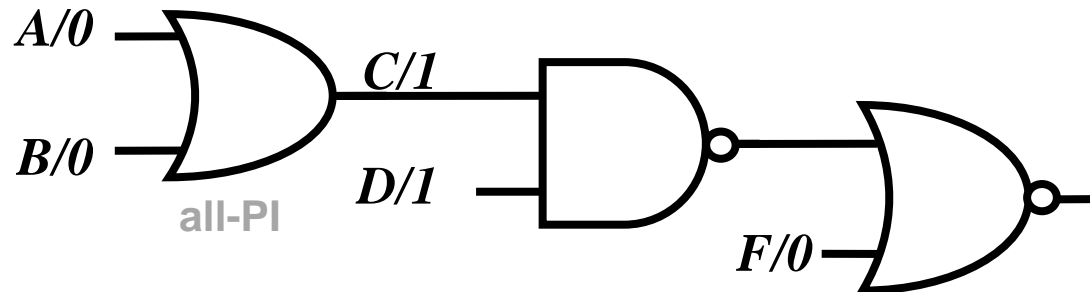
- **Example**

- ◆ Original **14** faults → **8** faults after EFC → **5** faults after DFC


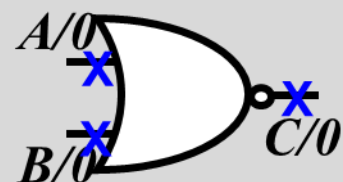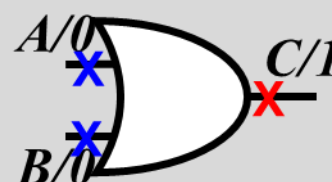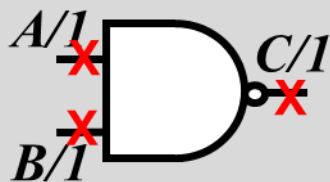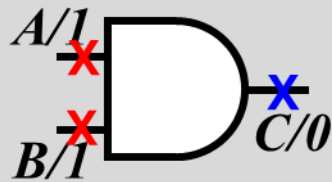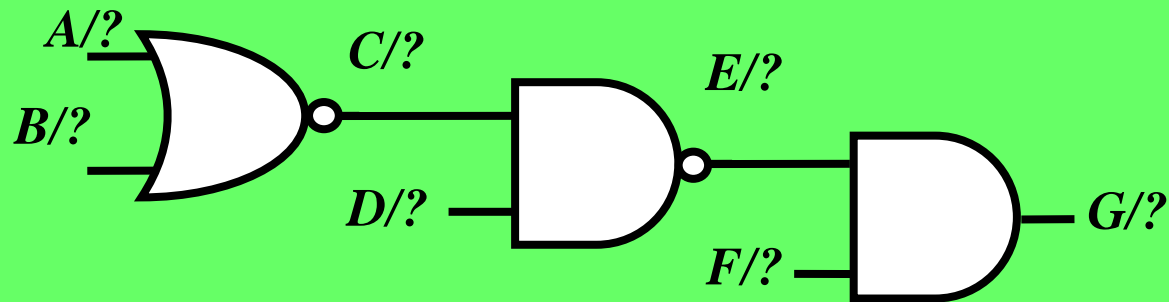
# Quiz

Q: Please perform DFC on this fanout-free circuit. (Please label their stuck- values)






# Fault Collapsing

- Introduction
- Equivalence Fault Collapsing
  - ◆ Fanout-free circuits
  - ◆ Fanout
- **Dominance Fault Collapsing**
  - ◆ Fanout-free circuits
  - ◆ **Circuits with fanout**
- Checkpoint Theorem
- Conclusion

# Fanout Stem and Branches

- Fanout branch faults **do NOT** always dominate fanout stem faults
- Example: ***F/1*** fault dominates ***E/1***. but ***L/1*** fault does not dominate ***E/1***
- Stem analysis*** of fanout faults is time consuming


Input			Output						
A	B	C	good	E/0	F/0	L/0	E/1	F/1	L/1
0	0	0	0	0	0	0	<u>1</u>	<u>1</u>	0
0	0	1	1	<u>0</u>	<u>0</u>	1	1	1	1
0	1	0	1	<u>0</u>	<u>0</u>	1	1	1	1
0	1	1	1	<u>0</u>	<u>0</u>	1	1	1	1
1	0	0	0	0	0	0	0	<u>1</u>	0
1	0	1	0	0	0	<u>1</u>	0	0	0
1	1	0	0	0	0	<u>1</u>	0	0	0
1	1	1	0	0	0	<u>1</u>	0	0	0

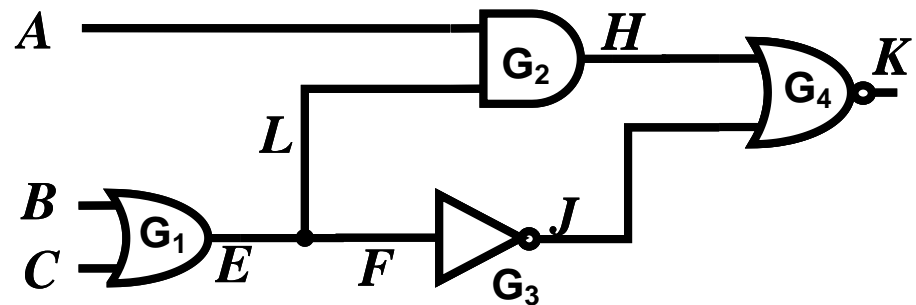

**Hard to Analyze Dominance between Stem and Branches**

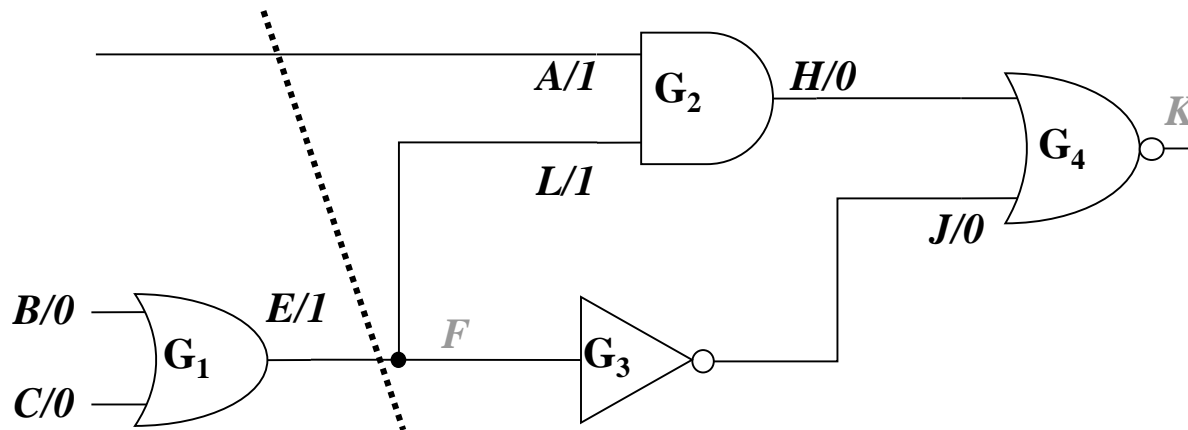
# How to Handle Circuits w/ Fanouts?

- Approximate solution: **Partition** circuit into fanout-free subcircuits
  - ♦ DFC each subcircuit **independently**
- Example:
  - ♦  $J$  is consider input because inverter  $G_3$  is ignored
  - ♦ Original **18** faults,  $\rightarrow$  after EFC **10** faults  $\rightarrow$  after DFC **7** faults
  - ♦ NOTE: this solution is **NOT optimal**
    - \*  $J/0$  is equivalent to  $F/1$ , which dominates  $E/1$


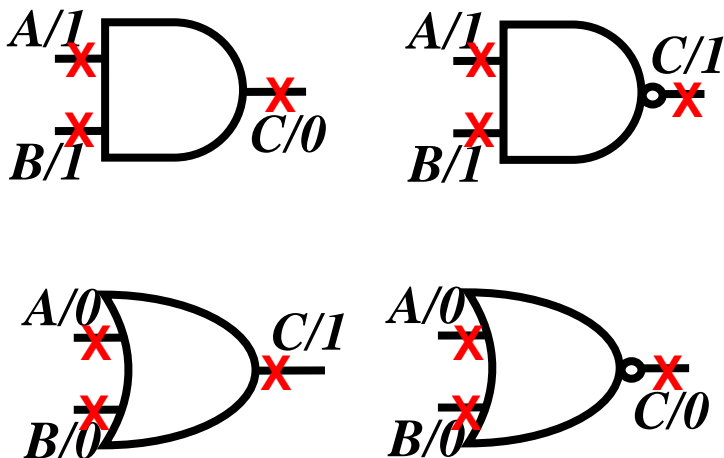
# Simple\_DFC Algorithm

- **Linear time**
- **Does NOT guarantee minimum DFC**
  - ♦ **No stem analysis**




```

Simple_DFC (N) /*N is a netlist*/
0. fault_list = { };
1. foreach gate or PI or PO g in N
2.   if ((g is PI and fanout stem) || (g is PO and fanout branch)) then
3.     fault_list = fault_list ∪ g output stuck-at 0 and 1;
4.   else if (g is gate) then
5.     foreach gate input i of gate g
6.       h = backtrack inverters starting from i;
7.       if (h is PI or fanout branch) then /* rule #1 */
8.         if (gate g is AND) || (gate g is NAND) then
9.           fault_list = fault_list ∪ i stuck-at 1;
10.        else if (gate g is OR) || (gate g is NOR)
11.          fault_list = fault_list ∪ i stuck-at 0;
12.        end if
13.      end if
14.    end foreach
15.    if (every gate input of g has a fault) then /* rule #2 */
16.      if (gate g is AND) || (gate g is NOR) then
17.        fault_list = fault_list ∪ g output stuck-at 0;
18.      else if (gate g is OR) || (gate g is NAND) then
19.        fault_list = fault_list ∪ g output stuck-at 1;
20.      end if
21.    end if
22.  end if
23. end foreach
24. return (fault_list );
    
```
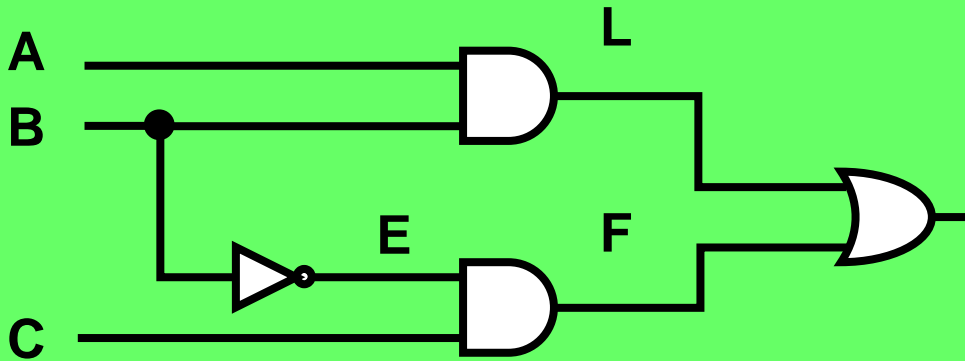
# Quiz

**Q: Please perform DFC on this circuit.  
(Please label their stuck- values)**



Simple\_DFC (*N*) /\**N* is a netlist\*/

```

0. fault_list = {};
1. foreach gate or PI or PO g in N
2.   if ((g is PI and fanout stem) || (g is PO and fanout branch)) then
3.     fault_list = fault_list ∪ g output stuck-at 0 and 1;
4.   else if (g is gate) then
5.     foreach gate input i of gate g
6.       h = backtrace inverters starting from i;
7.       if (h is PI or fanout branch) then /* rule #1 */
8.         if (gate g is AND) || (gate g is NAND) then
9.           fault_list = fault_list ∪ i stuck-at 1;
10.        else if (gate g is OR) || (gate g is NOR)
11.          fault_list = fault_list ∪ i stuck-at 0;
12.        end if
13.      end if
14.    end foreach
15.    if (every gate input of g has a fault) then /* rule #2 */
16.      if (gate g is AND) || (gate g is NOR) then
17.        fault_list = fault_list ∪ g output stuck-at 0;
18.      else if (gate g is OR) || (gate g is NAND) then
19.        fault_list = fault_list ∪ g output stuck-at 1;
20.      end if
21.    end if
22.  end if
23. end foreach
24. return (fault_list );
  
```


# Fault Collapsing

- Introduction
- Equivalence Fault Collapsing
  - ◆ Fanout-free circuits
  - ◆ Fanout
- Dominance Fault Collapsing
  - ◆ Fanout-free circuits
  - ◆ Circuits with fanout
- Checkpoint Theorem
- Conclusion
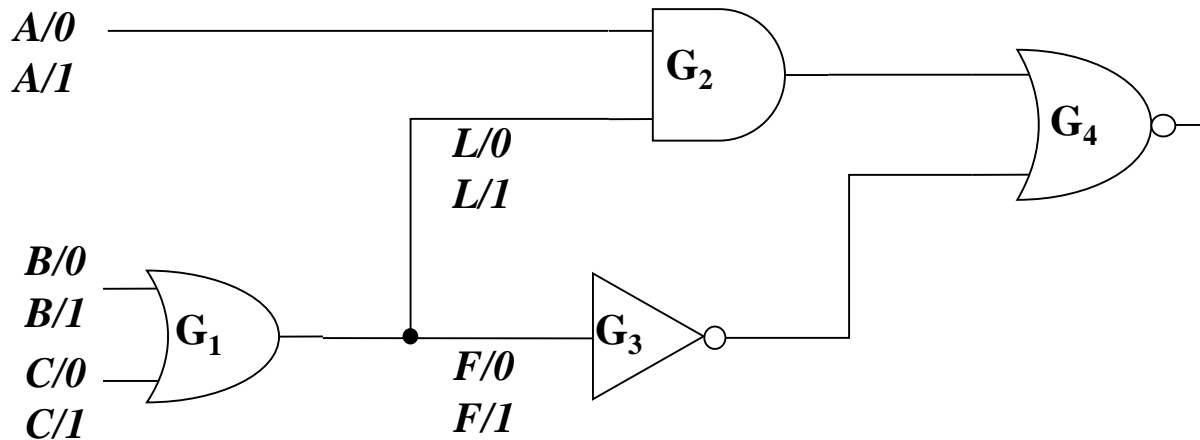
# Checkpoint Theorem [Breuer 76]

If a test detects all SSF on all checkpoints, this test detects all SSF in the circuit.


- Checkpoints = **primary inputs** + **fanout branches**
- Example:
  - ♦ **10** faults on checkpoints
  - ♦ Originally **18** faults, after EFC **10** faults, after DFC **7** faults




$$|\text{CHKPT}| \geq |\text{EFC}| \geq |\text{DFC}|$$
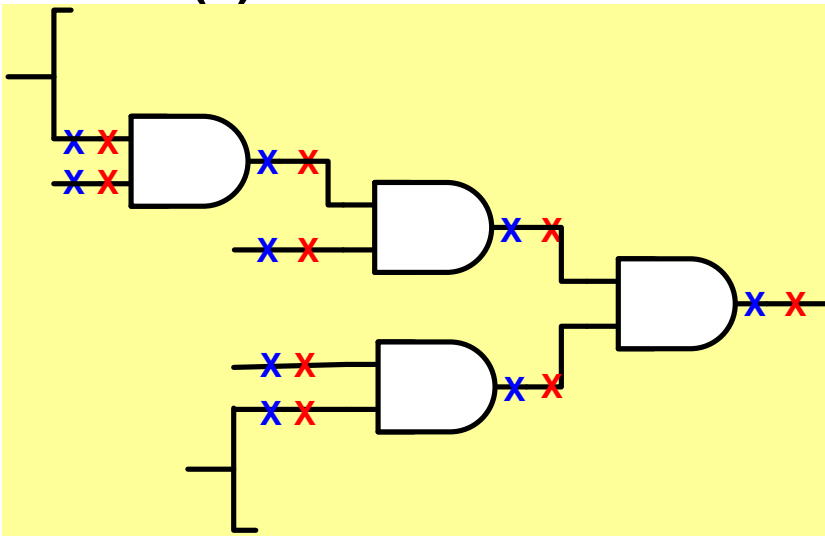
# Proof

- Partition circuit into fanout-free subcircuits
- Use dominance relationship to remove faults from right to left until
  - ◆ (1) PI
  - ◆ (2) Fanout branch



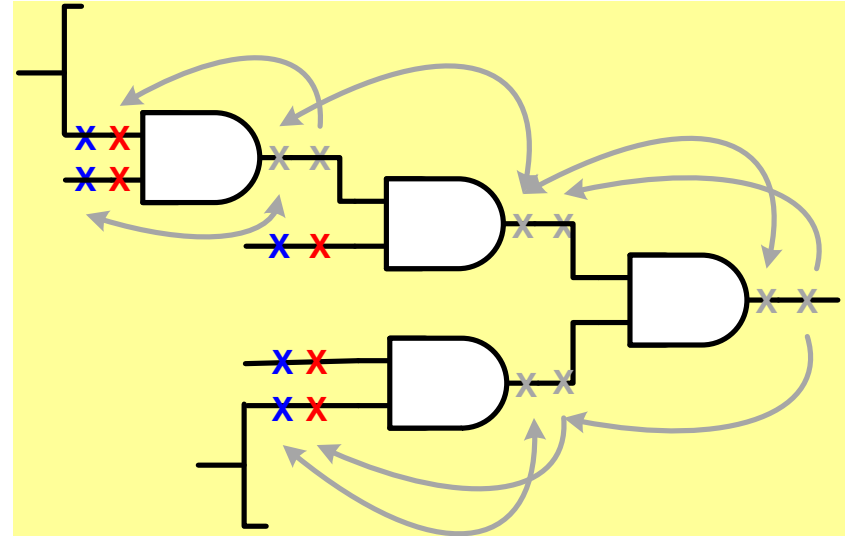\*can be changed to other elementary gates



# Chkpt are Simple Alternative to EFC/DFC



# Fault Collapsing

- Introduction
- Equivalence Fault Collapsing
  - ◆ Fanout-free circuits
  - ◆ Fanout
- Dominance Fault Collapsing
  - ◆ Fanout-free circuits
  - ◆ Circuits with fanout
- Checkpoint Theorem
- **Conclusion**

# Example ATPG Report

	uncollapsed	Collapsed (typically EFC)
<b>Total Faults</b>	1,234	800
<b>Detected faults</b>	1,000	700
<b>Untestable faults</b>	230	98
<b>Aborted faults</b>	4	2
<b>Fault Coverage</b>	1,000/1,234	700/800

*CollapseRatio*

$$= \frac{\text{number of } \textit{collapsed} \text{ faults}}{\text{number of } \textit{uncollapsed} \text{ faults}} \times 100\%$$
$$= \frac{800}{1234} \approx 64.8\%$$

*uncollapsed F.C.*

$$= \frac{\text{detected } \textit{uncollapsed} \text{ faults}}{\text{total } \textit{uncollapsed} \text{ faults}} \times 100\%$$


*Collapsed F.C.*

$$= \frac{\text{detected } \textit{collapsed} \text{ faults}}{\text{total } \textit{collapsed} \text{ faults}} \times 100\%$$

# Why DFC not Used in Practice?

- Because DFC fault coverage is *pessimistic*. A test pattern can detect a dominating fault without detecting its dominated fault
- Example: ABC=100 does *NOT* detect dominated fault E/1, but it detects dominating fault F/1
  - since F/1 is removed, this is not counted in DFC coverage

Input			Output						
A	B	C	good	E/0	F/0	L/0	E/1	F/1	L/1
0	0	0	0	0	0	0	1	1	0
0	0	1	1	0	0	1	1	1	1
0	1	0	1	0	0	1	1	1	1
0	1	1	1	0	0	1	1	1	1
1	0	0	0	0	0	0	0	<u>1</u>	0
1	0	1	0	0	0	1	0	0	0
1	1	0	0	0	0	1	0	0	0
1	1	1	0	0	0	1	0	0	0

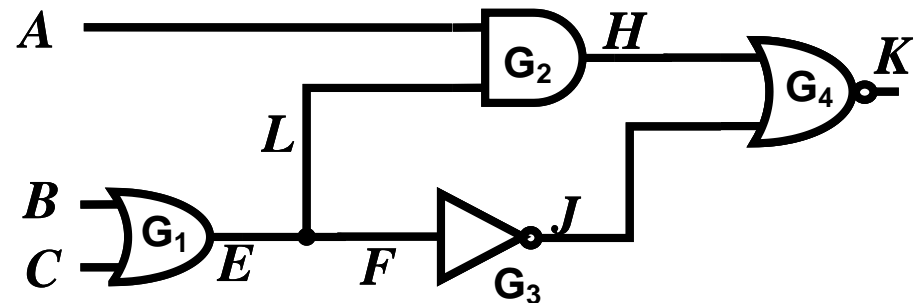


# Conclusions

- Fault collapsing reduces size of fault list
  - ◆ Speed up ATPG, Shorten test length
- DFC Rules:
  - ◆ (1) one fault on PI (2) one fault on output of all-PI gate
- DFC is more aggressive than EFC
  - ◆ but DFC not often used because its FC is pessimistic
- Checkpoint Theorem:
  - ◆ Detecting all checkpoint faults is good enough
  - ◆ Checkpoints are (1) PI, (2) fanout branches

# FFT

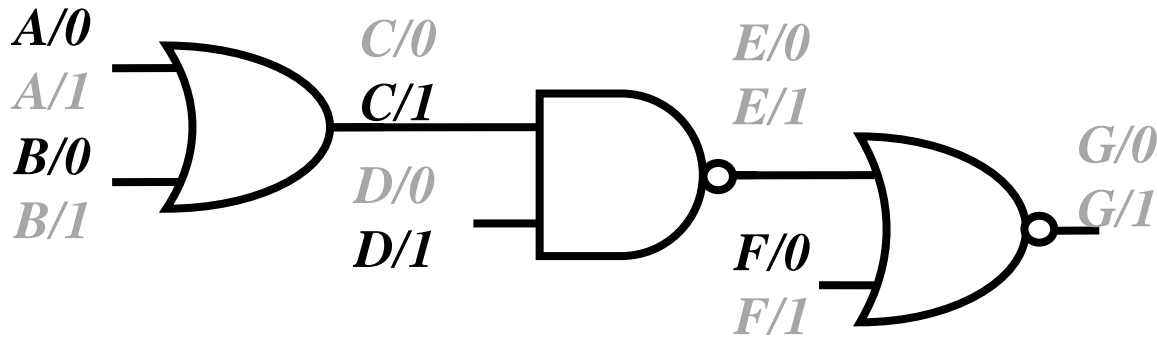- Q1: We only show DFC rule on AND gate fanout-free circuits.
  - ♦ Does it also applicable to other elementary gates? Please show why the other faults can be reduced



- Q2: Can we DFC on XOR gate? How about EFC?

# References

- **[Breuer 76] M. A. Breuer and A. D. Friedman, Diagnosis & Reliable Design of Digital Systems. Woodland Hills, CA: Computer Science Press, 1976.**