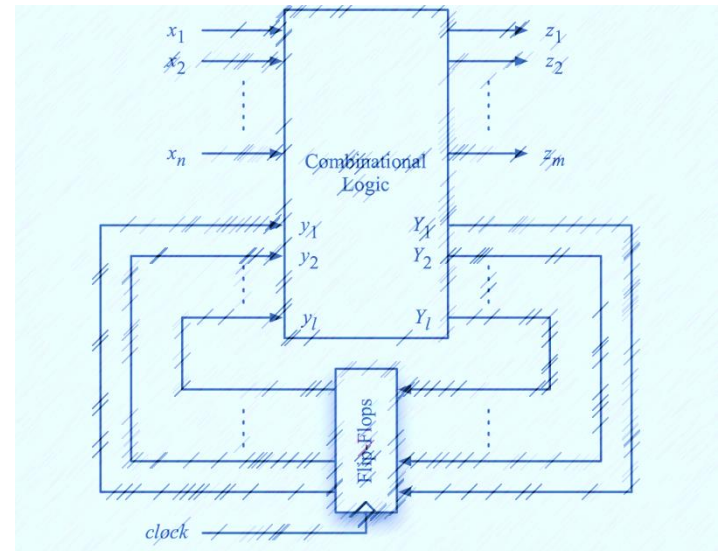



# Sequential ATPG

- Introduction
- Time-frame expansion methods
  - ◆ The Extended D-algorithm [Kubo 68]
  - ◆ 9-valued D algorithm [Muth 76]
  - ◆ Backward Time Frame Processing\* (not in exam)
    - EBT [Marlett 78]
    - BACK [Cheng 88]
  - ◆ Simulation-based methods\*
- Issues of Sequential ATPG\*
- Conclusions



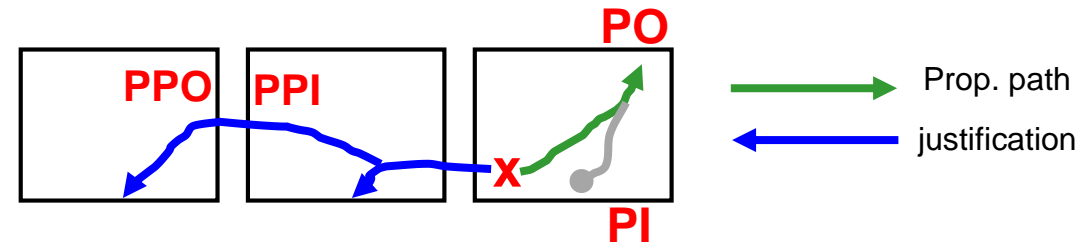
# Problems of Ext. D-Algorithm


- **Mixed Forward and Backward Time Frame Processing**
  - ◆ Reuse existing D-algorithm
    - both **forward** fault propagation and **backward** justification
  - ◆ How many time frames ?
    - Memory requirement **hard to predict**



Justification fails,  
Backtrack!

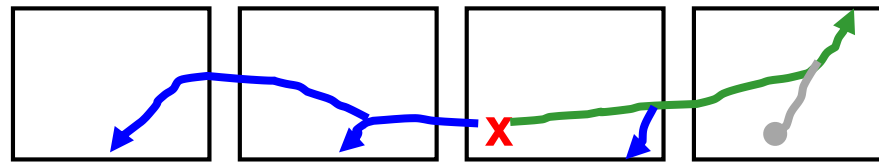


Justification fails,  
Backtrack!

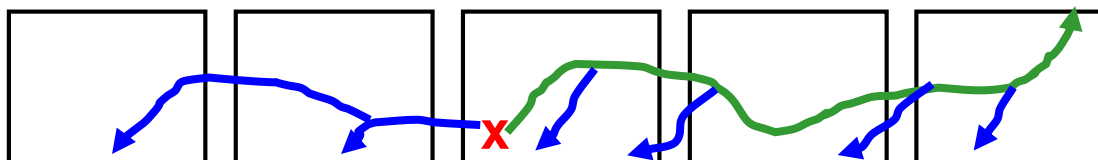

Test generated

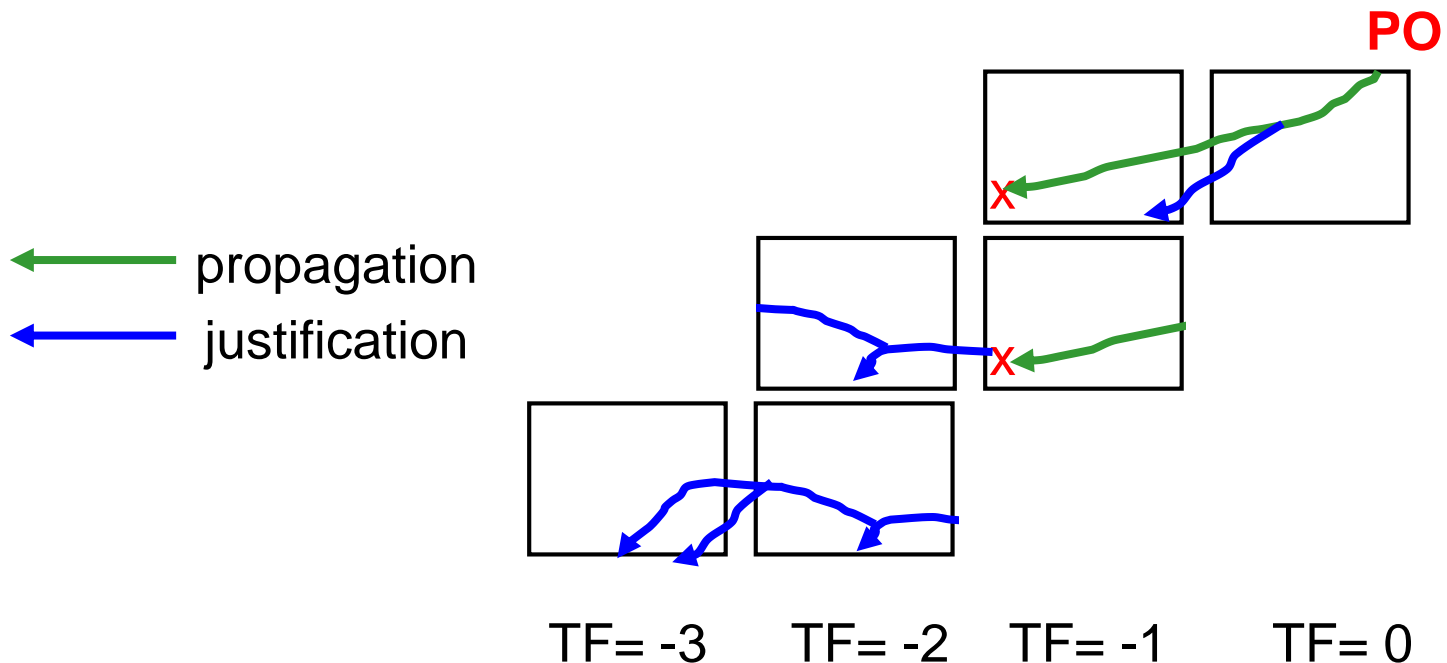
# Extended Backtrace (EBT) [Marlett 78]

- **Backward Time Frame Processing** Only
  - ◆ 1. Select a **path** from fault site to PO
  - ◆ 2. **Sensitize** path **backwards** from the PO
  - ◆ 3. **Justify** required values **backward**
    - If justification fails, choose another path
- Advantage: only two time frames needed




# EBT Example

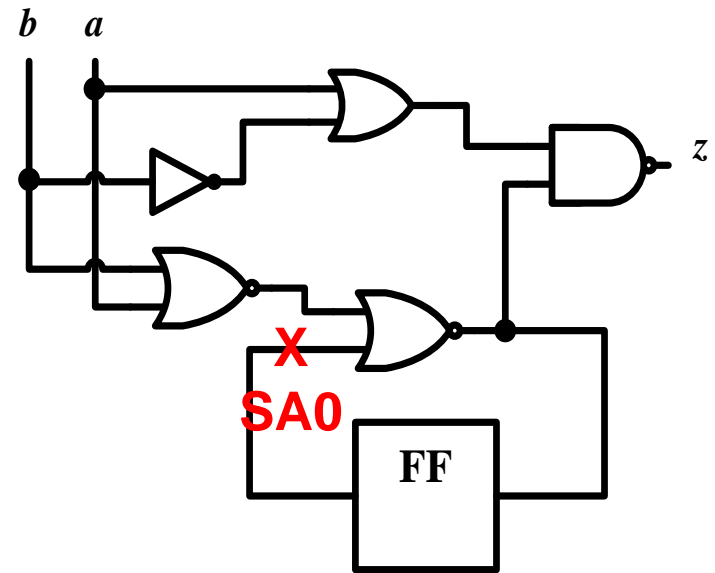
1. Create two time frames
2. Choose a path





past time frame

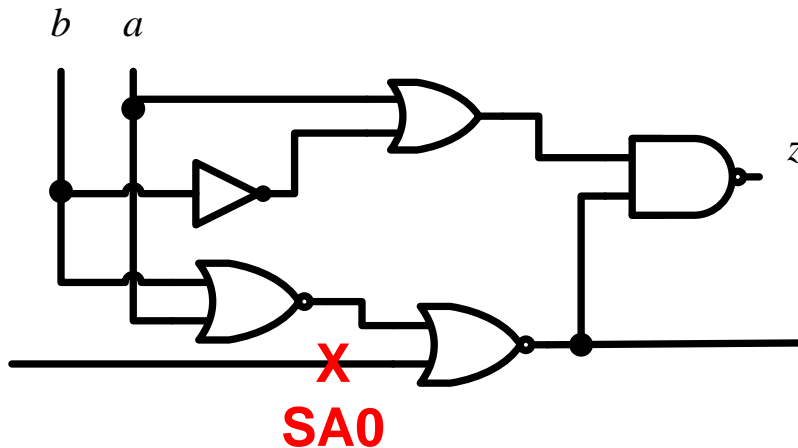

current time frame

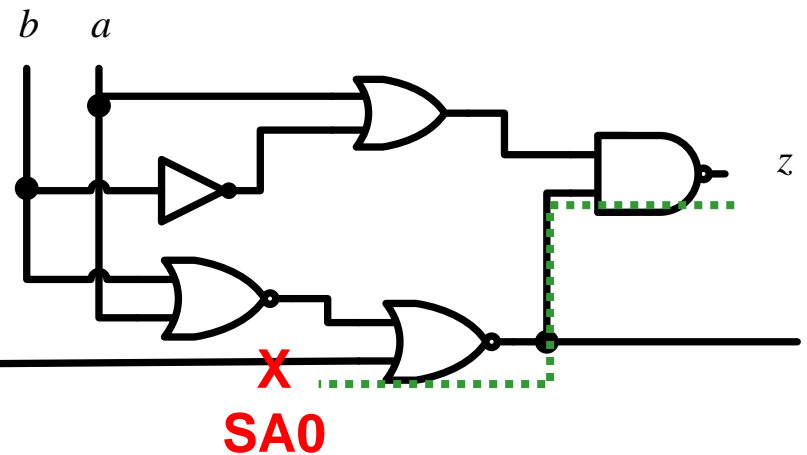


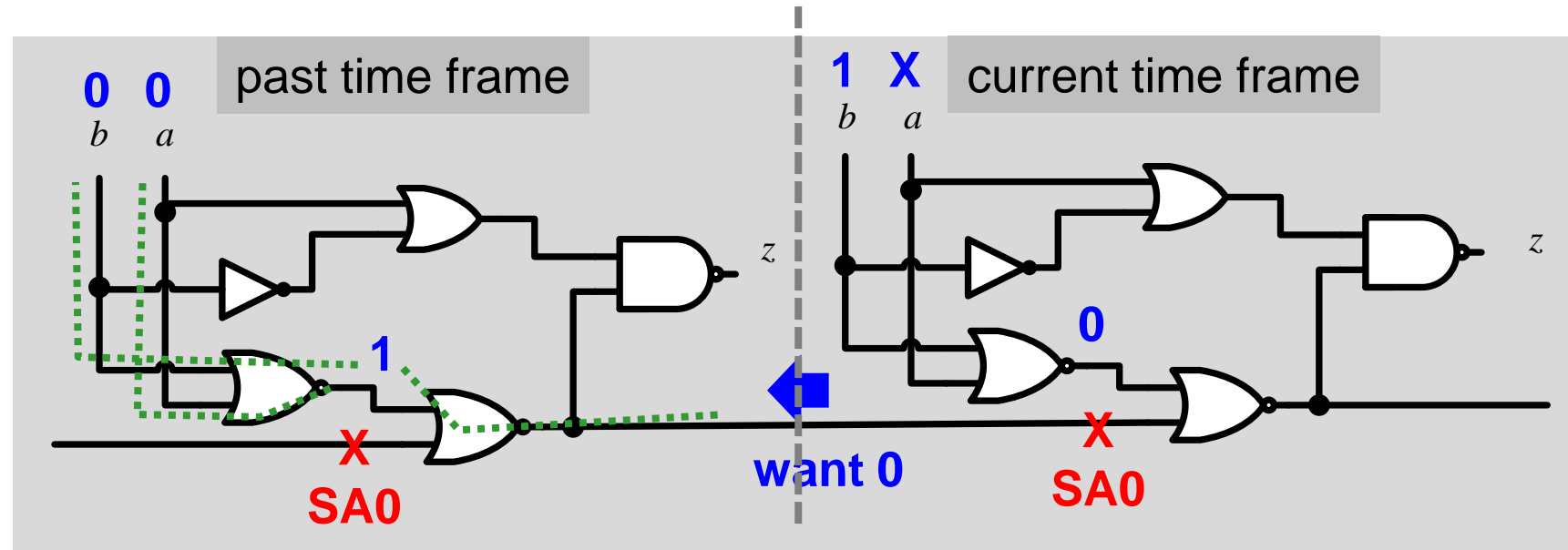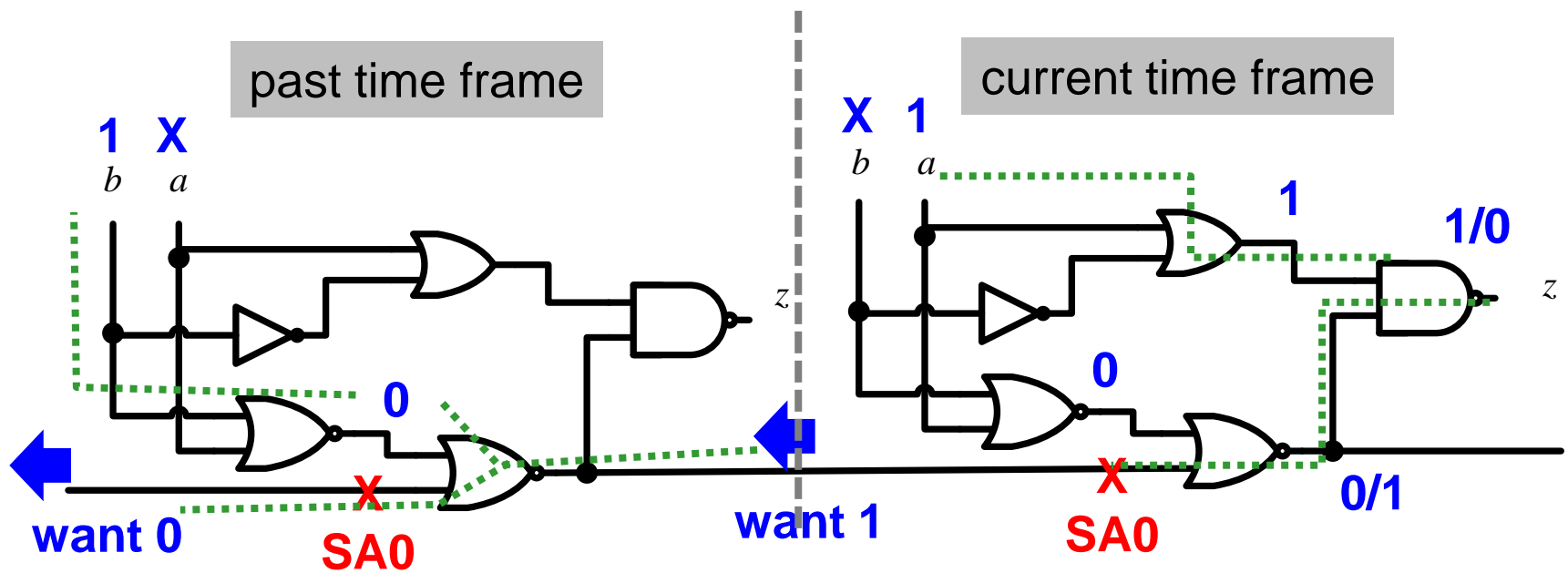

**ab = 00, 1x, x1**

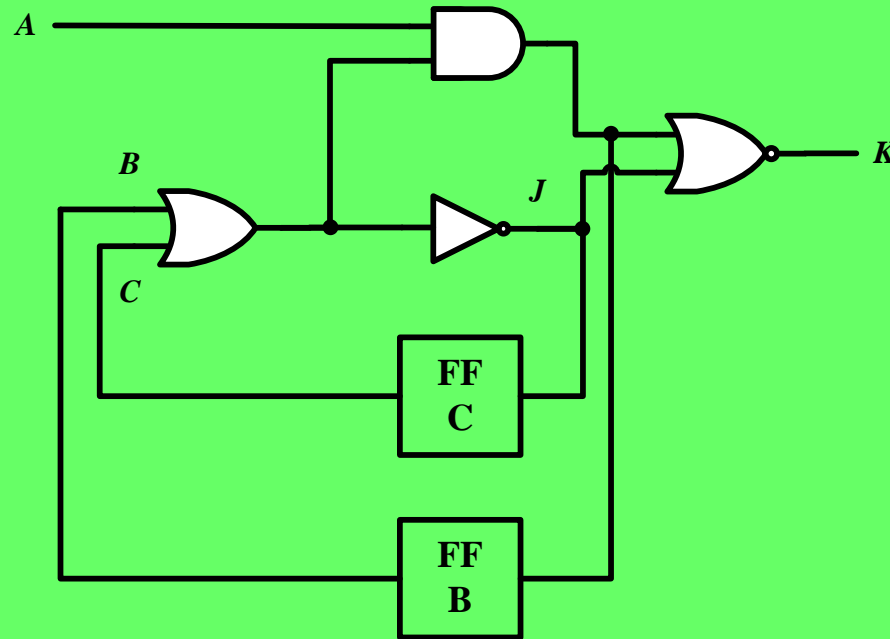
# Quiz

Q: Please redraw this into two time frames




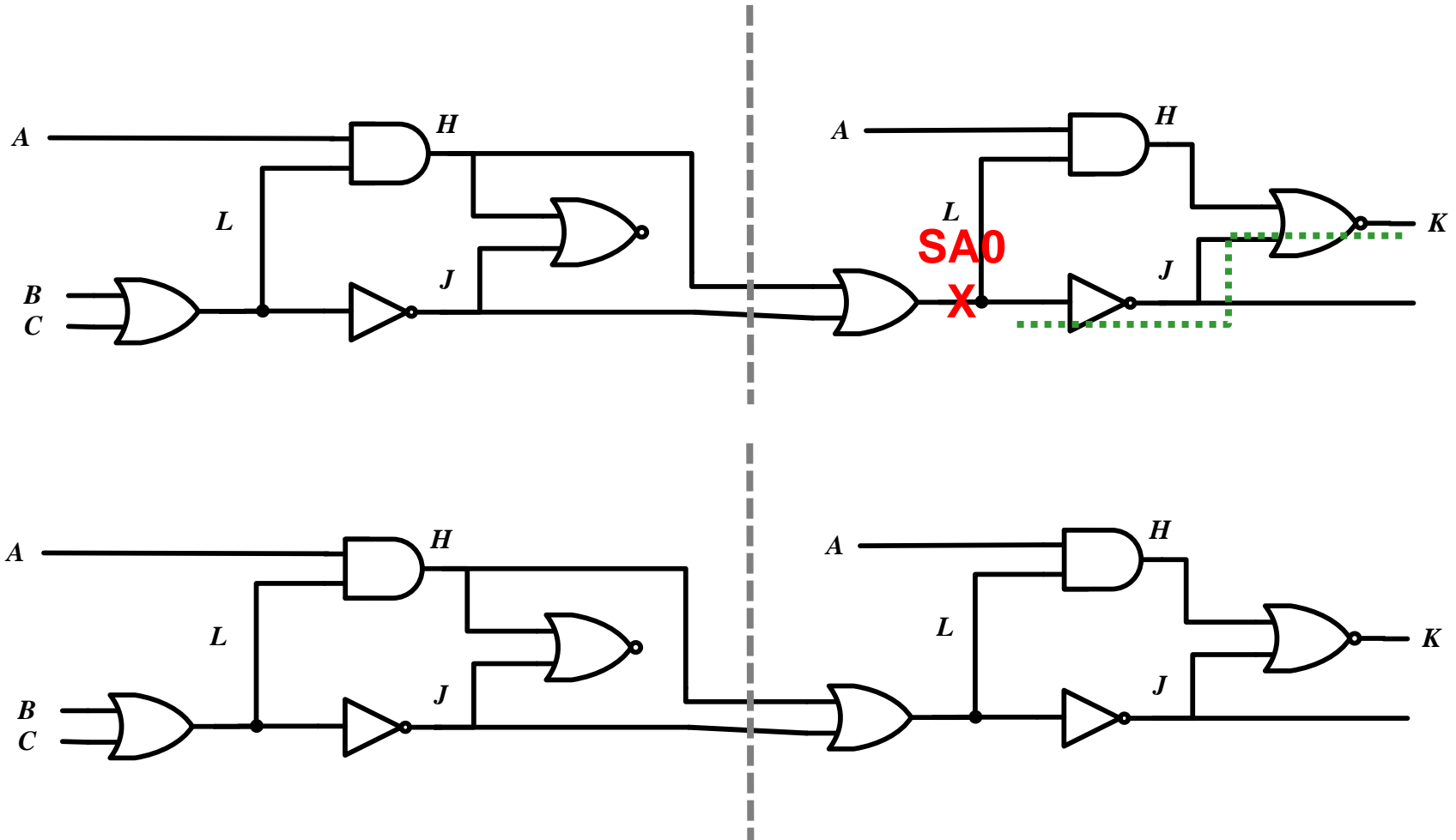
# Quiz (cont'd)

Q: Use EBT to generate test patterns for SA0 fault



# State Repetition

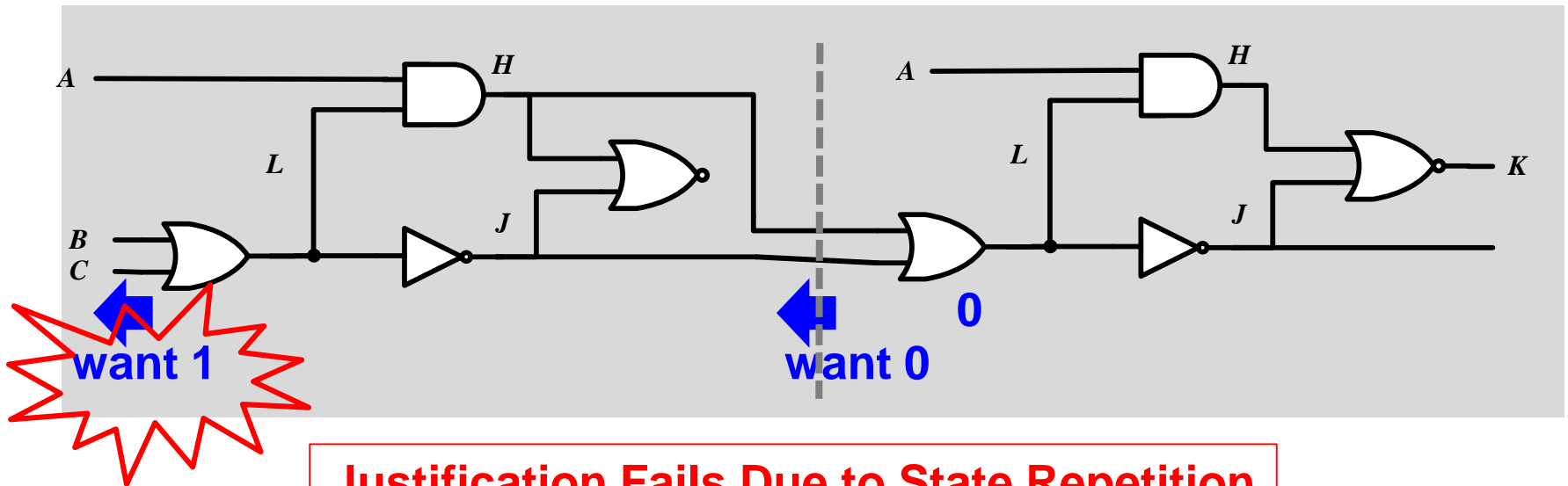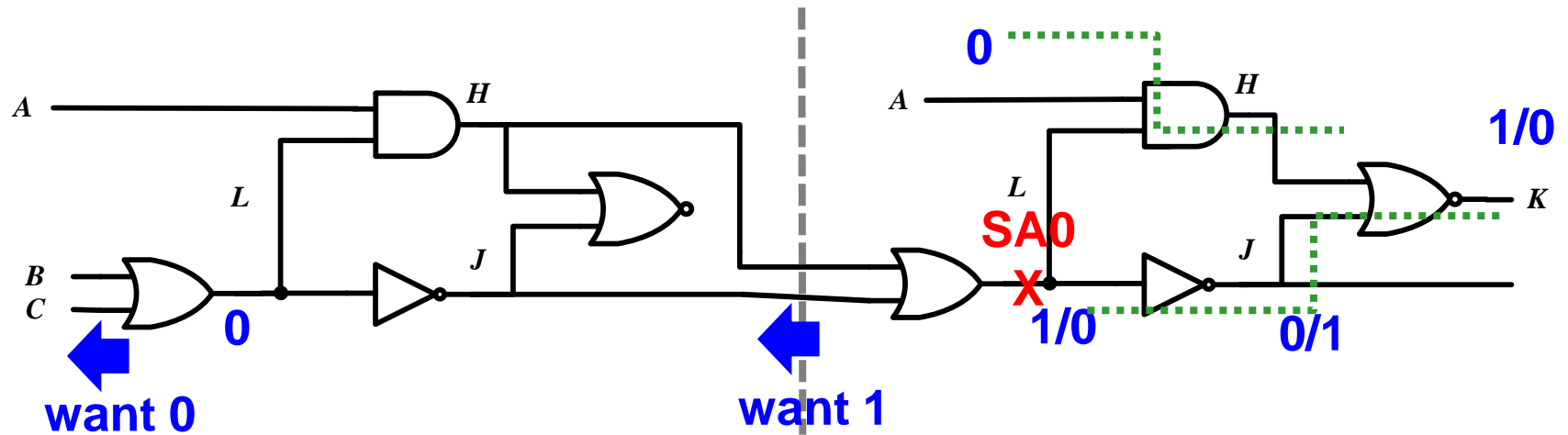

**Justification Fails Due to State Repetition**




# Comparison

	Advantages	Disadvantages	Example
Mixed F/B Time Frame	☺ Reuse existing D algorithm	☹ Too many time frames	Extended D
Backward TF Only	☺ Fixed time frames ☺ State repetition recognized	☹ Too many paths! How to choose path?	EBT

**Need Help to Make Smart Decision**
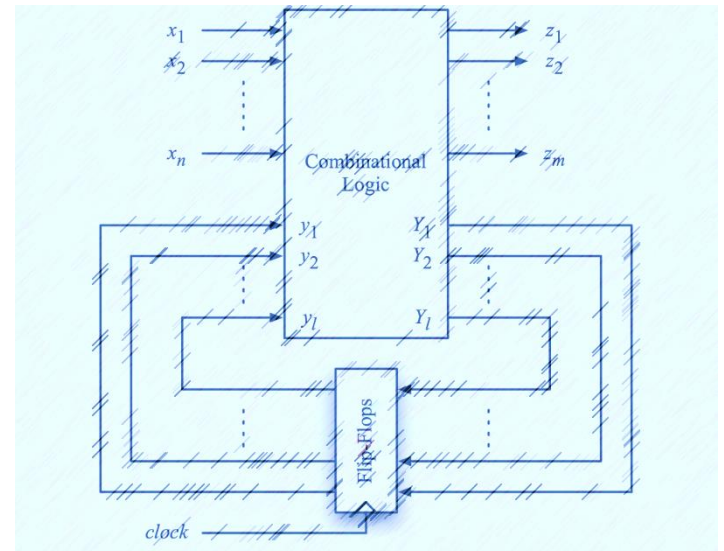
# Sequential ATPG

- Introduction
- Time-frame expansion methods
  - ◆ The Extended D-algorithm [Kubo 68]
  - ◆ 9-valued D algorithm [Muth 76]
  - ◆ Backward Time Frame Processing\* (not in exam)
    - EBT [Marlett 78]
    - BACK [Cheng 88]
  - ◆ Simulation-based methods\*
- Issues of Sequential ATPG\*
- Conclusions



# BACK Algorithm [Cheng 88]




- BACK selects a *PO* for fault detection,
  - ◆ Do not explicitly select a *path*
- PO selection based on a testability measures
  - ◆ *Drivability*
- Sensitized path will be created implicitly when drivability calculation

**BACK Chooses PO Instead of Path**

# Review: SCOAP (CH 6)




- $CC^0(N)$ ,  $CC^1(N)$

- ◆ Minimum number of combinational PI assignments and logic levels required to control a 0 or a 1 on node  $N$
- ◆ Estimates **effort** to control signal to zero or one
  - **Smaller** number, **easier** to control

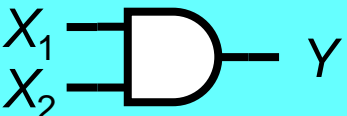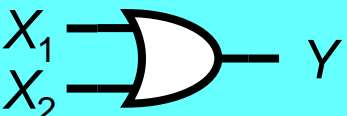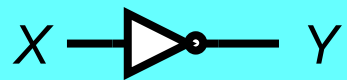	$CC^0(Y)$	$CC^1(Y)$
	$\min[CC^0(X_1), CC^0(X_2)] + 1$	$CC^1(X_1) + CC^1(X_2) + 1$
	$CC^0(X_1) + CC^0(X_2) + 1$	$\min[CC^1(X_1), CC^1(X_2)] + 1$
	$CC^1(X) + 1$	$CC^0(X) + 1$
Primary inputs	1	1


# Drivability: $d^{0/1}$ , $d^{1/0}$

- Estimates **effort** to propagate a **D or D'** from fault site to Y
  - $d^{0/1}(Y) = \text{drivability of } D'$  to node Y
  - $d^{1/0}(Y) = \text{drivability of } D$  to node Y

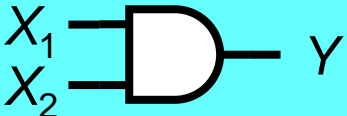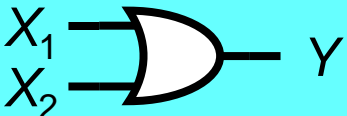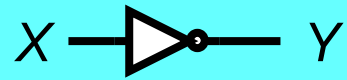	$d^{0/1}(Y)$	$d^{1/0}(Y)$
	$\min \{CC^1(X_1) + d^{0/1}(X_2),$ $d^{0/1}(X_1) + CC^1(X_2),$ $d^{0/1}(X_1) + d^{0/1}(X_2)\} + 1$	$\min \{CC^1(X_1) + d^{1/0}(X_2),$ $d^{1/0}(X_1) + CC^1(X_2),$ $d^{1/0}(X_1) + d^{1/0}(X_2)\} + 1$
	$\min \{CC^0(X_1) + d^{0/1}(X_2),$ $d^{0/1}(X_1) + CC^0(X_2),$ $d^{0/1}(X_1) + d^{0/1}(X_2)\} + 1$	$\min \{CC^0(X_1) + d^{1/0}(X_2),$ $d^{1/0}(X_1) + CC^0(X_2),$ $d^{1/0}(X_1) + d^{1/0}(X_2)\} + 1$
	$d^{1/0}(X) + 1$	$d^{0/1}(X) + 1$
Y = FF out X = FF in	$d^{0/1}(X) + K \text{ (constant)}$	$d^{1/0}(X) + K \text{ (constant)}$


# Example 1/2: SCOAP (BA Fig. 8.7)

- Fault-free circuit

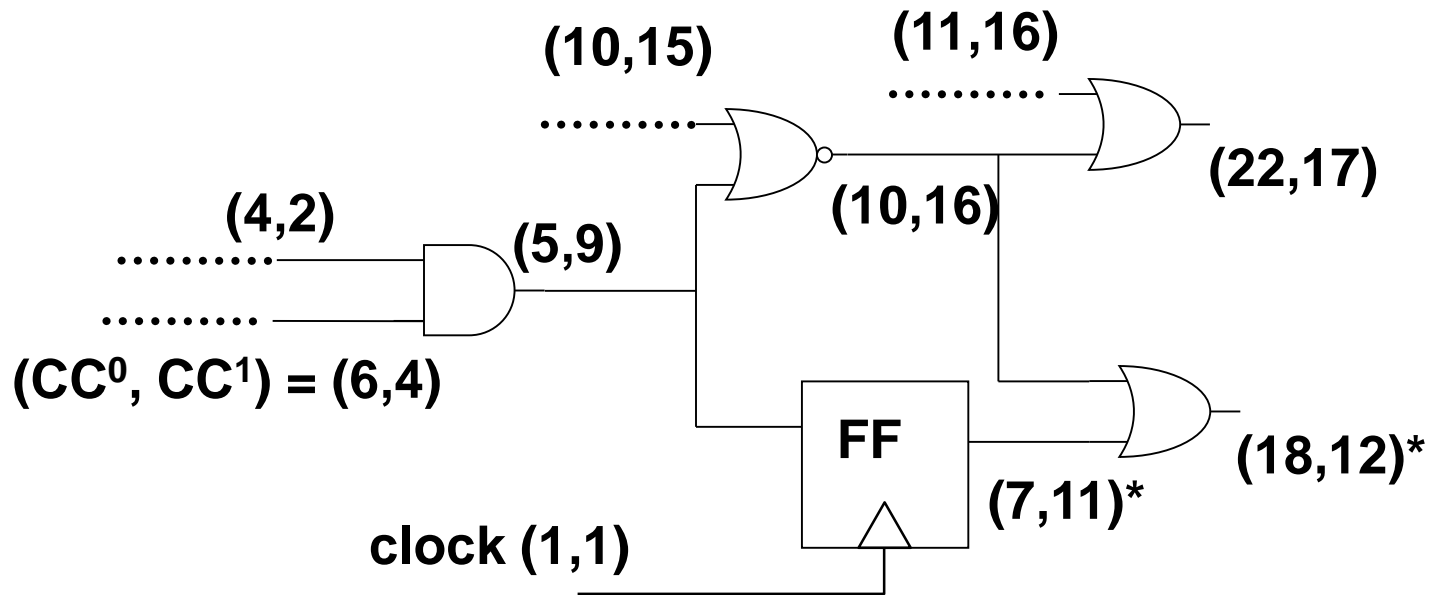

\* different from textbook

# Example 2/2: Drivability (BA Fig. 8.7)

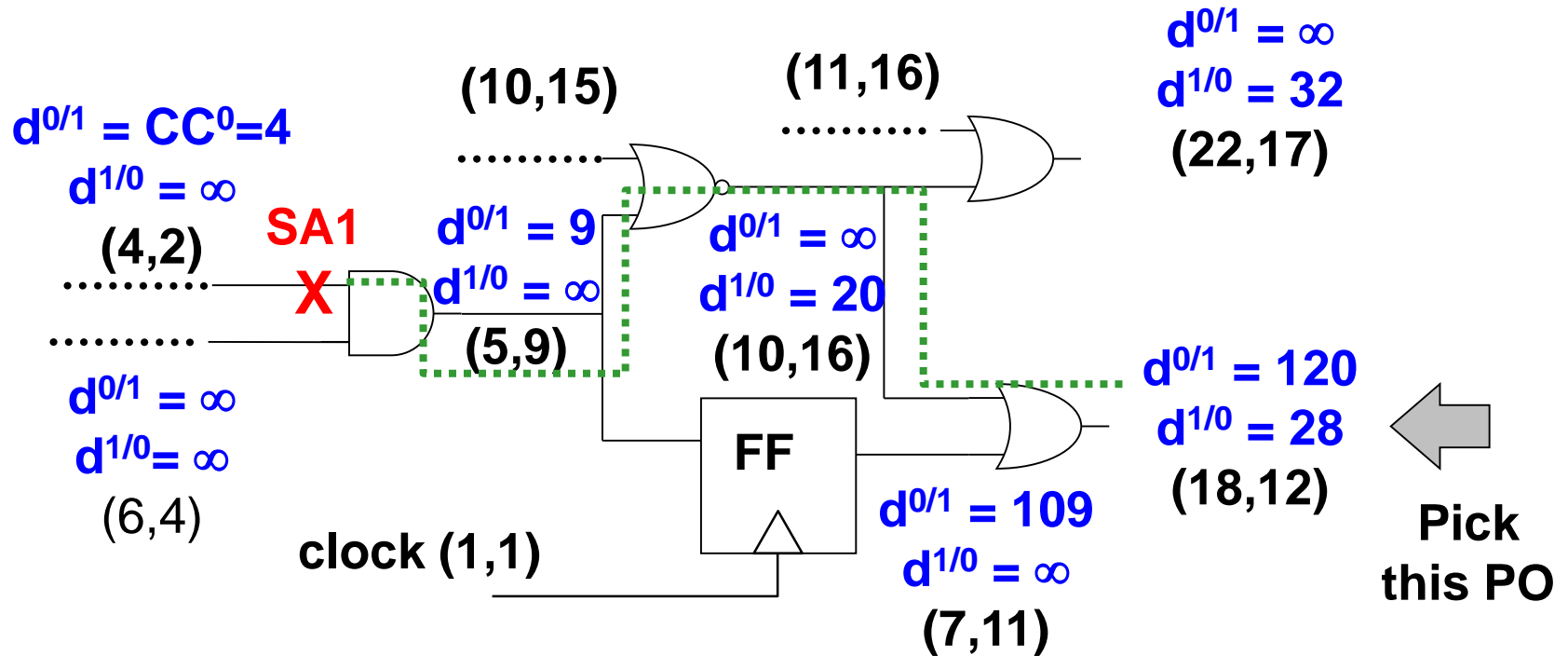


K=100

When D impossible,  $d^{1/0} = \infty$
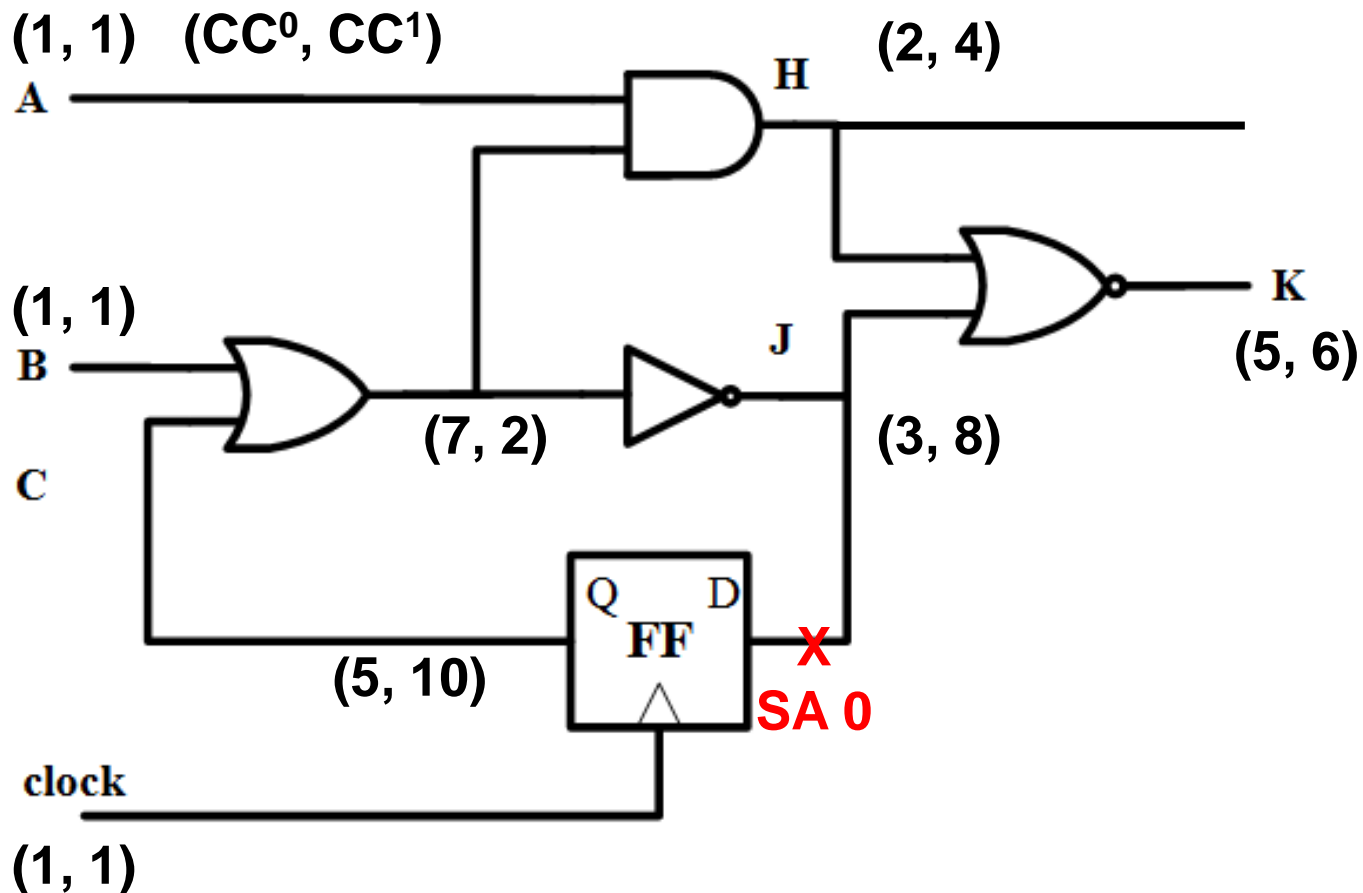
# Quiz


**Q: Based on SCOAP, please calculate drivability of SA0 fault.  
(Assume  $K=100$ )**




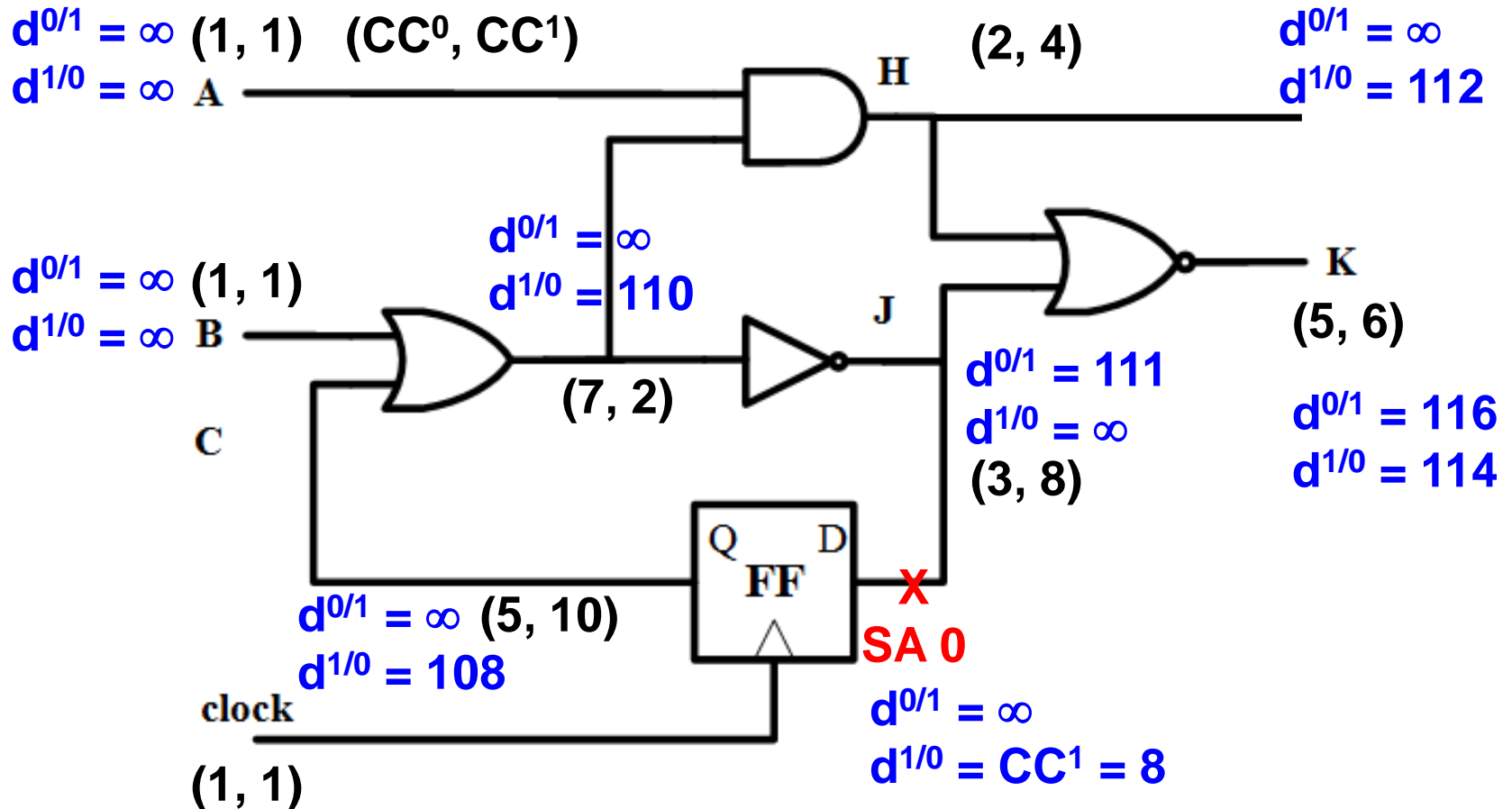
# Quiz

**Q: Based on SCOAP, please calculate drivability of SA0 fault.  
(Assume K=100)**




# Summary

- **Backward time frame processing** has advantages:
  - ◆ Fixed time frame
  - ◆ State repetition recognized
- EBT selects **one path** at a time
- BACK proposes **drivability** to select best PO

	Advantages	Disadvantages	Example
Mixed F/B Time Frame	😊 Reuse existing alg.	😞 Too many time frames	Extended D
Backward TF Only	😊 Fixed time frames 😊 State repetition recognized	😞 Too many paths!	EBT BACK
Forward TF Only	😊 No need to justify	😞 Hard to decide time frames	FASTEST (PODEM-like)
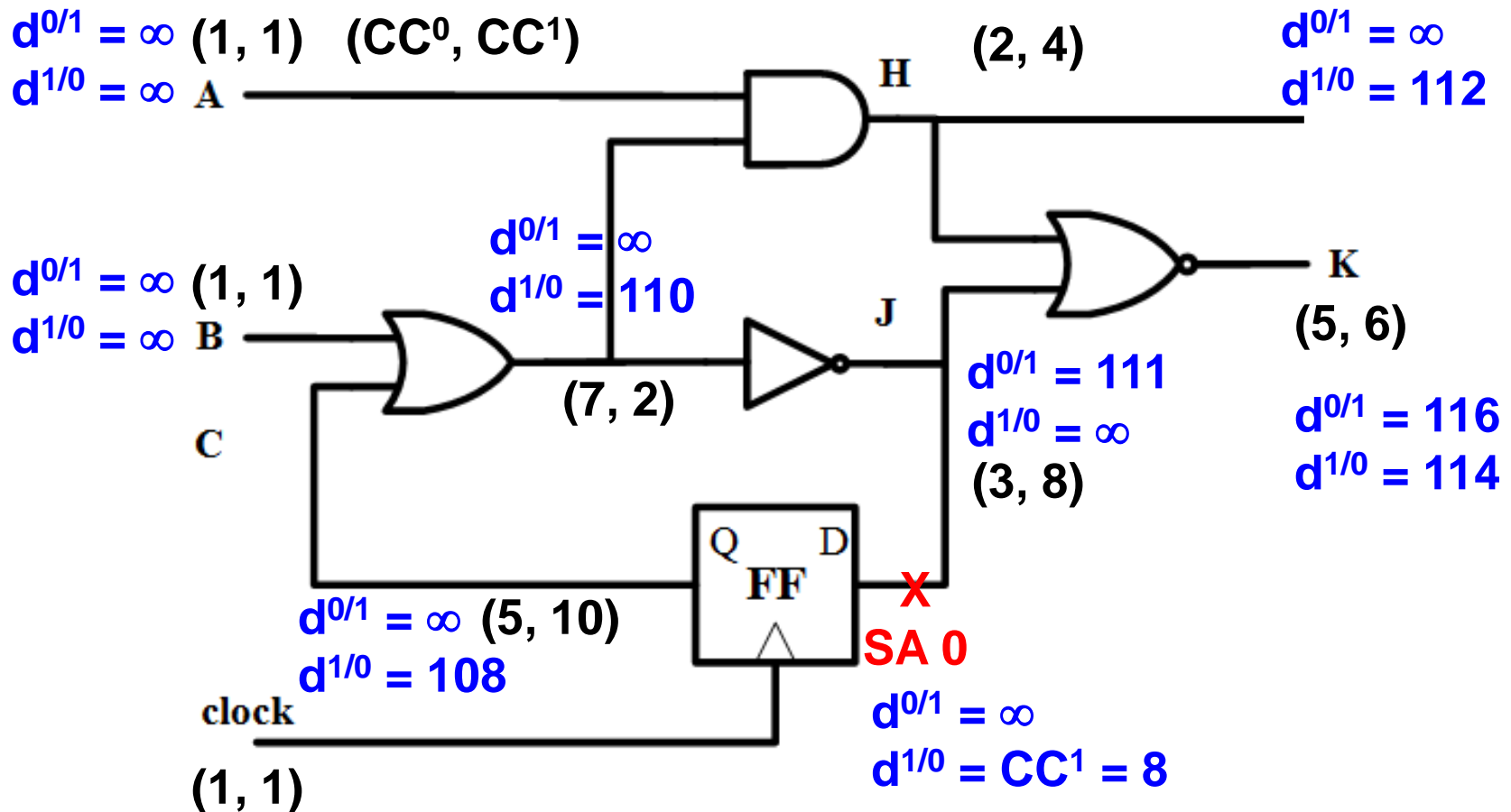
# FFT1

- Do we need feedback to iteratively calculate Drivability?




# FFT2

- Q: For forward time frame processing, can we fix time frames, like EBT?

	Advantages	Disadvantages	Example
Mixed F/B Time Frame	😊 Reuse existing alg.	😞 Too many time frames	Extended D
Backward TF Only	😊 Fixed time frames 😊 State repetition recognized	😞 Too many paths!	EBT BACK
Forward TF Only	😊 No need to justify	😞 Hard to decide time frames	PODEM-like

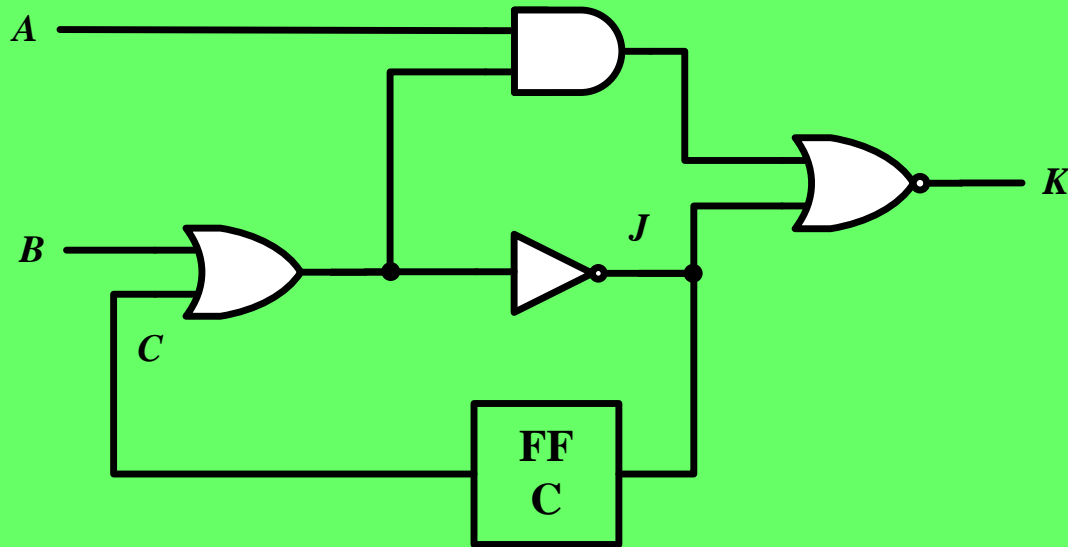
# Quiz

Q: Please redraw this into two time frames


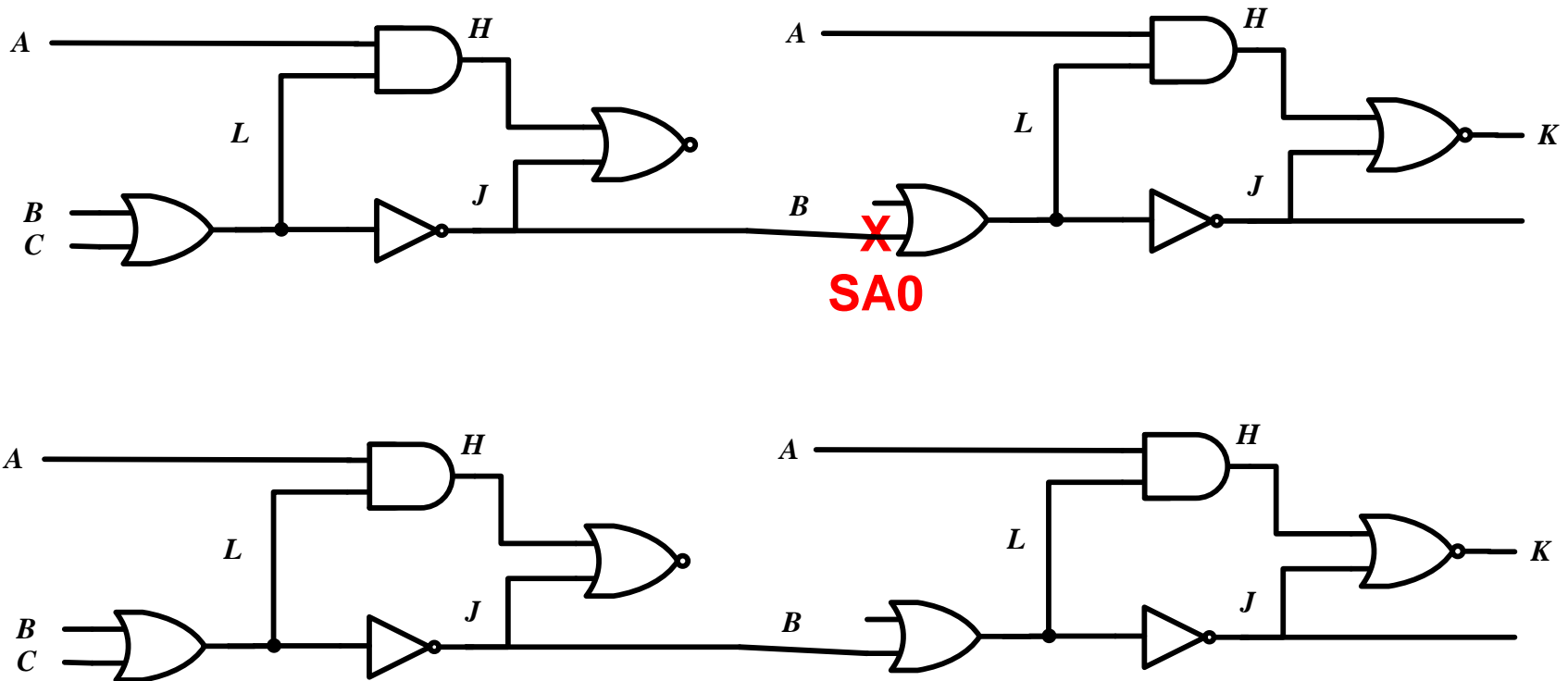
# Quiz (cont'd)

Q: Use EBT to generate test patterns for SA0 fault



# Drivability

- *Drivability* estimates effort of propagating a **D or D'** from fault site to that signal
  - ◆ Similar to **SCOAP**
- Review of SCOAP

	$CC^0(Y)$	$CC^1(Y)$
$Y = X_1 \text{ AND } X_2$	$\min[CC^0(X_1), CC^0(X_2)] + 1$	$CC^1(X_1) + CC^1(X_2) + 1$
$Y = X_1 \text{ OR } X_2$	$CC^0(X_1) + CC^0(X_2) + 1$	$\min[CC^1(X_1), CC^1(X_2)] + 1$
$Y = X'$	$CC^1(X) + 1$	$CC^0(X) + 1$
Primary inputs	1	1

**Drivability is like SCOAP for a Specific Fault**


# Drivability: $d(0/1)$ & $d(1/0)$

- $d^{0/1}(Y) = \text{drivability of } D'$ 
  - ◆ Effort to bring node Y to  $D'$  when the fault presents
- $d^{1/0}(Y) = \text{drivability of } D$

	$d^{0/1}(Y)$	$d^{1/0}(Y)$
$Y = X_1 \text{ AND } X_2$	$\min \{CC^1(X_1) + d^{0/1}(X_2),$ $d^{0/1}(X_1) + CC^1(X_2),$ $d^{0/1}(X_1) + d^{0/1}(X_2)\} + 1$	$\min \{CC^1(X_1) + d^{1/0}(X_2),$ $d^{1/0}(X_1) + CC^1(X_2),$ $d^{1/0}(X_1) + d^{1/0}(X_2)\} + 1$
$Y = X_1 \text{ OR } X_2$	$\min \{CC^0(X_1) + d^{0/1}(X_2),$ $d^{0/1}(X_1) + CC^0(X_2),$ $d^{0/1}(X_1) + d^{0/1}(X_2)\} + 1$	$\min \{CC^0(X_1) + d^{1/0}(X_2),$ $d^{1/0}(X_1) + CC^0(X_2),$ $d^{1/0}(X_1) + d^{1/0}(X_2)\} + 1$
$Y = X'$	$d^{1/0}(X) + 1$	$d^{0/1}(X) + 1$
$Y = \text{FF out}$ $X = \text{FF in}$	$d^{0/1}(X) + K \text{ (constant)}$	$d^{1/0}(X) + K \text{ (constant)}$




# Drivability Example 1/2 (BA Fig. 8.7)

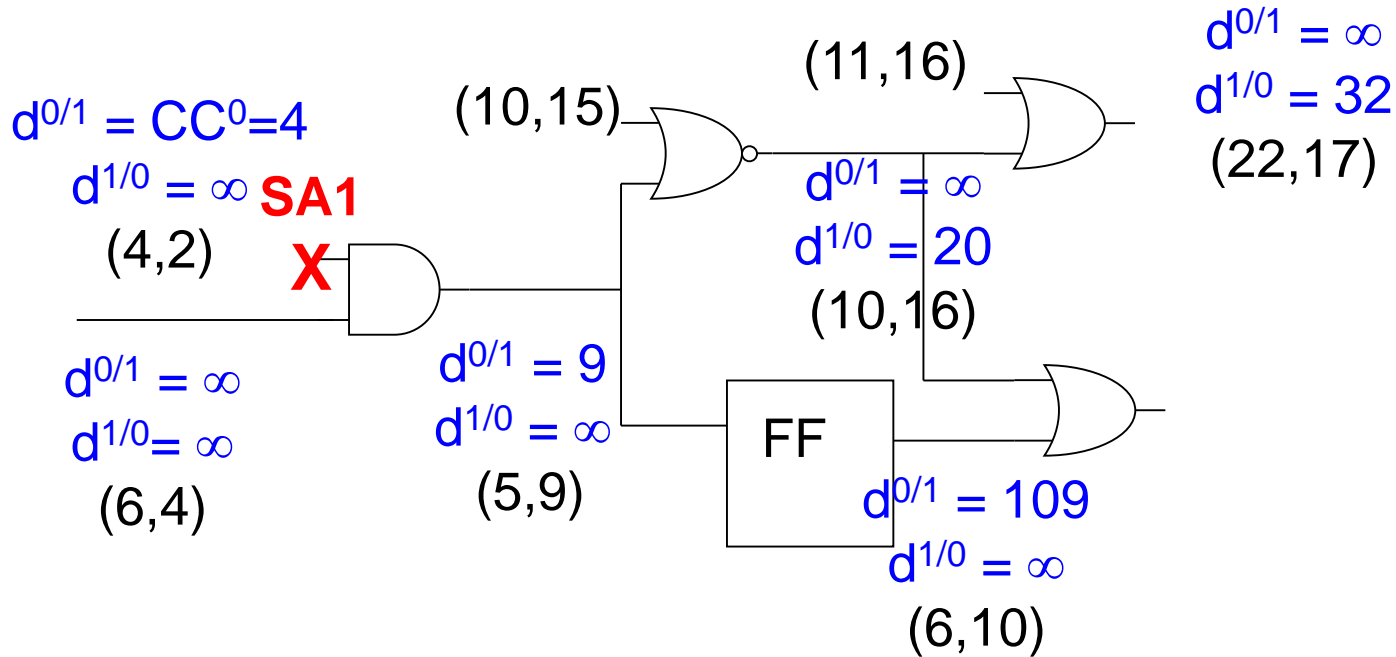

- **K=100**
- **When D impossible,  $d^{1/0} = \infty$**

# Drivability Example 2/2 (BA Fig. 8.7)

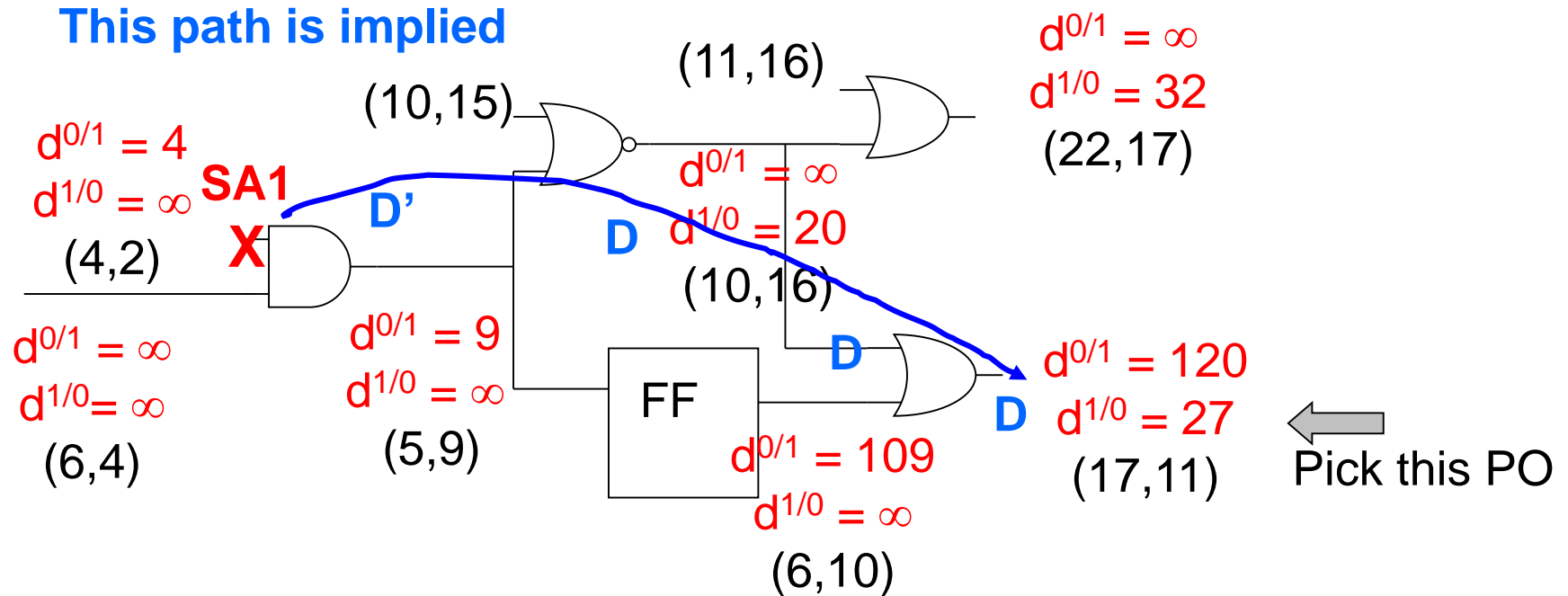

- To justify a D or D' at gate output, select gate input with smallest drivability as D or D' input