



# VLSI Testing

## 積體電路測試

### *Delay Test*


**Professor James Chien-Mo Li 李建模**

**Lab. of Dependable Systems**

**Graduate Institute of Electronics Engineering**


**National Taiwan University**

# Course Roadmap (EDA Topics)

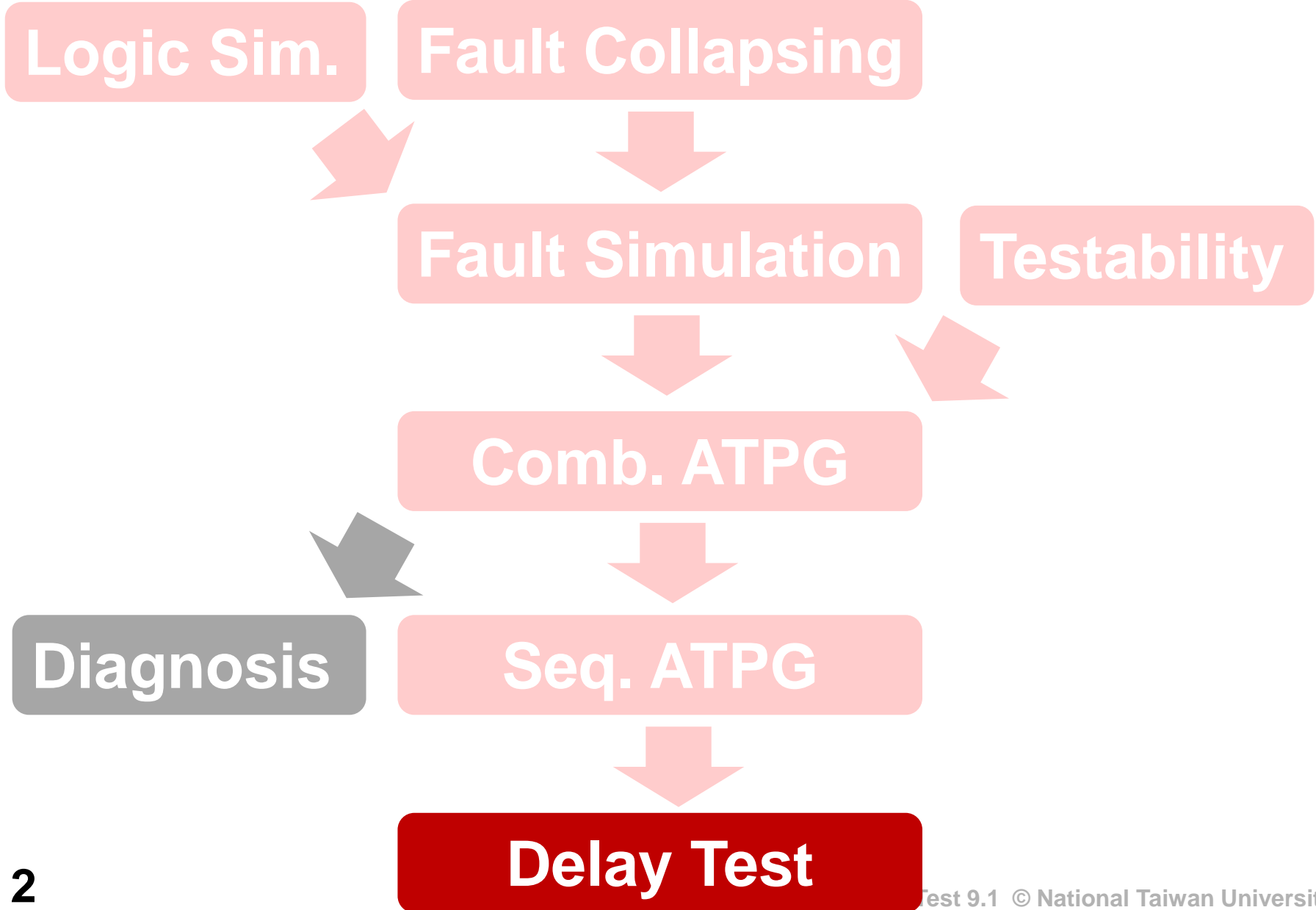
 
# Motivating Problem

- You already know stuck-at test very well.... but not enough
- Manger asks you to generate a test pattern to validate IC speed
  - ♦ make sure path BEGJK **timing** is correct



# Why Am I Learning This?

- In this chapter, we learn :
  - ◆ Delay fault models
  - ◆ Generate test patterns for delay faults
  - ◆ Delay fault simulation

*“Delay always breeds danger  
and to protect a great design  
is often to ruin it.”*


*(Miguel de Cervantes)*

# Test Generation

| <b>Fault Models</b>                    | <b>Combinational<br/>Circuits<br/>(or Sequential<br/>ckt. with scan)</b> | <b>Sequential<br/>Circuits</b>               |
|--|--|--|
| <b>No fault model</b>                  | <b>PET</b>   | <b>Checking experiment</b>                   |
| <b>Single Stuck-at<br/>Fault Model</b> | <b>D<br/>PODEM<br/>FAN</b>   | <b>Extended D<br/>9-valued</b>               |
| <b>Delay Fault Model</b>               | <b>Path Delay<br/>Transition Delay</b>                                   | <b>Launch on Capture<br/>Launch on Shift</b> |
 
# Delay Test

- Introduction
  - ◆ What and why
  - ◆ Delay fault models: PDF, TDF
  - ◆ Comparison
- Path Delay Fault [Smith 85]
- Transition Delay Fault [Barzilai 83][Levendel 86]
- Experimental Results\* (not in exam)
- Issues of Delay Tests\* (not in exam)
- Conclusions




# What is Delay Test ?

- **Delay tests** (aka. **delay fault testing**) [Breuer 74]
  - ♦ Apply test patterns to detect **delay faults**
- Functional verification test patterns can be applied at system speed
  - ♦ However, not enough to detect delay faults
- Delay test is also called **AC test**
  - ♦ As opposed to **DC test** for stuck-at faults

**Delay Test Detects Delay Faults**
 
# Why Delay Test?

- Some defects change circuit **timing** but not function
  - ♦ **Random defects**: Resistive opens, resistive bridging,
  - ♦ **Systematic defects**: crosstalk, process variation in  $V_t$




- IC becomes faster, **small delay defects (SDD)** become significant
  - ♦ 100 ps SDD
    - \* only 1% for 100MHz clock period, insignificant
    - \* but 10% for 1GHz clock period, **very significant**

**Delay Tests Important for Advanced IC**



 
# How Delay Test?

- Delay faults needs *two-pattern test*
  - ♦ As opposed to *one-pattern* test for stuck-at faults
- A two-pattern test consists of **a pair of test patterns (test vectors)**
  - ♦  $V_1$ : initialize circuit state
  - ♦  $V_2$ : *launch* transition, *propagate fault effect* to output
- Control timing ( $T$ ) between  $V_1$  and  $V_2$  carefully
  - ♦ If  $T$  is as fast as system operation, this is called *at-speed testing*



 
# Delay Test

- Introduction
  - ◆ What and why
  - ◆ Delay fault models: PDF, TDF
  - ◆ Comparison
- Path Delay Fault [Smith 85]
- Transition Delay Fault [Barzilai 83][Levendel 86]
- Experimental Results\* (not in exam)
- Issues of Delay Tests\* (not in exam)
- Conclusions


 
# Two Delay Fault Models



- **Path Delay Fault, PDF** [Smith 85]
  - ◆ Path delay of the faulty path > clock period
- **Transition (Delay) Fault, TDF** [Barzilai 83] [Levendel 86]
  - ◆ Path delay of all paths through the fault > clock period
- Other delay fault models
  - ◆ Gate delay fault [Iyengar 88]
  - ◆ Segment delay fault [Heragu 96]
  - ◆ ...


  
# Example


- Clock period = 10.0ns, good gate delay = 2.0ns
- For good circuit
  - ♦ **short path delay** = 6.0ns
  - ♦ **long path delay** = 8.0ns
- PDF (fault distributed along path)
  - ♦  $\underline{3.0} + \underline{2.6} + \underline{2.7} = 8.3 < 10 \rightarrow \text{pass}$
  - ♦  $\underline{3.0} + \underline{2.6} + \underline{2.7} + \underline{2.9} = 11.2 > 10 \rightarrow \text{fail}$
- TDF (lumped fault = 9.0 ns)
  - ♦  $2.0 + 2.0 + 2.0 + \underline{9.0} = 15.0 \rightarrow \text{fail}$
  - ♦  $2.0 + 2.0 + 2.0 + \underline{9.0} + 2.0 = 17.0 \rightarrow \text{fail}$

*fault size* = extra delay caused by fault



 
# Number of Delay Faults

- PDF: Two path delay faults for each path
  - Rising (notation  $\uparrow$ ) Falling (notation  $\downarrow$ )
  - Example: two PDF
    - \* BEGJK $\uparrow, \downarrow$



 - NOTE: Number of paths is worst-case *exponential* to gate count
- TDF: Two faults for each node
  - Slow-to-rise (STR) fault; Slow-to-fall (STF) fault
  - Example: six TDF in AND
    - \* A STR, A STF, B STR, B STF, C STR, C STF
  - NOTE: Number of faults is *linear* to gate count




# Quiz

**Q1: How many PDF in this circuit?**

**A:**

**Q2: How many TDF in this circuit?**

**A:**

 

# Comparison: PDF vs. TDF

|                             | Path Delay Fault                      | Transition Delay Fault                |
|-----------------------------|---------------------------------------|---------------------------------------|
| Number of faults            | ☹ WC exponential<br>(need path list)  | ☺ linear                              |
| Fault size and distribution | ☺ small delay faults<br>☺ distributed | ☹ large delay faults only<br>☹ lumped |
| Silicon speed Validation    | ☺ useful                              | ☹ not useful                          |
| ATPG                        | ☹ less mature tool<br>☹ FC not high   | ☺ mature ATPG<br>☺ FC very high       |


General definition  
Difficult for ATPG



Specific definition  
Easier for ATPG
 
# Summary

- Introduction and delay fault models
  - ◆ PDF assumes distributed fault
    - \* Worst-case **exponential** in numbers, **difficult** for ATPG
  - ◆ TDF assume lumped fault
    - \* **linear** in numbers, **easiest** for ATPG
- Path Delay Fault
- Transition Delay Fault
- Delay Test Application
- Circuit Model for Delay Test ATPG
- Experimental Results\* (not in exam)
- Issues of Delay Tests\* (not in exam)
- Conclusions





# FFT

- Number of paths is worst-case exponential to number of gates
  - ♦ Q: why? Please give an example

