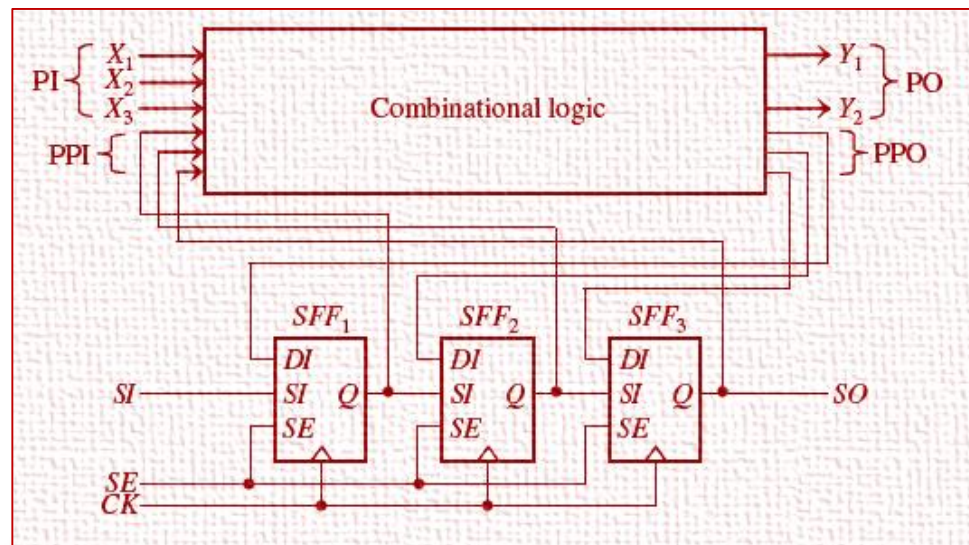



# DFT - Part 1

- Introduction
- Internal Scan
  - ◆ FF-based
    - \* MUXed-D scan (1973, Stanford)
      - MUXed-D scan flip-flop
      - Test Mode Operation
    - \* Clocked scan (1968, NEC)
    - \* Other scan
  - ◆ Latch-based
    - \* LSSD (1977, IBM)
- Scan Design Flow
- Issues and Solutions
- Conclusion



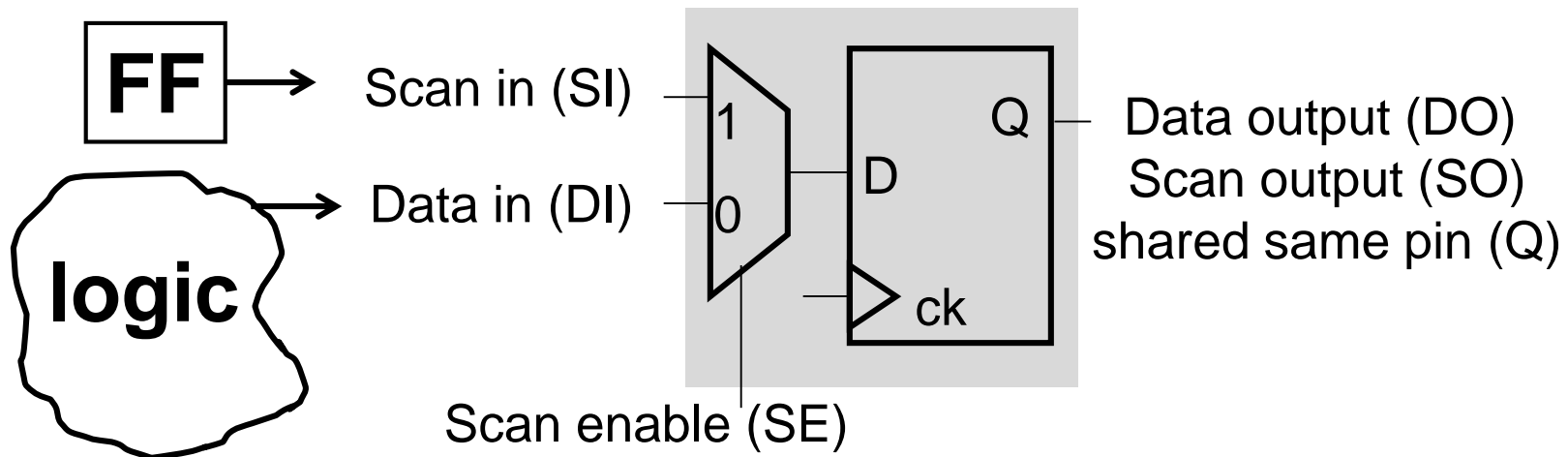
# MUXed-D Scan Flip-flop [Williams 73]

- Often used in flip-flop based, standard cell design
- 3 input, 1 output, 1 clock pin
- **Scan Enable** (SE) pin selects inputs
  - ♦ **Data in** (DI): from logic
  - ♦ **Scan in** (SI): from previous scan FF
- **Data output** (DO) and **Scan output** (SO) often share same pin (Q)
- One multiplier (MUX) slower and larger than regular non-scan FF



 
# MUXed-D Scan Flip-flop

- Positive edge triggered MUXed-D scan FF (WWW Fig. 2.9)
  - ♦ **SE=1**, SI → Q at positive clock edge
  - ♦ **SE=0**, DI → Q at positive clock edge




	operation
<b>SE=0</b>	<b>Capture (DI → Q)</b>
<b>SE=1</b>	<b>Shift (SI → SO)</b>

 


**SE = 1 enables scan**
 
# Muxed-D Scan Architecture

- Original circuit
  - ♦ Single clock
  - ♦ Positive edge triggered
  - ♦ Non-scan DFF



 - After scan insertion
  - ♦ Three extra pins
    - \* SI, SE, SO




SFF = scan FF

# Normal Mode Operation


- Always  $SE = 0$
- Same as original circuit

	operation
<b>SE=0</b>	<b>Capture (<math>DI \rightarrow Q</math>)</b>
SE=1	Shift ( $SI \rightarrow SO$ )

 

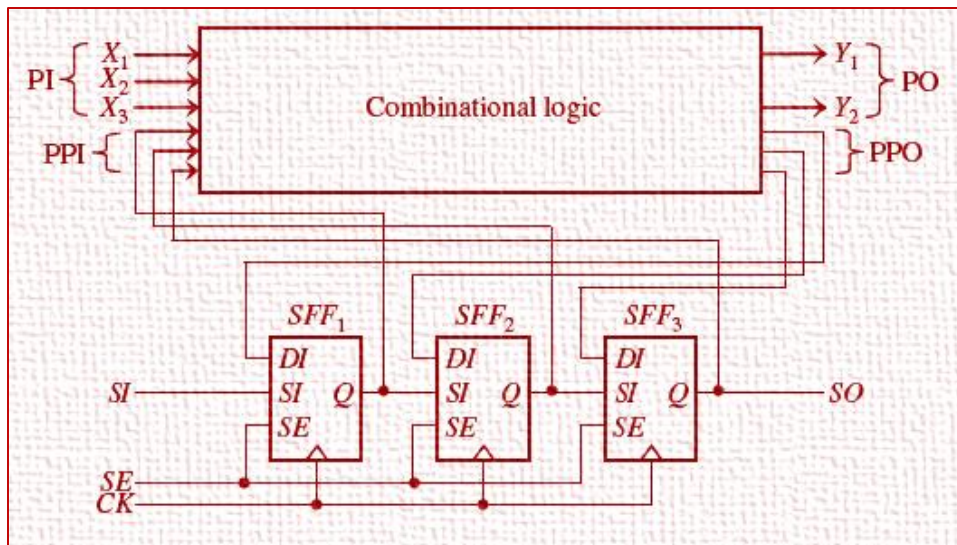
# Test Mode Operation


- Stuck-at fault testing
  - ◆ One pattern per scan
- Delay fault testing
  - ◆ Two-patterns per scan
    - \* Launch-on-Shift
    - \* Lunch-on-Capture



# SAF Operation

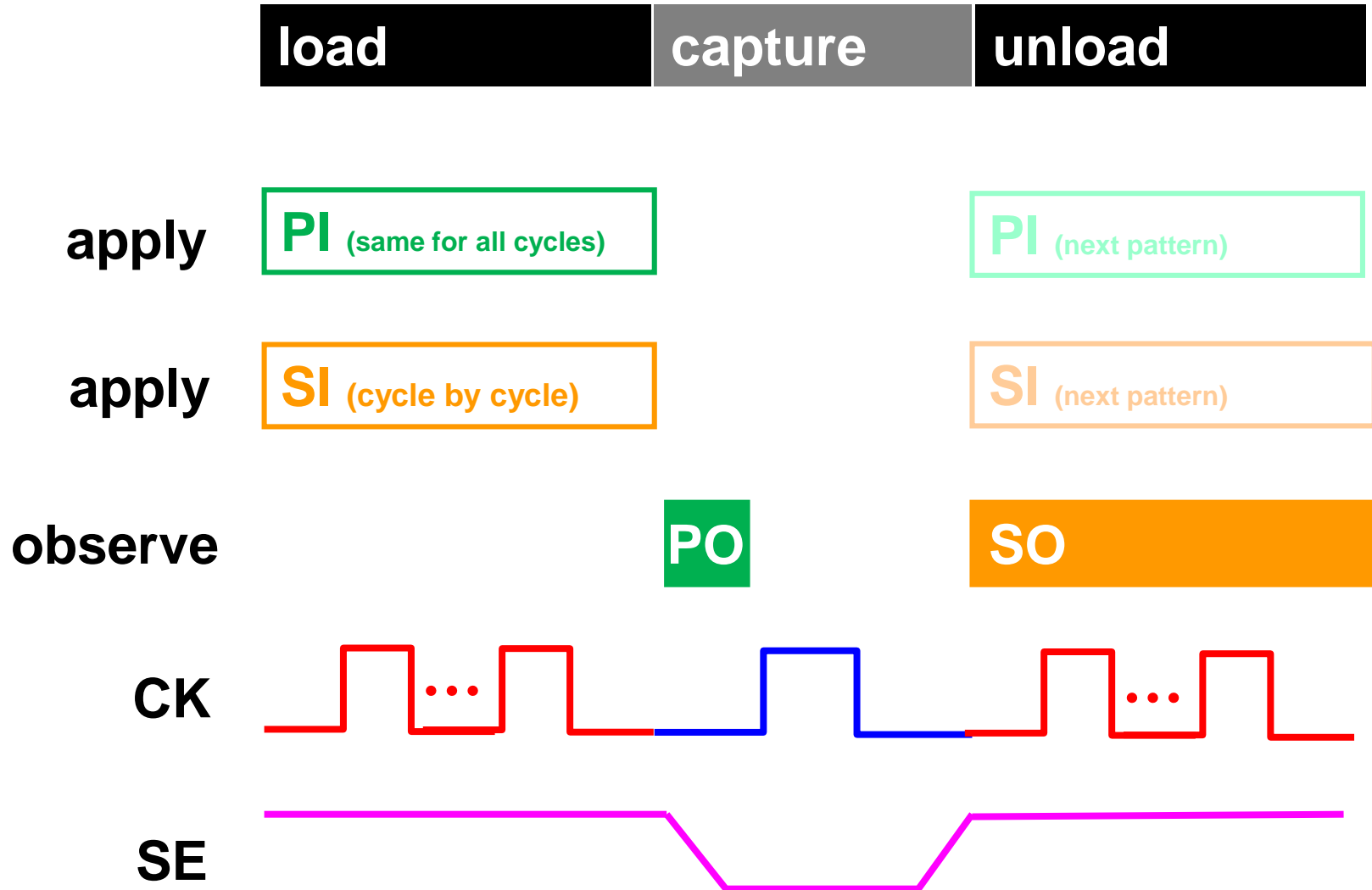

# SAF Example

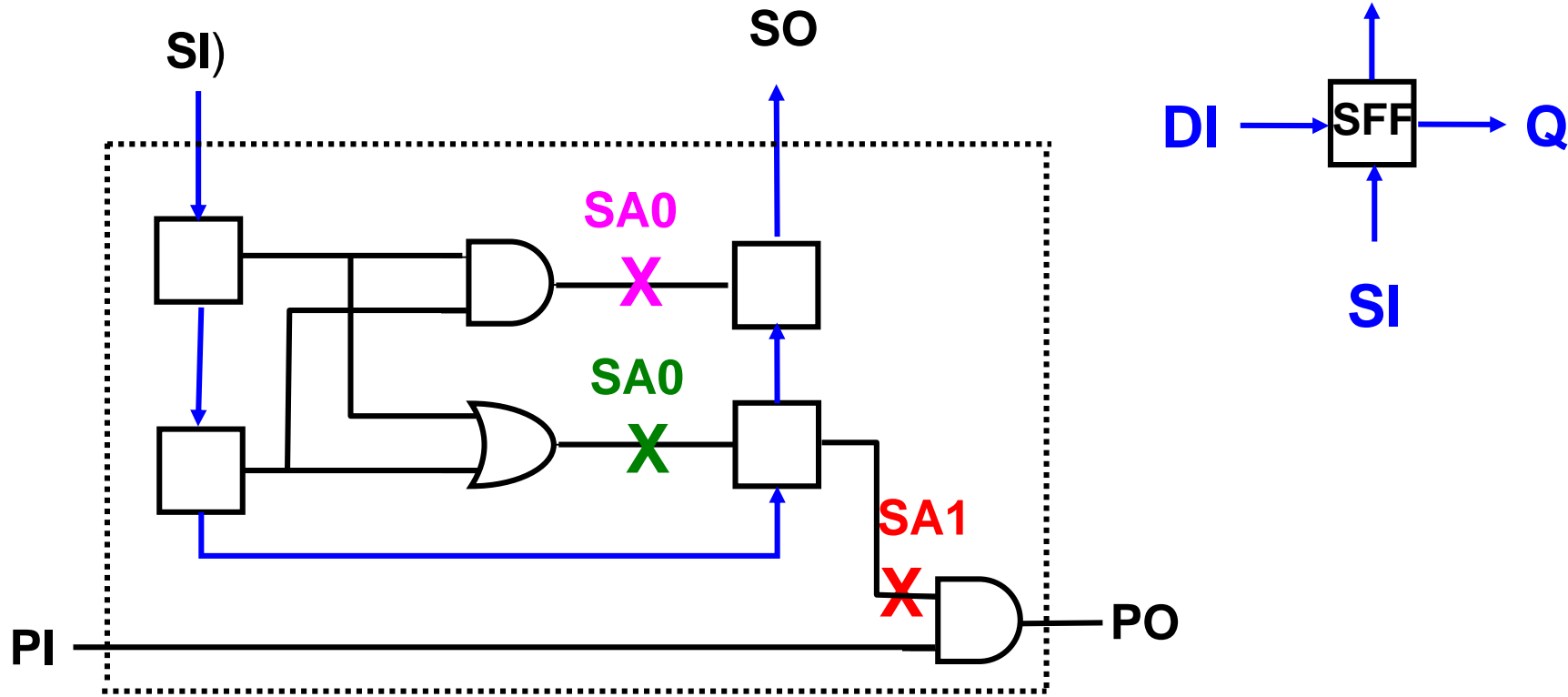

load		capture		unload
CK = PPPP		CK=P		CK = PPPP
SE = 1111	SE 1→0	SE = 0	SE 0→1	SE = 1111
SI = X011				SO = <span style="color: magenta;">H</span> <span style="color: green;">H</span> XX
PI = 1	PO = <span style="color: red;">L</span>			


P = CK pulse  
H=expected 1  
L=expected 0  
Left bit first in/out




# Test Mode Operation

- **Stuck-at fault testing**
  - ◆ **One pattern per scan in/out**
- **Delay fault testing**
  - ◆ **Two-patterns per scan in/out**
    - \* **Launch-on-Shift (aka. Skew load)**
    - \* **Lunch-on-Capture (aka. Broad-side load)**

# LOS Operation

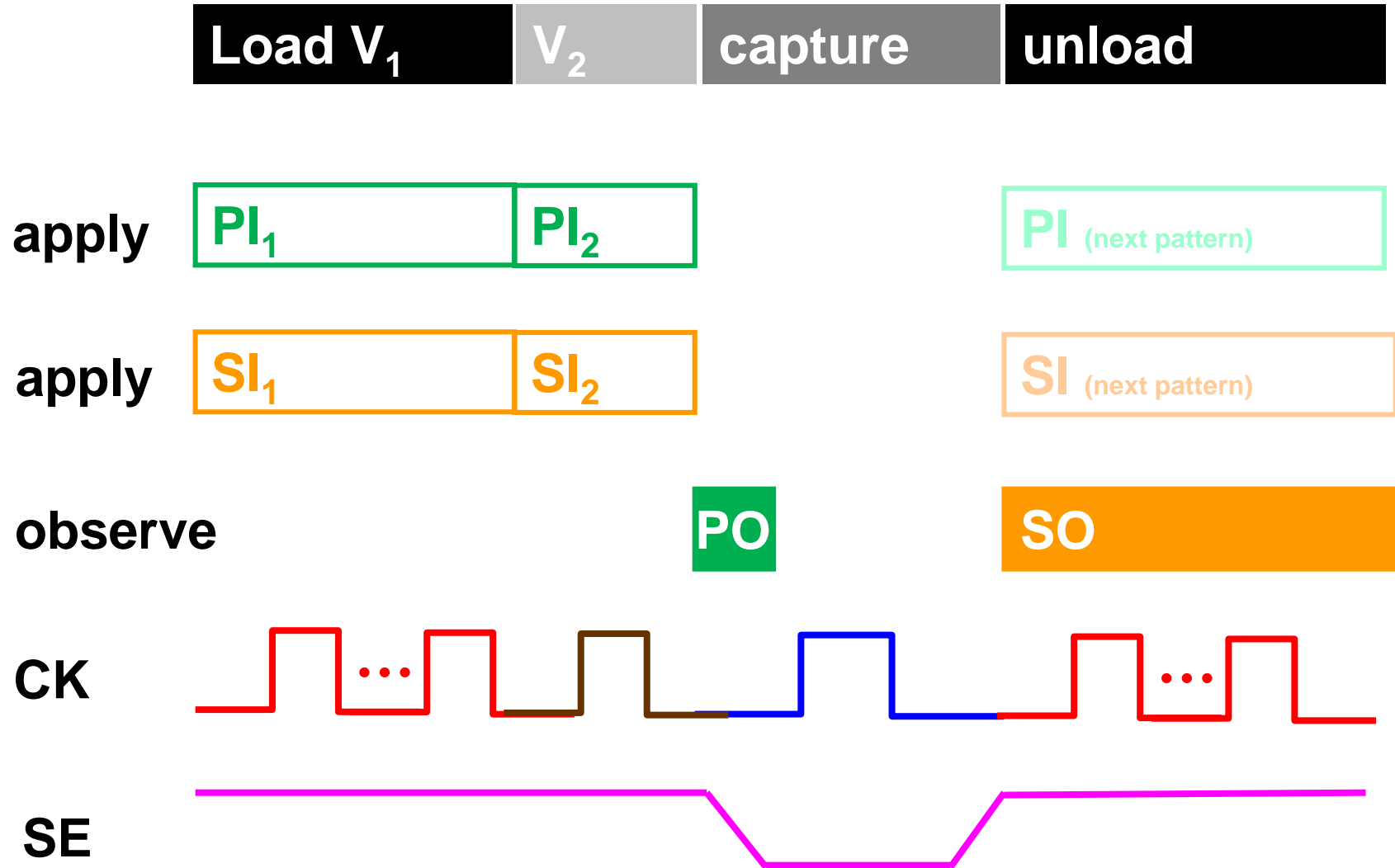

# LOS Example

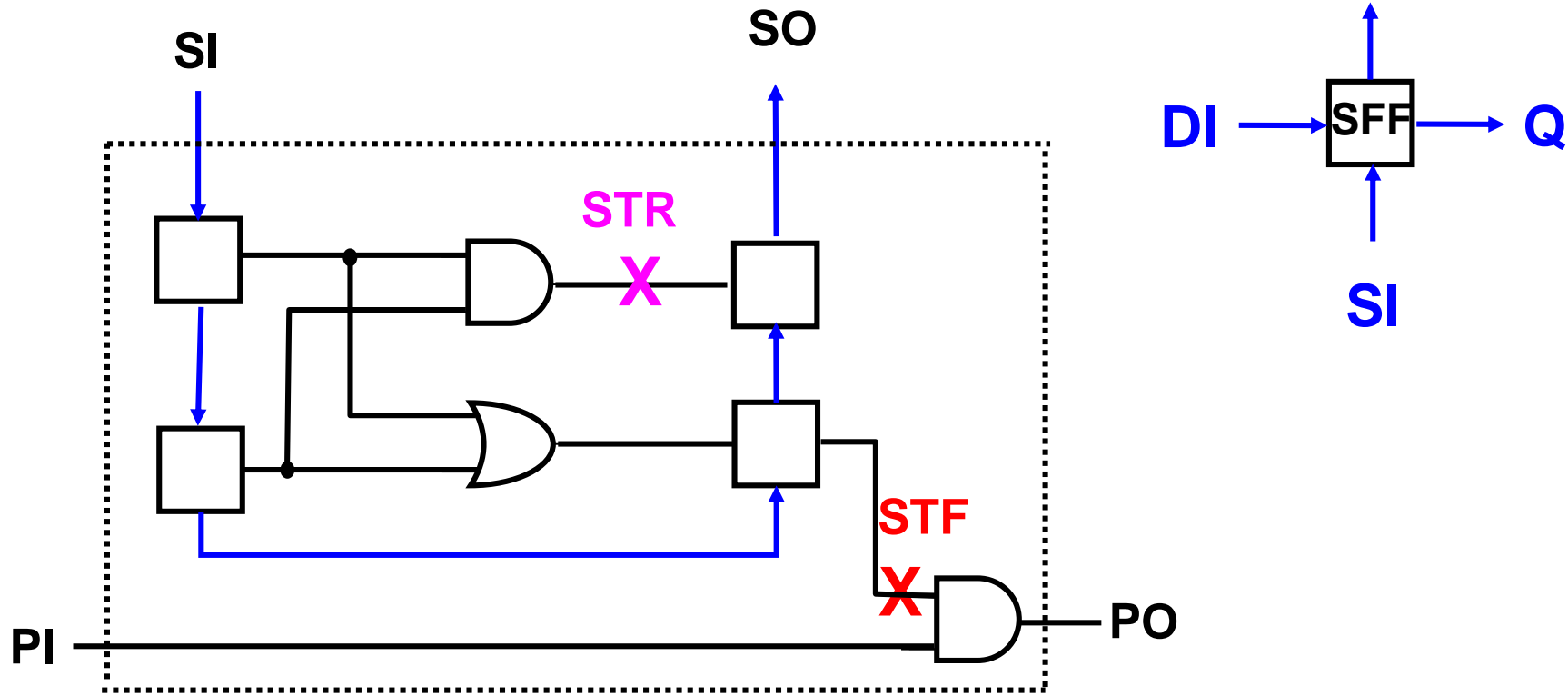

load $V_1$	$V_2$		Capture		unload
CK = PPPP	CK=P		CK=P		CK = PPPP
SE = 1111	SE=1	SE 1→0	SE = 0	SE 0→1	SE = 1111
SI = X101	SI=1				SO = HXXX
PI = X	PI=1	PO=L			


# LOS -- Pro and Cons

- Advantages

- + Easier for combinational ATPG


- Disadvantages

 - $V_2$ -capture time is not at-speed
    - » Scan\_enable signal fall time limitation
    - » Currently, ~ 5ns minimum
    - » Solution: route scan\_enable as clock (area overhead)
  - Invoke transitions that never happen in normal operation
  - Some TDF not testable; *structure dependency problem*
    - »  $V_2$  is shifted version of  $V_1$


 
# Structure Dependency

- STR fault untestable using LOS
- This fault can actually happen in normal operation
  - ♦ This fault needs to be tested, but how?



**Some faults are untestable by LOS**

# Test Mode Operation

- Stuck-at fault testing
  - ◆ One pattern per scan in/out
- Delay fault testing
  - ◆ Two-patterns per scan in/out
    - \* Launch-on-Shift (aka. Skew load)
    - \* Lunch-on-Capture (aka. Broad-side load)

# LOC Operation



apply



apply




observe

P  
O




CK

 

SE



# LOC Example

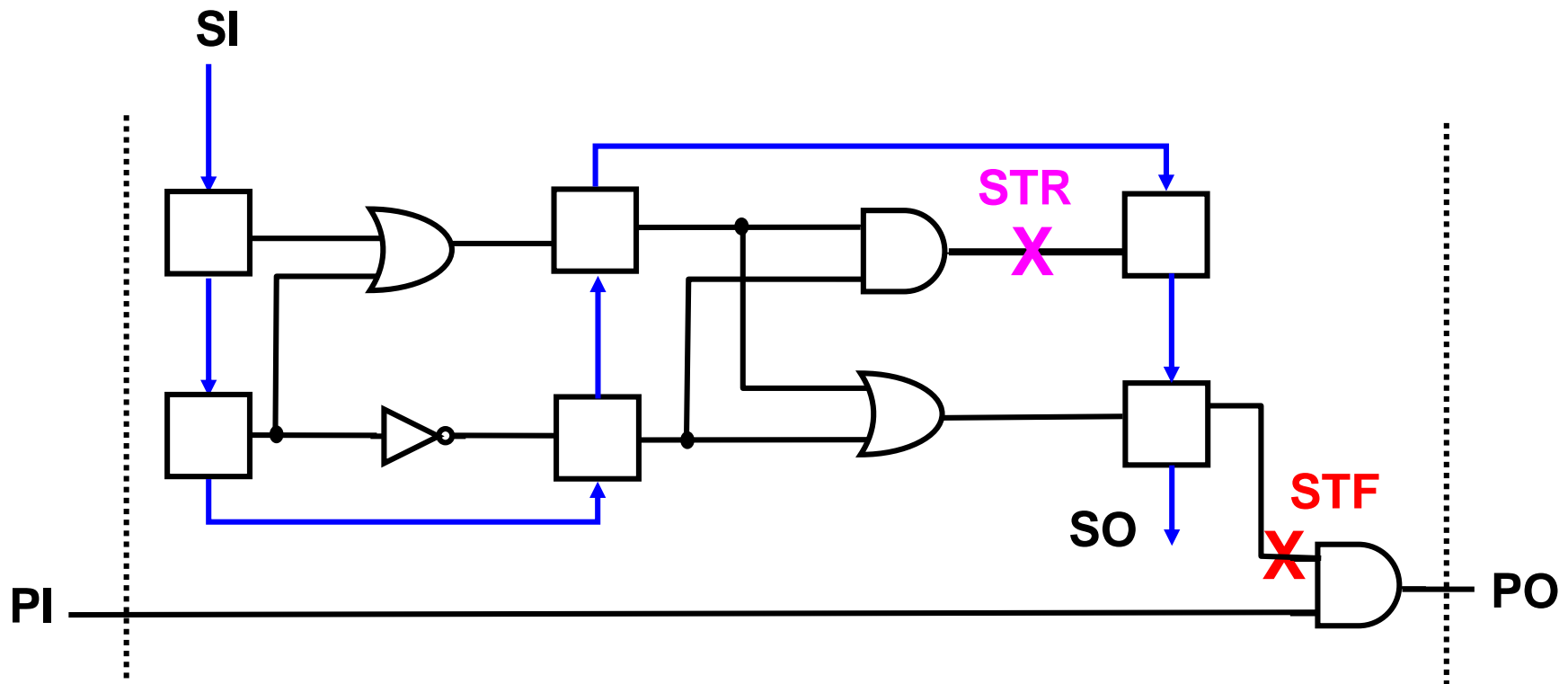

Load $V_1$		$V_2$		capture		unload
CK=PPPPPP		CK=P		CK=P		CK=PPPPPP
SI=1X0001		SI=X				SO=X <sup>H</sup> XXXX
SE=111111	SE 1→0	SE=0	SE=0	SE=0	SE 0→1	SE=111111
PI=X	PI=1		PO=L		SO=X	




# LOC -- Pro and Cons

- Advantages

- +  $V_2$ -capture can be applied at system clock speed
  - + True at-speed testing
- + Avoid structure dependency problem of LOS
- + Minimum work in physical design, SE can be routed as normal signal

- Disadvantages

 - ATPG is more complex
  - » Requires two time frames



# FFT

- **Q: Are there faults untestable by LOC?**
  - ♦ **If so, how should we test them?**