 


# Fault Modeling

- Introduction
- **Fault Models**
  - ◆ Stuck-at fault (1961)
  - ◆ Bridging fault (1973)
  - ◆ **Delay fault (1974)**
    - \* Path delay fault (PDF)
    - \* Transition delay fault (TDF)
  - ◆ Transistor level fault
- Fault Detection
- Fault Coverage
- Conclusion





# Classification of Fault Models


  
# Some Defects Are Not Stuck-at

- Some defects change circuit **timing** but not function
  - ① **Random defects**: Resistive opens, resistive bridging,
  - ② **Systematic defects**: crosstalk, process variation in  $V_t$




- **Delay fault** cause a circuit [Breuer 74]
  - ♦ fails to operate correctly at **specified speed**
  - ♦ but produces correct output at **slower speed**

**Delay Fault Models Are Needed**
 
# How to Detect Delay Faults?

- Two categories

- ① **Global delay fault**: affects large area of circuit
  - \* Example: Wrong doping  $\rightarrow V_t$  shift
  - \* Can be detected by *on-chip process monitors*




- ② **Local delay fault**: affects small area of circuit
  - \* Poor contact/via  $\rightarrow$  resistive open
  - \* Can be detected by *delay testing*

**Delay Testing Detects Delay Faults**
 
# What Patterns for Delay Test?

- Delay faults needs *two-pattern test*
  - ♦ As opposed to *one-pattern test* for stuck-at faults
- A two-pattern test consists of a pair of test patterns (test vectors)
  - ♦  $V_1$ : initialize circuit state
  - ♦  $V_2$ : *launch* transition, *propagate fault effect* to output
- Control timing ( $T$ ) between  $V_1$  and  $V_2$  carefully



**Delay Faults Require 2-pattern Test**


# Fault Modeling

- Introduction
- **Fault Models**
  - ◆ Stuck-at fault (1961)
  - ◆ Bridging fault (1973)
  - ◆ **Delay fault (1974)**
    - \* **Path delay fault (PDF)**
    - \* **Transition delay fault (TDF)**
  - ◆ Transistor level fault
- Fault Detection
- Fault Coverage
- Conclusion


 
# Two Delay Fault Models


- **Path Delay Fault, PDF** [Smith 85]
  - ♦ Path delay of the faulty path > clock period
- **Transition (Delay) Fault, TDF** [Barzilai 83] [Levendel 86]
  - ♦ Path delay of all paths through the faulty node > clock period
- Other delay fault models
  - ♦ Gate delay fault [Iyengar 88]
  - ♦ Segment delay fault [Heragu 96]
  - ♦ ...




**Trade off Model Complexity and Accuracy**
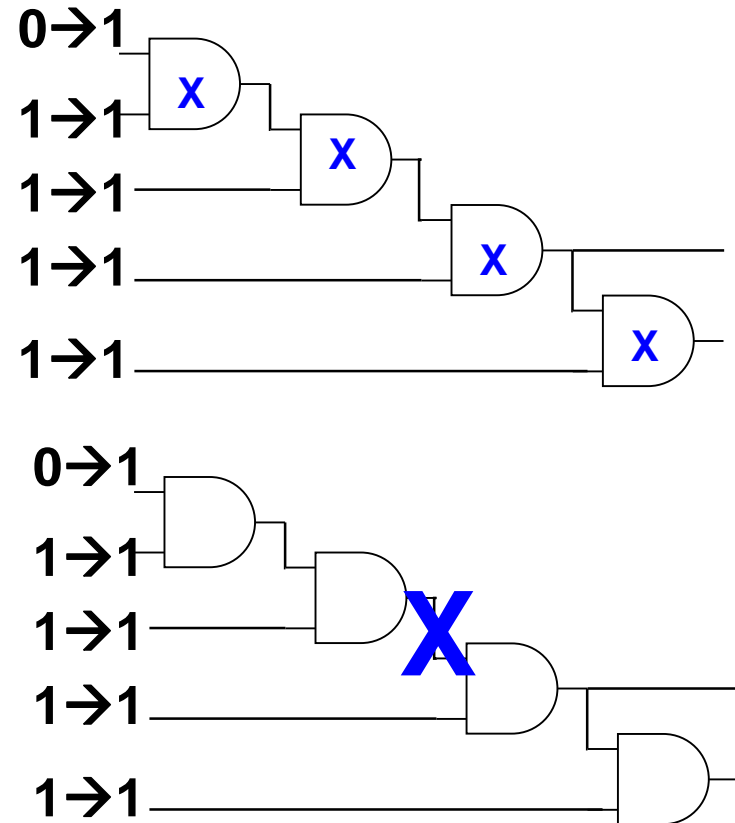
# Example

- Clock period = **10.0ns**
  - ♦ good gate delay = **2.0ns**
- PDF (fault distributed along path)
  - ♦  $\underline{3.0} + \underline{2.6} + \underline{2.7} = 8.3 < 10 \rightarrow \text{pass}$
  - ♦  $\underline{3.0} + \underline{2.6} + \underline{2.7} + \underline{2.9} = 11.2 > 10 \rightarrow \text{fail}$
- TDF (lumped fault = 9.0 ns)
  - ♦  $2.0 + 2.0 + 2.0 + \underline{9.0} = 15.0 \rightarrow \text{fail}$
  - ♦  $2.0 + 2.0 + 2.0 + \underline{9.0} + 2.0 = 17.0 \rightarrow \text{fail}$



 
Faulty size =  $\text{delay}_{\text{faulty}} - \text{delay}_{\text{good}}$




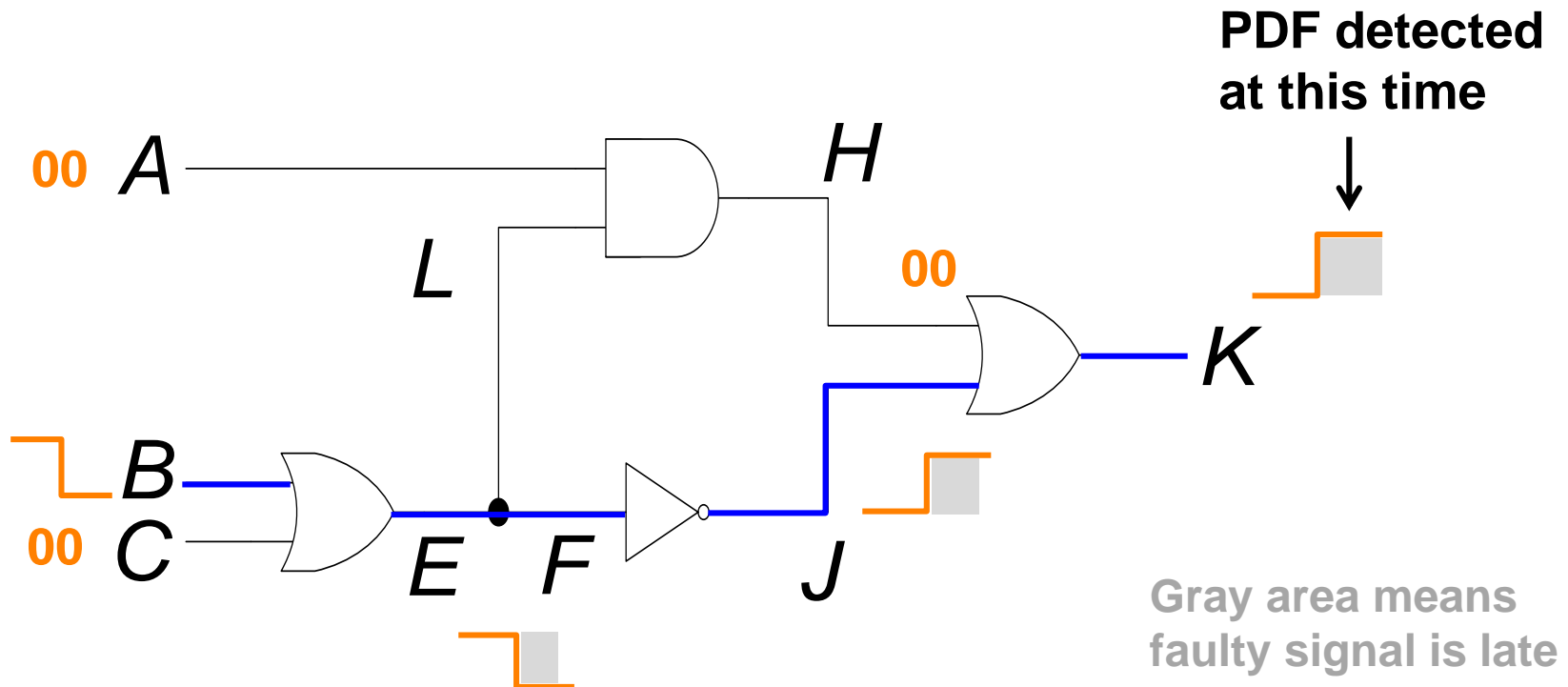
# Path Delay Fault (PDF)

- For each path, two polarity: **falling** ↓ , **rising** ↑ (at PI)
- Example:
  - ♦ 5 paths: {AHK, BELHK, BEFJK, CELHK, CEFJK}
  - ♦ 10 path delay faults
  - ♦ Two-pattern test for PDF ↓BEFJK




# Quiz

Q1: How many path delay faults in this circuit?

A:

Q2: Does  $ABC=001 \rightarrow 011$  detect  $\uparrow BEFK$  fault?

A:

 


# Fault Modeling

- Introduction
- **Fault Models**
  - ◆ Stuck-at fault (1961)
  - ◆ Bridging fault (1973)
  - ◆ **Delay fault (1974)**
    - \* Path delay fault (PDF)
    - \* **Transition delay fault (TDF)**
  - ◆ Transistor level fault
- Fault Detection
- Fault Coverage
- Conclusion


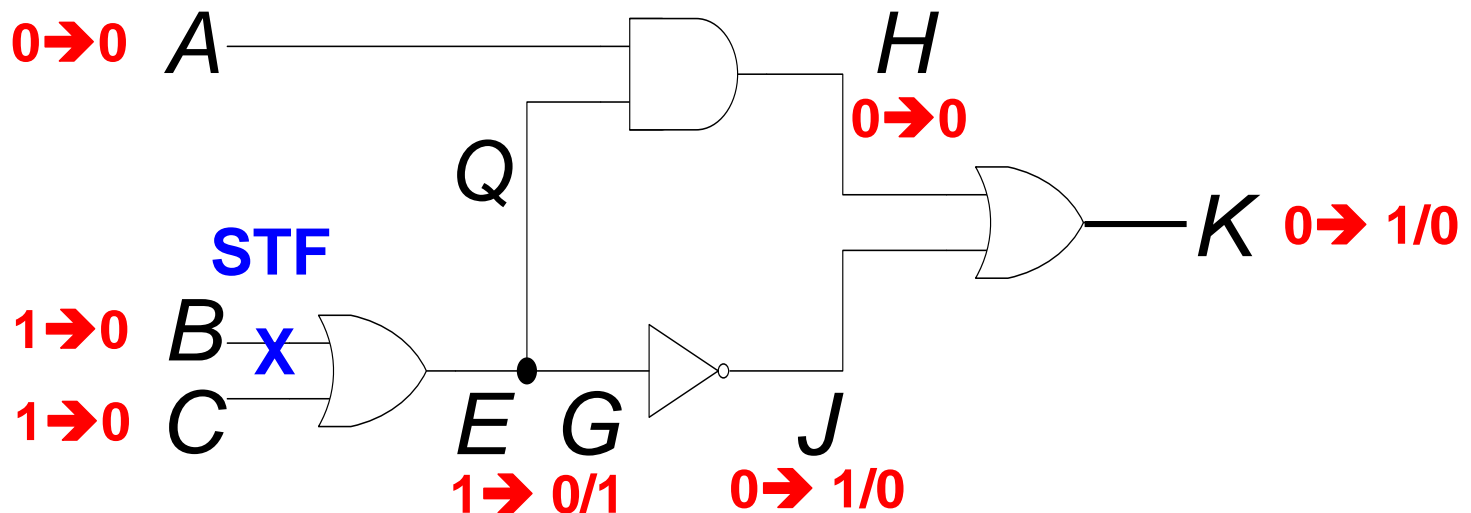
# Transition Delay Fault (TDF)

- Each node has 2 TDF: *slow-to-rise (STR)*, *slow-to-fall (STF)*
- Two-pattern test for TDF
  - ♦  $V_1$ : Initialization pattern: control initial value at fault site
    - \* 0 for STR fault, 1 for STF fault
  - ♦  $V_2$ : launch transition and propagate fault effect to output
    - \* Detect **SA0** for STR fault, **SA1** for STF fault
- Example: total 9 nodes, 18 TDF
  - ♦ **B STF** fault detected




# Quiz

Q1: How many transition delay faults in this circuit?


A:

Q2: Does  $ABC=001 \rightarrow 011$  detects B STR fault?

A:

 

# Experimental Results

 

**No One Can Replace Each Other**

# Summary

- Delay fault important for advanced technologies
- Two popular delay fault models
  - ♦ Path delay fault (PDF): two faults **per path**
    - \* Rising, falling
  - ♦ Transition delay fault (TDF): two faults **per node**
    - \* STR, STF

	Path Delay Fault	Transition Delay Fault
Number of faults	☹ WC exponential	😊 linear
Fault size and distribution	😊 small fault size 😊 distributed	☹ large fault size only ☹ lumped

# FFT

- Q: Give an example circuit where number of paths is exponential to number of gates

	Path Delay Fault	Transition Delay Fault
Number of faults	☹️ <b>WC exponential</b>	😊 <b>linear</b>
Fault size and distribution	😊 <b>small fault size</b> 😊 <b>distributed</b>	☹️ <b>large fault size</b> ☹️ <b>lumped</b>