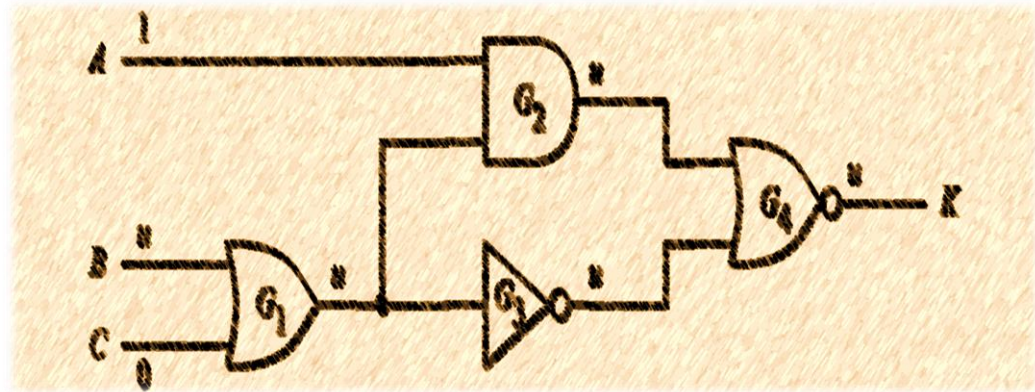




Logic Simulation

- Introduction
- Simulation Models
- Logic Simulation Techniques
 - ◆ Compiled-code simulation
 - * Logic Optimization
 - * Logic Levelization
 - * Code Generation
 - ◆ Event-driven simulation
 - ◆ Parallel Simulation
- Issues of Logic Simulations
- Conclusions



Compiled-Code Simulation

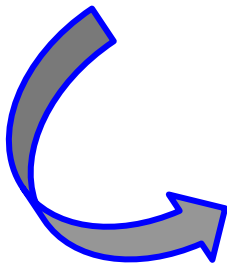
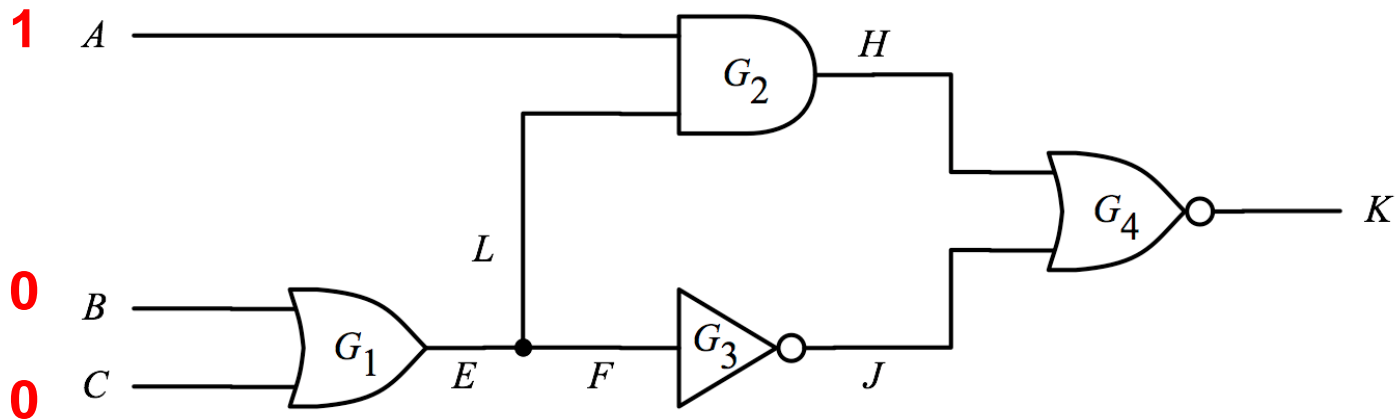
- Translate circuit into sequence of codes
 - ♦ **Execute codes** = run logic simulation



```
while{true} do
    read(A,B,C);
    E  OR(B,C);
    H  AND(A,E);
    J  NOT(E);
    K  NOR(H,J);
end
```

$E = \text{OR}(0,0) = 0$
 $H = \text{AND}(1,0) = 0$
 $J = \text{NOT}(0) = 1$
 $K = \text{NOR}(0,1) = 0$

How to Compile Code?

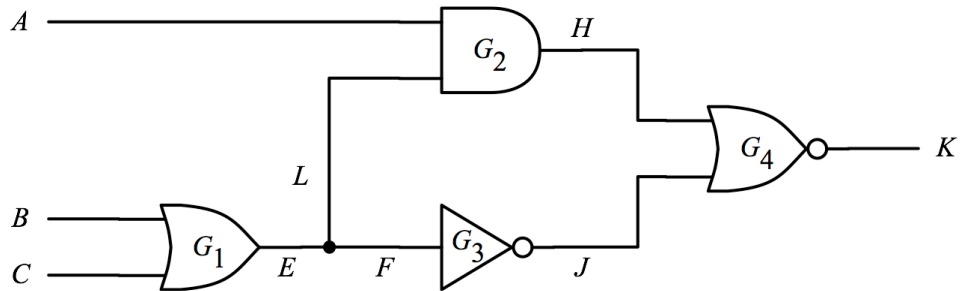
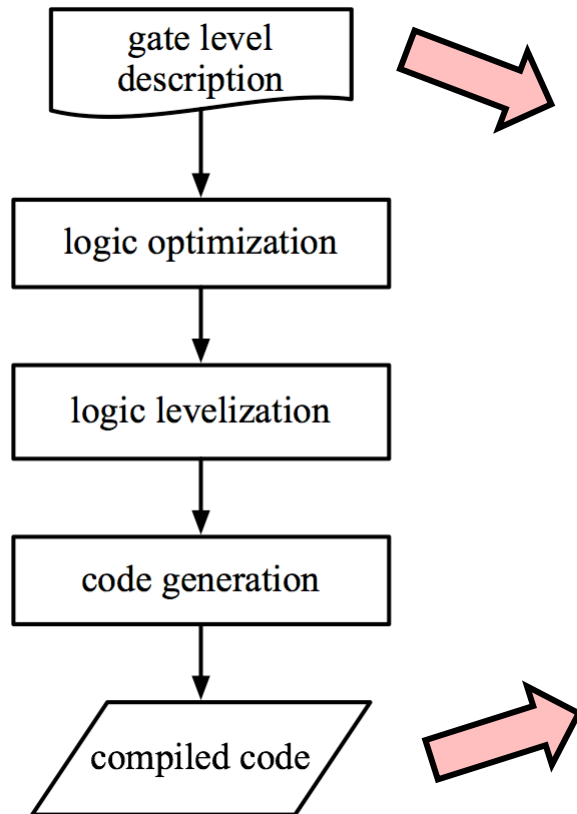


```
while{true} do
    read(A,B,C);
    E  OR(B,C);
    H  AND(A,E);
    J  NOT(E);
    K  NOR(H,J);
end
```

(WWW Fig. 3.12)

Logic Optimization

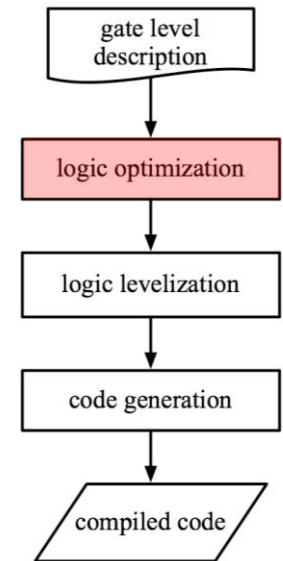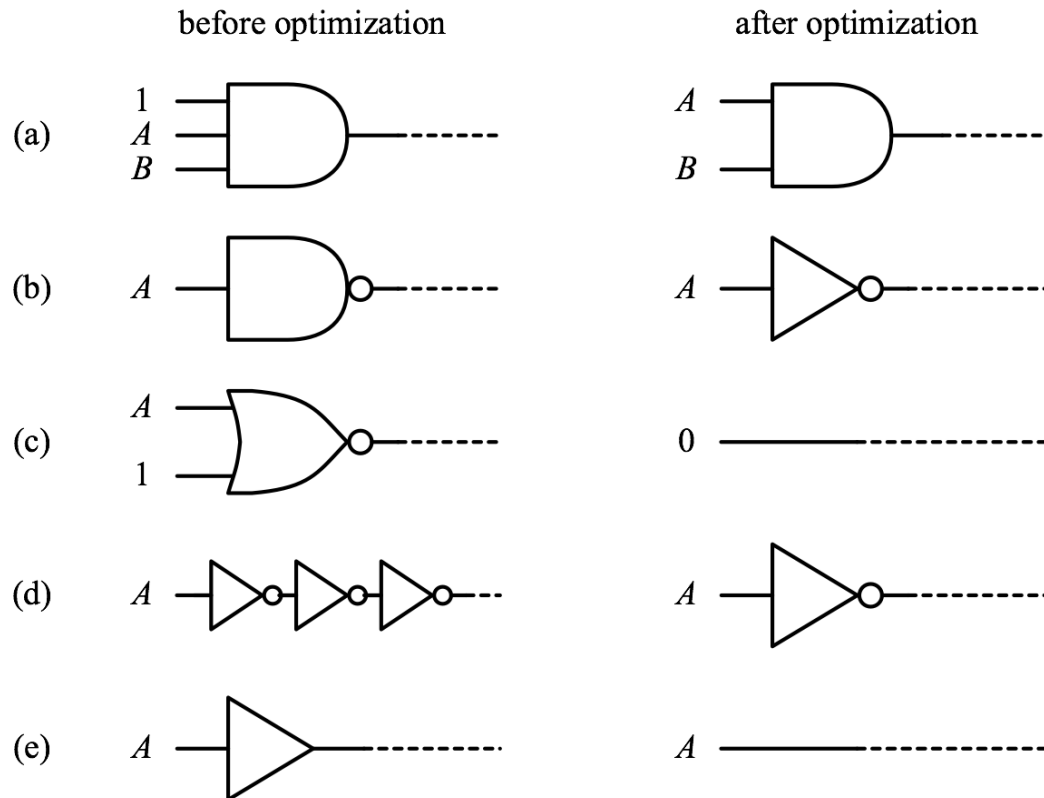
- Simplify logic before generating codes
- Shorten code length and simulation time
- Example (WWW Fig. 3.13)



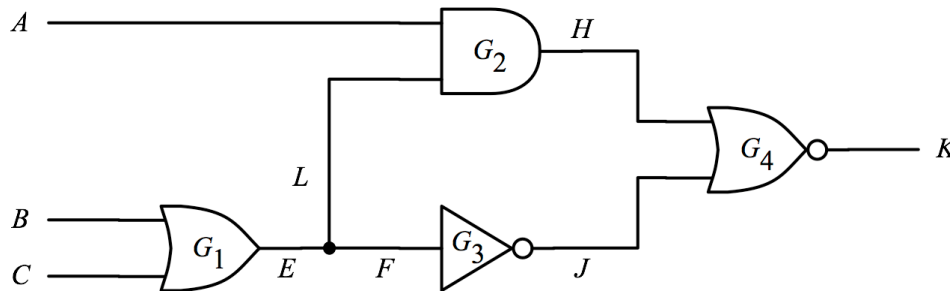(b) Code generation flow

Logic Levelization

- **Levelization**: order gate in sequence such that
 - ♦ a gate won't be evaluated until
 - ♦ all its driving gates have been evaluated




correct

```
while{true} do
    read(A,B,C);
    E OR(B,C);
    H AND(A,E);
    J NOT(E);
    K NOR(H,J);
end
```



wrong
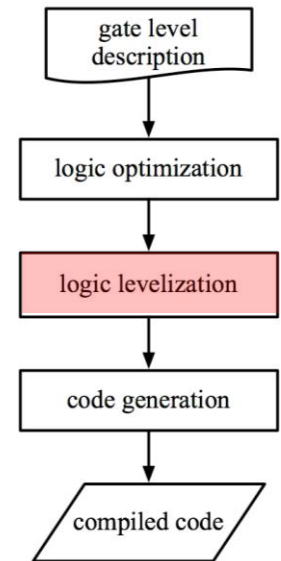
```
while{true} do
    read(A,B,C);
    H AND(A,E);
    E OR(B,C);
    J NOT(E);
    K NOR(H,J);
end
```



(b) Code generation flow

Levelization Ensures Correct Order

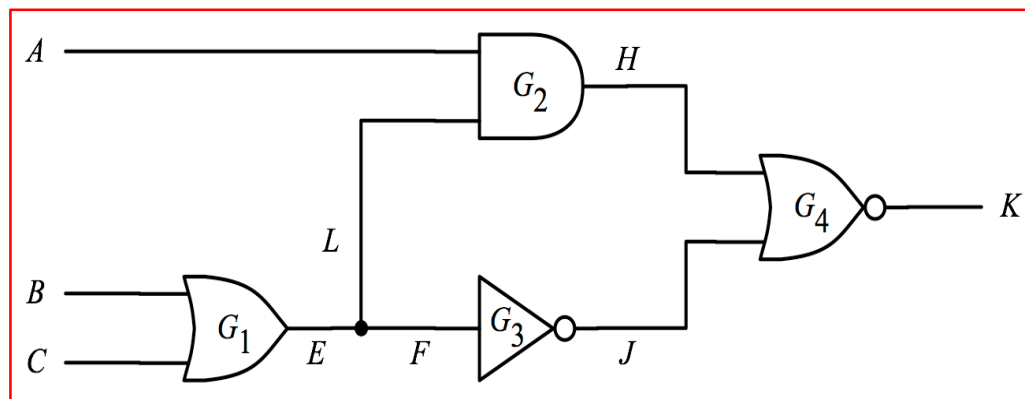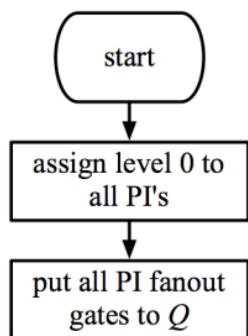

(WWW Fig 3.17)


g = gate

l = level

Q = queue (FIFO)


step	A	B	C	G_1	G_2	G_3	G_4	Q <front, back>
0	0	0	0					< G_2 , G_1 >
1	0	0	0					< G_1 , G_2 > put G_2 back
2	0	0	0	1				< G_2 , G_2 , G_3 >
3	0	0	0	1	2			< G_2 , G_3 , G_4 >
4	0	0	0	1	2			< G_3 , G_4 , G_4 > why? FFT
5	0	0	0	1	2	2		< G_4 , G_4 , G_4 >
6, 7, 8	0	0	0	1	2	2	3	<>

Quiz

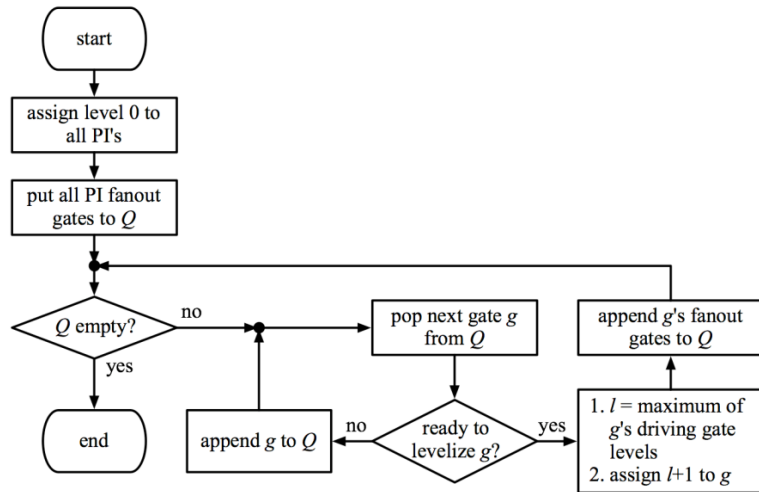

Q: Please levelize this circuit

A:

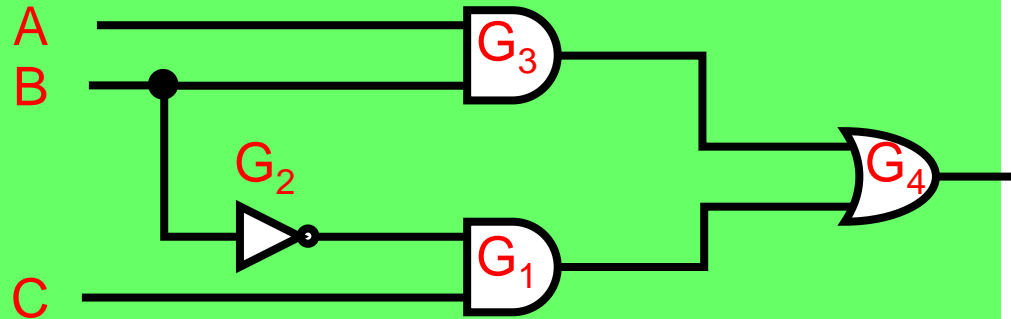

step	A	B	C	G_1	G_2	G_3	G_4	Q <front, back>
0	0	0	0					< G_1, G_2, G_3 >
1								
2								
3								
4								
5								
6								

Code Generation

① High-level code (like C)

😊 Portable, easy debug

😞 Need compilation every time circuit changed

② Machine code

😊 Fast to run


😞 Not portable, hard to debug

③ Interpreted code


(at run time, codes are interpreted and executed)

😊 Portable, easy debug

😞 Slower than machine code

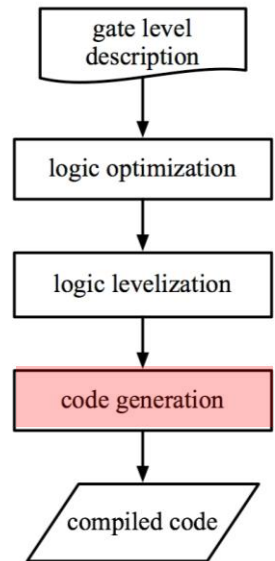

(b) Code generation flow

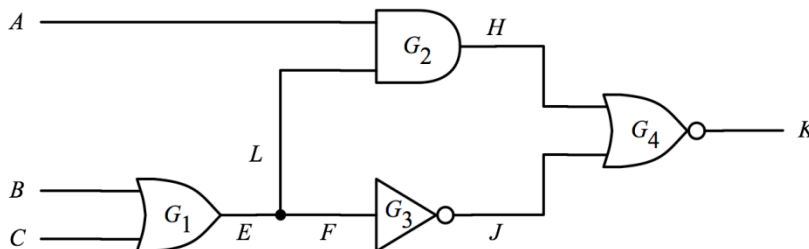

```
while{true} do
    read(A,B,C);
    E OR(B,C);
    H AND(A,E);
    J NOT(E);
    K NOR(H,J);
end
```


Summary

- Compiled-code simulation: convert gates into **codes** for evaluation
 - ◆ **Optimization**: simplifies logic
 - ◆ **Levelization**: sort gates in order (*i.e.* topological sort of graph)
 - ◆ **Code generated**: 1.high-level, 2.machine, 3.interpreted



😊 Pros

- ◆ **Simple** to implement
- ◆ Can speed-up by **parallelism**
 - * see parallel simulation

😞 Cons

- ◆ Only **cycle-based accuracy**, no timing (zero gate delay)
- ◆ Need to evaluate **whole circuit** even only small portion changed
 - * see event-driven simulation

FFT

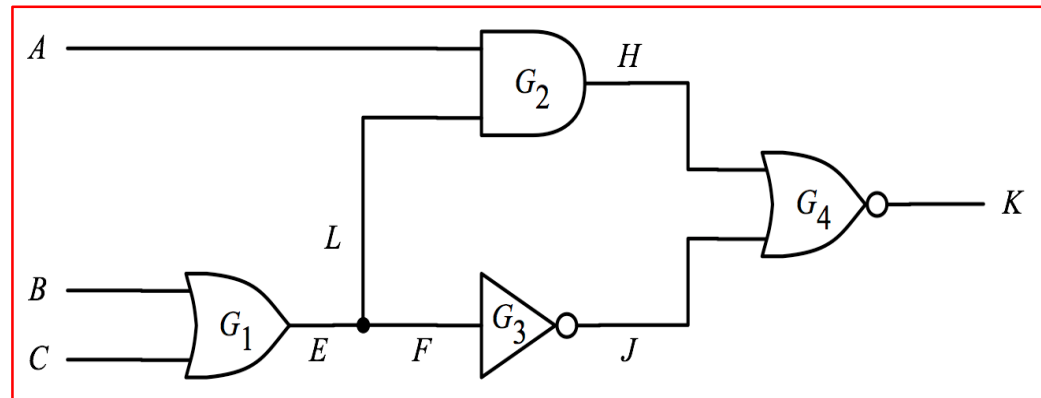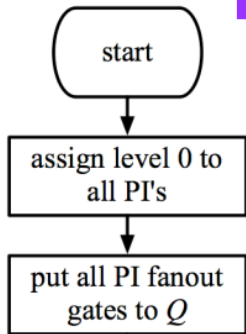

(WWW Fig 3.17)

g = gate


l = level

Q = queue (FIFO)

step	A	B	C	G_1	G_2	G_3	G_4	Q <front, back>
0	0	0	0					< G_2 , G_1 >
1	0	0	0					< G_1 , G_2 >
2	0	0	0	1				< G_2 , G_2 , G_3 > why G_2 again?
3	0	0	0	1	2			< G_2 , G_3 , G_4 >
4	0	0	0	1	2			< G_3 , G_4 , G_4 > why G_4 again?
5	0	0	0	1	2	2		< G_4 , G_4 , G_4 >
6, 7, 8	0	0	0	1	2	2	3	<>


FFT

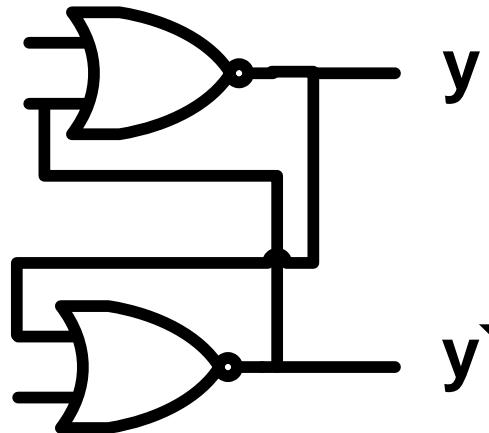- Q:How to levelize SR latch?
 - ♦ with feedback






Appendix: Logic Symbols

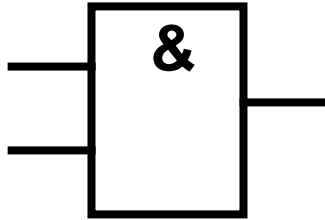- IEEE logic symbols: rectangular shape v.s. distinctive shape
- AND



- Or

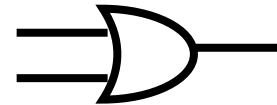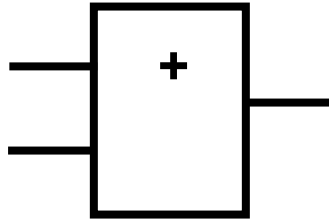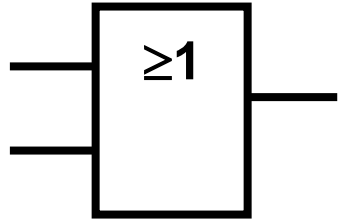

- inverter

