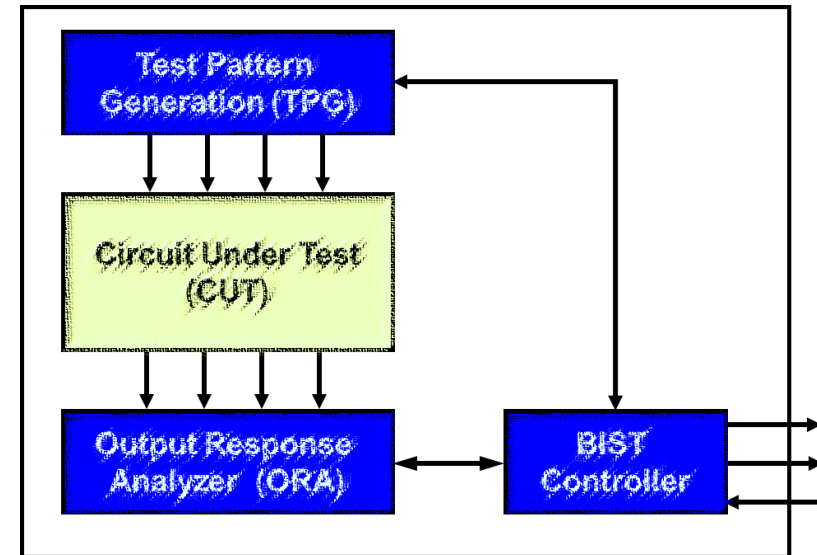



# BIST Part1 - TPG

- Introduction
- Test Pattern Generation (TPG)
  - ◆ Deterministic: ROM, Algorithm, Counter
  - ◆ Pseudo Random
    - \* Linear Feedback Shift Register, LFSR (1977)
      - Two types of LFSR
      - Design of LFSR
        - ⇒ How to find seed?
        - ⇒ What polynomial?
        - ⇒ All-zero pattern?
        - ⇒ What is LFSR degree?
    - \* Cellular Automata, CA (1984)



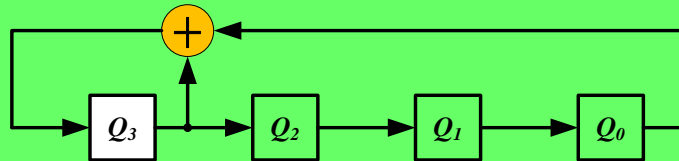
# Quiz

Q: Given two LFSR of  $x^4+x^3+1$ ,  $x^4+x^2+1$ . seed=1000. Fill in table.  $L_c=?$



state	$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	1	0	0	0
1	1	1	0	0
2	1	1	1	0
3	1	1	1	1
4	0	1	1	1
5	1	0	1	1
6	0	1	0	1
7	1	0	1	0
8	1	1	0	1
9	0	1	1	0
10	0	0	1	1
11	1	0	0	1
12	0	1	0	0
13	0	0	1	0
14	0	0	0	1
15 (=0)	1	0	0	0

$L_c=15$

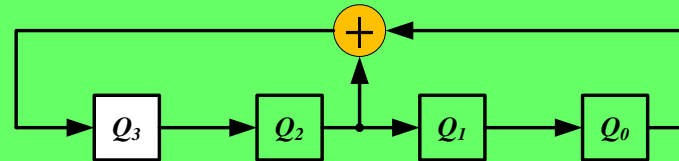


state	$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	1	0	0	0
1				
2				
3				
4				
5				
6				
7				
8				
9				
10				
11				
12				
13				
14				
15				




$L_c=?$

# Polynomial and $L_c$

$$x^4 + x^3 + 1$$

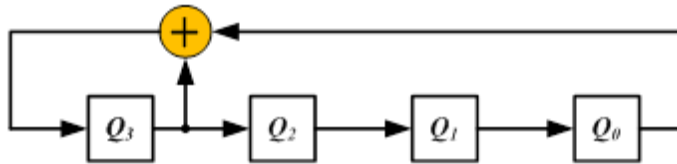

$$x^4 + x^2 + 1$$

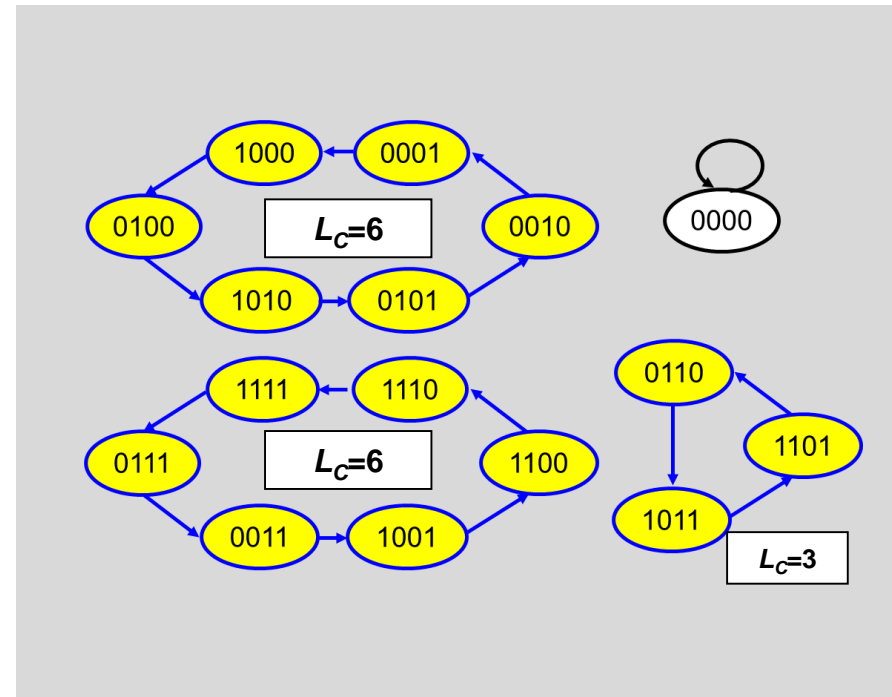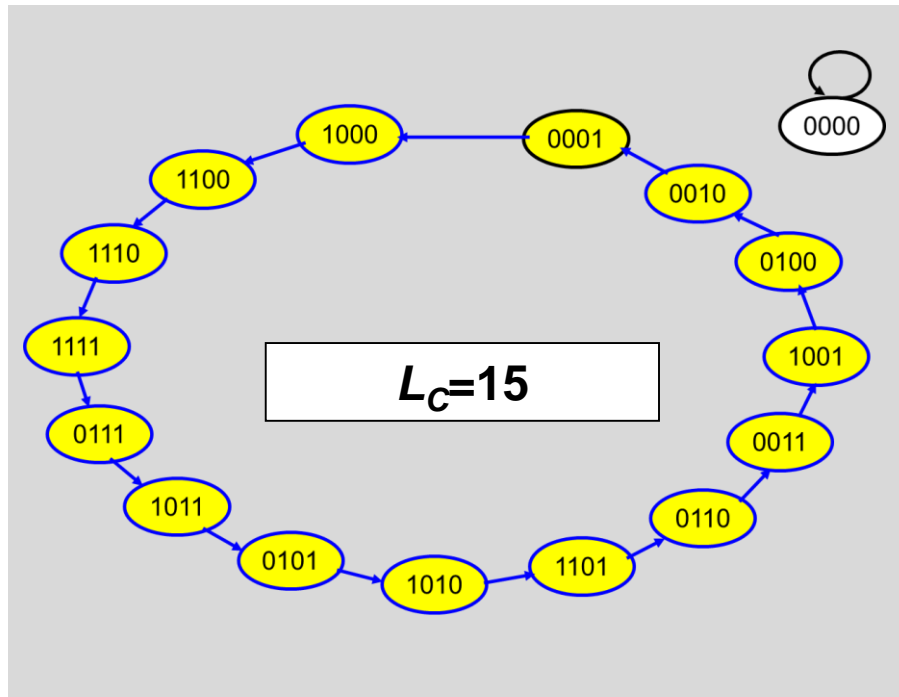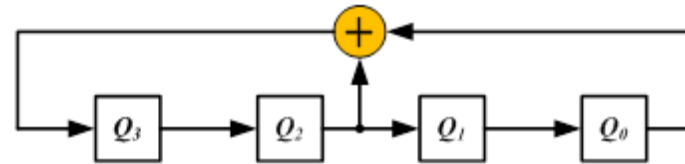

**Larger  $L_c$  , Better TPG**

# Primitive Polynomial


- **Primitive polynomial** (PP) generates **maximum-length sequence**
  - ♦  $L_c = 2^N - 1$ ,  $N$ =degree of PP
- PP **NOT unique** for a given  $N$ 
  - ♦  $1+x+x^4$ ,  $1+x^3+x^4$  are both PP
- PP of degree  $N$  must satisfy:
  - ♦ PP is *irreducible*
  - ♦ PP has odd number of terms
  - ♦ PP divides  $1+x^{2^N-1}$  ;  $N>3$
  - ♦ more details see (BMS 87)
- PP can be found by *Seive Method*
  - ♦ Many available on line

$N$	primitive polynomial $f(X)$
1,2,3,4,6,7,15,22	$1 + X + X^N$
5,11,21,29	$1 + X^2 + X^N$
10,17,20,25,28,31	$1 + X^3 + X^N$
9	$1 + X^4 + X^N$
23	$1 + X^5 + X^N$
18	$1 + X^7 + X^N$
8	$1 + X^2 + X^3 + X^4 + X^N$
12	$1 + X + X^2 + X^4 + X^N$
13	$1 + X + X^3 + X^4 + X^N$
14,16	$1 + X^3 + X^4 + X^5 + X^N$
19,27	$1 + X + X^2 + X^5 + X^N$
24	$1 + X + X^2 + X^7 + X^N$
26	$1 + X + X^2 + X^6 + X^N$
30	$1 + X + X^2 + X^{23} + X^N$
32	$1 + X + X^2 + X^{22} + X^N$

**PP Often Used to Design TPG**

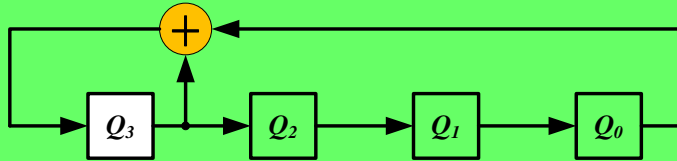
# Quiz

Q: Compare two PP  $x^4+x^3+1$ ,  $x^4+x+1$ . Fill in table.  $L_c=?$



state	$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	1	0	0	0
1	1	1	0	0
2	1	1	1	0
3	1	1	1	1
4	0	1	1	1
5	1	0	1	1
6	0	1	0	1
7	1	0	1	0
8	1	1	0	1
9	0	1	1	0
10	0	0	1	1
11	1	0	0	1
12	0	1	0	0
13	0	0	1	0
14	0	0	0	1
15 (=0)	1	0	0	0

$L_c=15$

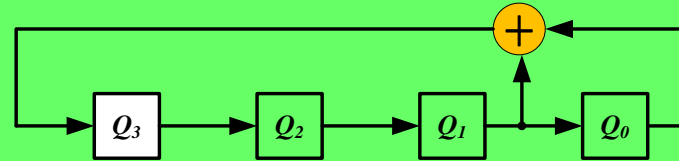


state	$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	1	0	0	0
1				
2				
3				
4				
5				
6				
7				
8				
9				
10				
11				
12				
13				
14				
15 (=0)				

$L_c=?$
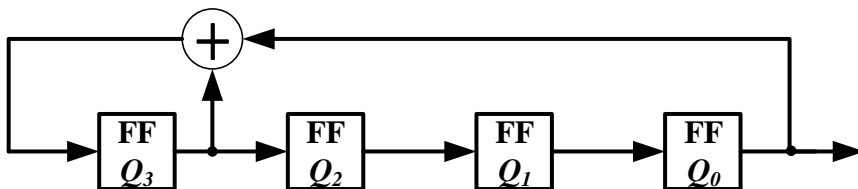
# m-Sequence

- A sequence generated by *primitive polynomial* LFSR is called
  - ♦ **Maximum-length sequence (m-sequence)**
  - ♦ **aka. pseudorandom sequence, pseudonoise sequence**
- m-sequence has period  $L_c = 2^N - 1$
- Example:  $N=4$ 
  - ♦  $x^4 + x^3 + 1$
  - ♦ Period  $L_c = 15$



**m-sequence=000111101011001**  
(left bit first)

state	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	1	0	0	0
1	1	1	0	0
2	1	1	1	0
3	1	1	1	1
4	0	1	1	1
5	1	0	1	1
6	0	1	0	1
7	1	0	1	0
8	1	1	0	1
9	0	1	1	0
10	0	0	1	1
11	1	0	0	1
12	0	1	0	0
13	0	0	1	0
14	0	0	0	1

m-sequence


# Properties of m-Sequence (1)

- 1. Period  $L_c = 2^N - 1$ 
  - ♦ Example:  $x^4 + x^3 + 1$ ,  $N=4$
  - ♦ 000111101011001
  - ♦  $L_c=15$
- 2.  $2^{N-1}$  ones and  $2^{N-1}-1$  zeros (almost equal probability)
  - ♦ Example:
  - ♦ 8 ones, 7 zeros
- 3. If a window of width  $N$  is slid along m-sequence, each of  $2^N - 1$  non-zero  $N$ -tuple is seen **exactly once** in a period

0	0	0	1	1	1	1	0	1	0	1	1	0	0	1	0	0	0	
0	0	0	1															
	0	0	1	1														
		0	1	1	1													
			1	1	1	1												
				1	1	1	0											
					1	1	0	1										
						1	0	1	0									
							0	1	0	1								
								1	0	1	1							
									0	1	1	0						
										1	1	0	0					
											1	0	0	1				
												0	0	1	0			
													0	1	0	0		
															1	0	0	0

# Properties of m-Sequence (2)

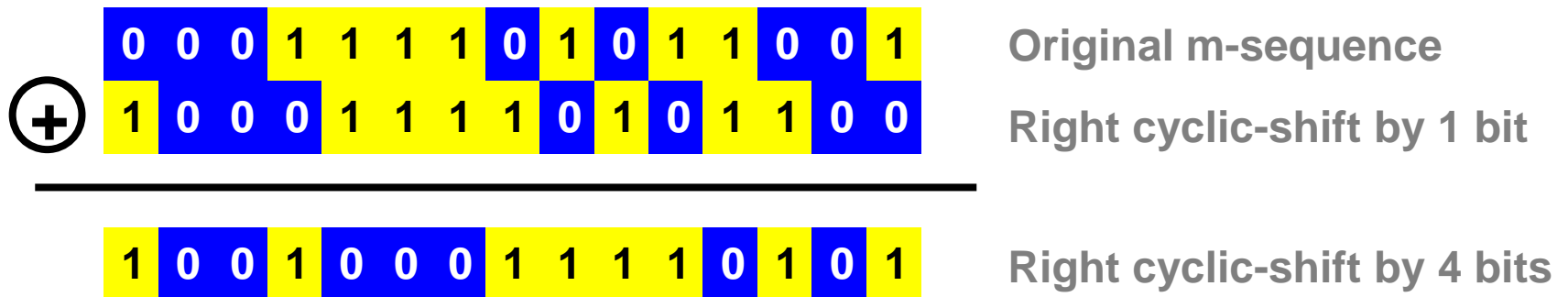- 4. m-sequence + its *cyclic shift* = **another cyclic shift** of itself
  - ♦ **cyclic-shift-and-add property**
  - ♦ This property is useful for *phase shifter* (see BIST-2 chapter)
  - ♦ Example: m-sequence of  $x^4+x^3+1$ ,  $N=4$ 
    - \* NOTE: mod-2 add = XOR



- See *finite field theory* or (BMS 87) for more properties

**m-sequence Has Nice Properties**



# Quiz

Q: Given another m-sequence **000100110101111**  
generated by PP  $x^4+x+1$ .

Show that it also satisfies properties:

- 1)  $L_c=15$
- 2) 8 ones and 7 zeros
- 3) it has cyclic-shift-add property

original + left-shift-by-2-bit = left-shift-by-?-bit


A:

$\oplus$

0	0	0	1	0	0	1	1	0	1	0	1	1	1	1
0	1	0	0	1	1	0	1	0	1	1	1	1	0	0

---


--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

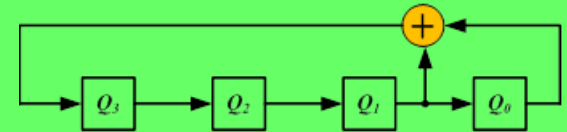


	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	1	0	0	0
1	0	1	0	0
2	0	0	1	0
3	1	0	0	1
4	1	1	0	0
5	0	1	1	0
6	1	0	1	1
7	0	1	0	1
8	1	0	1	0
9	1	1	0	1
10	1	1	1	0
11	1	1	1	1
12	0	1	1	1
13	0	0	1	1
14	0	0	0	1
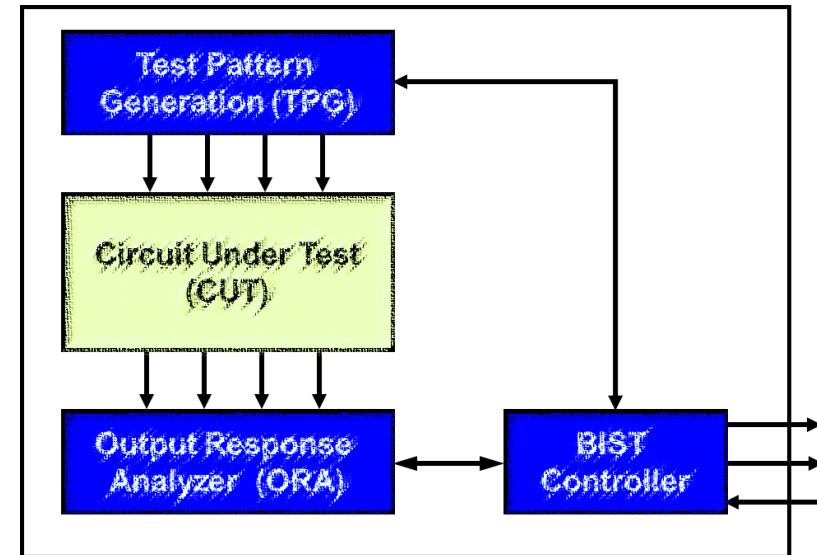
# BIST Part1 - TPG


- Introduction
- Test Pattern Generation (TPG)
  - ◆ Deterministic: ROM, Algorithm, Counter
  - ◆ Pseudo Random
    - \* Linear Feedback Shift Register, LFSR (1977)
      - Two types of LFSR
      - Design of LFSR
        - ⇒ How to find seed?
        - ⇒ What polynomial?
        - ⇒ All-zero pattern?
        - ⇒ What is LFSR degree?
    - \* Cellular Automata, CA (1984)



# State Diagram

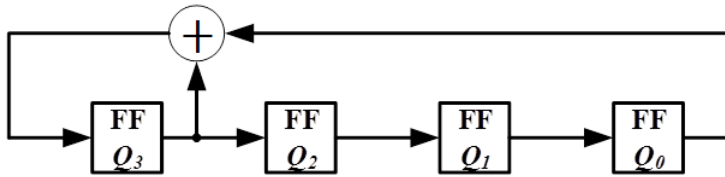


$$f(x) = x^4 + x^3 + 1$$

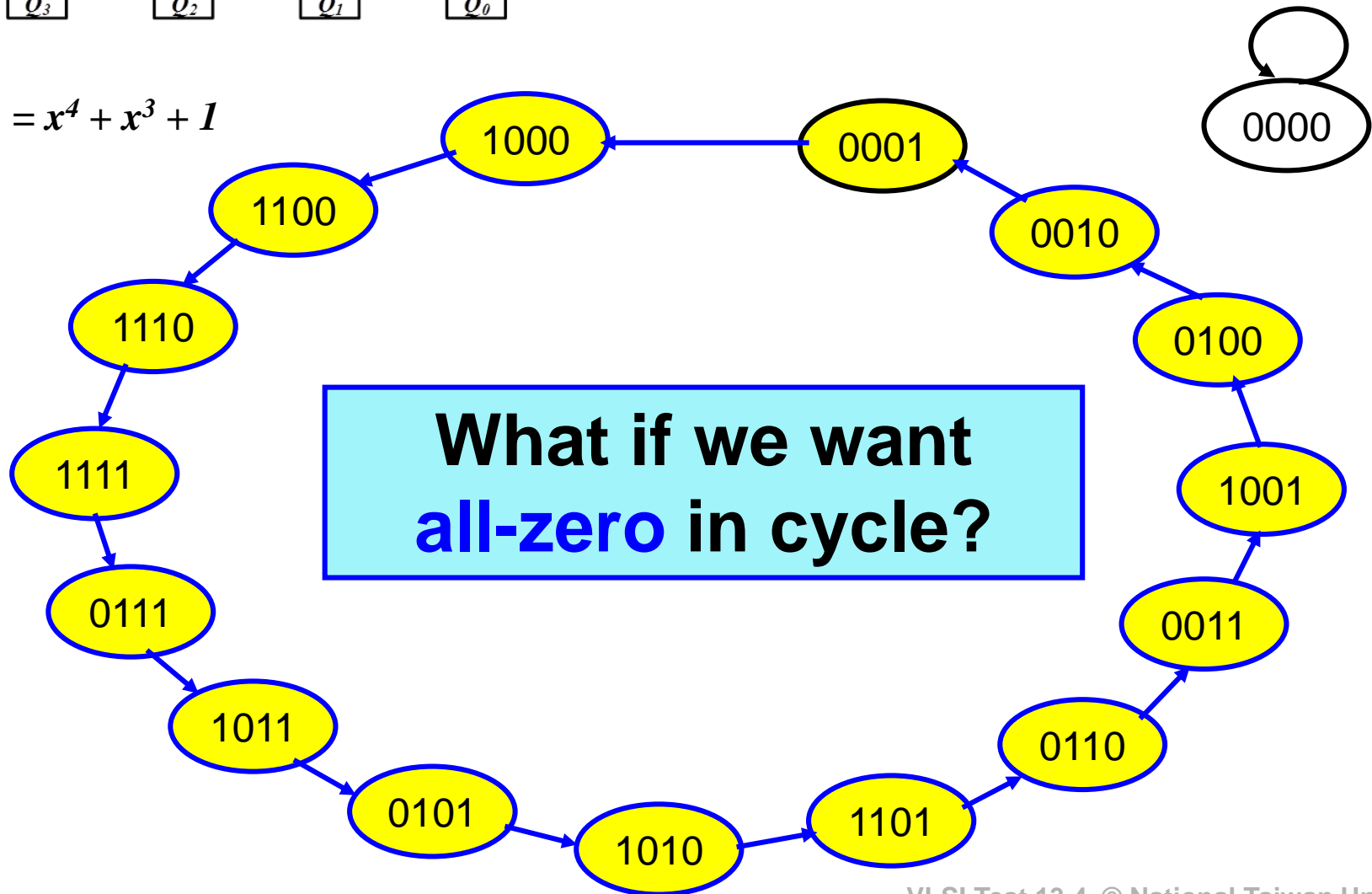
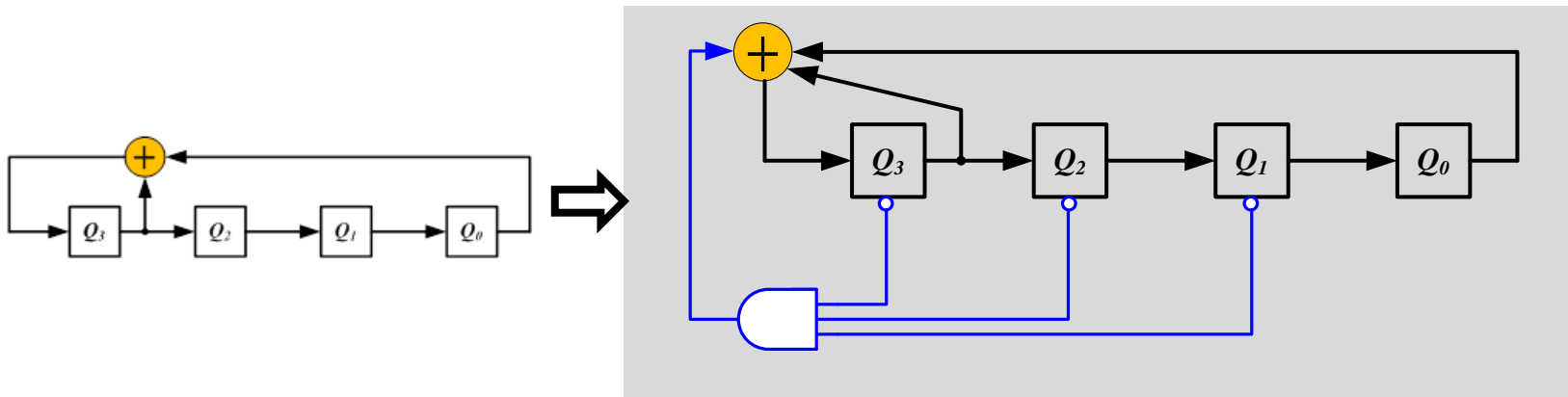
# Exhaustive Feedback Shift Register

- Exhaustive feedback Shift Register (aka. *De Bruijn Counter*)
  - ◆  $2^N$  different states
- Example:  $N=4$ ; 16 exhaustive states
  - ◆ 0001  $\rightarrow$  0000  $\rightarrow$  1000





- **NOTE: This is NOT LFSR because AND is nonlinear**

# DB Counter Generates All-zero Patterns
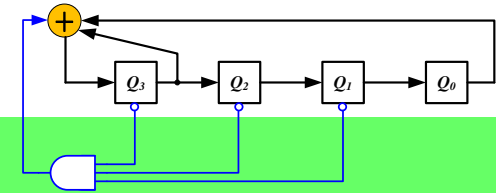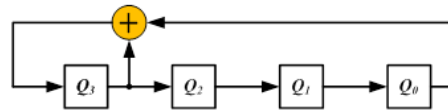
# Quiz

Q: Show this DB counter generates all 16 states.  
Fill in table.




state	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	1	0	0	0
1	1	1	0	0
2	1	1	1	0
3	1	1	1	1
4	0	1	1	1
5	1	0	1	1
6	0	1	0	1
7	1	0	1	0
8	1	1	0	1
9	0	1	1	0
10	0	0	1	1
11	1	0	0	1
12	0	1	0	0
13	0	0	1	0
14	0	0	0	1
15 =0	1	0	0	0

state	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	1	0	0	0
1				
2				
3				
4				
5				
6				
7				
8				
9				
10				
11				
12				
13				
14				
15				
16				
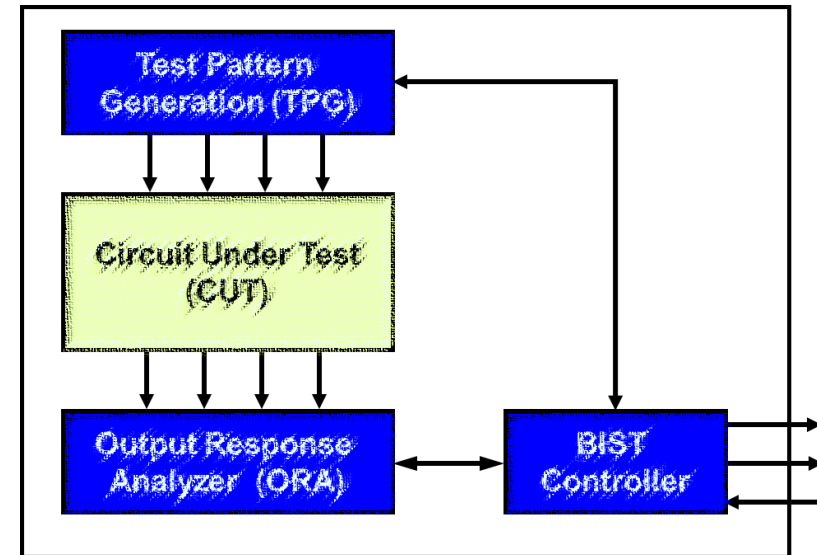
# BIST Part1 - TPG

- Introduction
- Test Pattern Generation (TPG)
  - ◆ Deterministic: ROM, Algorithm, Counter
  - ◆ Pseudo Random
    - \* Linear Feedback Shift Register, LFSR (1977)
      - Two types of LFSR
      - Design of LFSR
        - ⇒ How to find seed?
        - ⇒ What polynomial?
        - ⇒ All-zero pattern?
        - ⇒ What is LFSR degree?
    - \* Cellular Automata, CA (1984)



# What is LFSR Degree? [Konemann 91] \*not in exam

- Suppose **N**-degree LFSR, **S** care bits (*i.e.* specified bits)
  - ♦ **N** variables, **S** equations
  - ♦ What is minimum **N** to guarantee a solution (seed) can be found?
- Probability of not finding a solution


$$P(S, N) = \prod_{i=0}^{S-1} \frac{(2^N - 1) - (2^i - 1)}{(2^N - 1) - 1} \approx 1 - e^{(-2^{(S-N)})}$$

- ♦ When **N** ≥ (**S**+20), probability not finding solution is **10<sup>-6</sup>**
- Example: scan chain length = 1,000. Assume 5% care bits
  - ♦ **S** = 1000x5%=**50**; **N** = 50+20=**70**
  - ♦ Primitive polynomial:  $f(x)=x^{70}+x^{16}+x^{15}+x+1$

**LFSR Degree  $N \geq (S + 20)$**
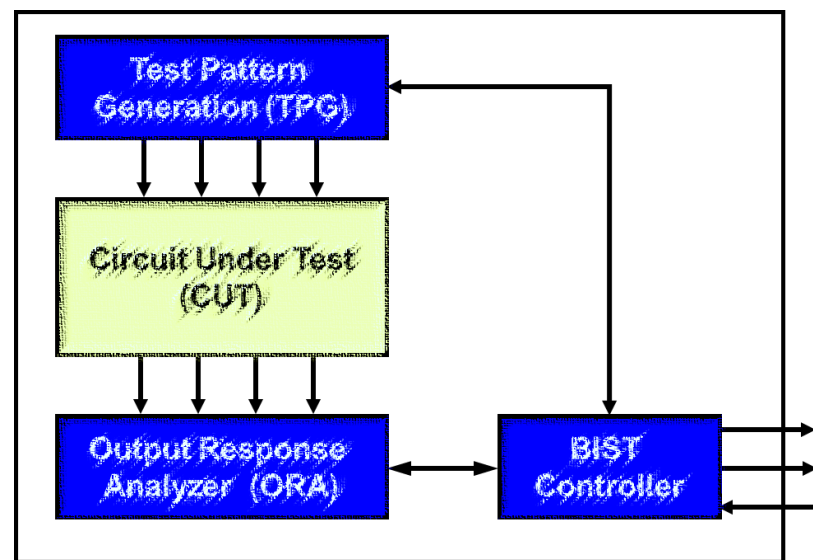
# Summary

- What polynomial to use?
  - ♦ **Primitive polynomials** generates m-sequence
    - \*  $L_c = 2^N - 1$
    - \* Almost half one and half zero
    - \* **Cyclic-shift-and-add** property
- How to generate all-zero pattern?
  - ♦ **Exhaustive feedback shift register**
- How many degree  $N$ ?
  - ♦  $N \geq \text{care-bits} + 20$





# Pros and Cons of LFSR

- Advantages

- 😊 Small area.
- 😊 Easy to design: PP → structure
- 😊 m-sequence has nice properties


- Disadvantages

- 😞 Not enough randomness
- 😞 Large LFSR has many tap points. too slow!

How to solve? see Cellular Automata

state	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
0	1	0	0	0
1	0	1	0	0
2	0	0	1	0
3	0	0	0	1
4	1	1	0	0
5	0	1	1	0
6	0	0	1	1
7	1	1	0	1
8	1	0	1	0
9	0	1	0	1
10	1	1	1	0
11	0	1	1	1
12	1	1	1	1
13	1	0	1	1
14	1	0	0	1

↔ ↔  
1 1

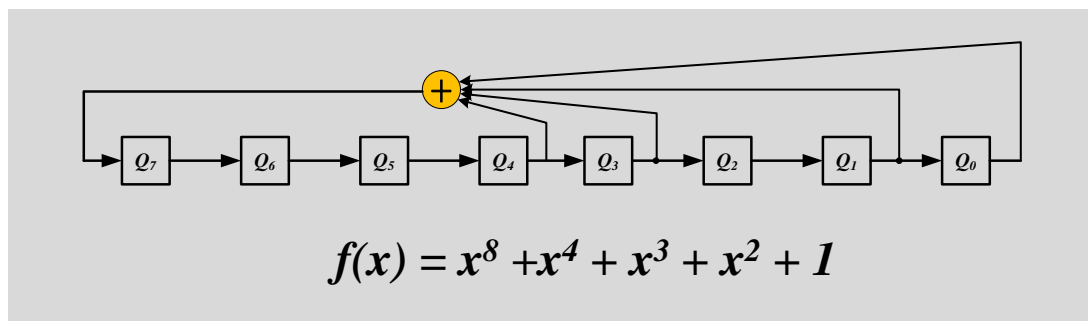

**LFSR Is Most Popular TPG**

# FFT

- Q: *De Bruijn Counter* generates  $2^N$  sequence
  - ♦  $N=4$ ,  $L_c=16$ . 0001111010110010
  - ♦ Does it satisfy cyclic-shift-and-add property?

$$\begin{array}{r} \oplus \quad \begin{array}{|c|c|c|c|c|c|c|c|c|c|c|c|c|c|c|c|} \hline 0 & 0 & 0 & 1 & 1 & 1 & 1 & 0 & 1 & 0 & 1 & 1 & 0 & 0 & 1 & 0 \\ \hline 0 & 0 & 0 & 0 & 1 & 1 & 1 & 1 & 0 & 1 & 0 & 1 & 1 & 0 & 0 & 1 \\ \hline \end{array} \\ \hline \\ ? \end{array}$$

