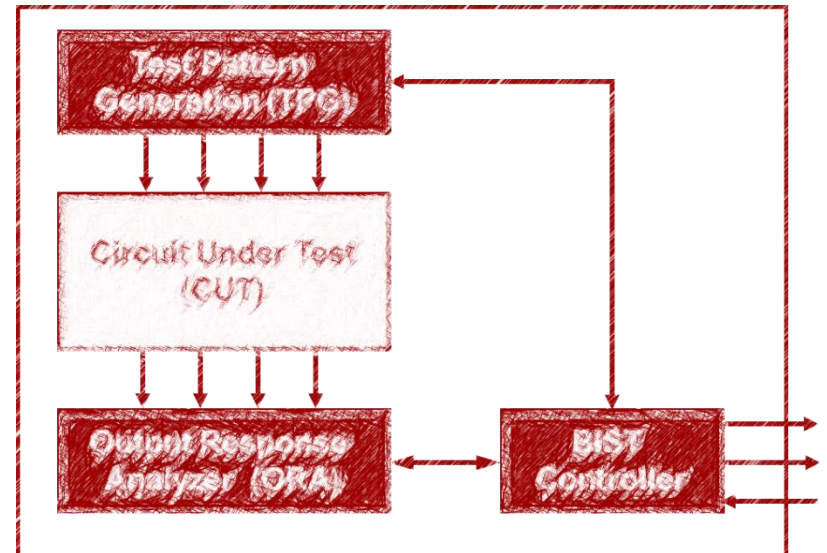


BIST Part1 - TPG

- Introduction
- **Test Pattern Generation**
 - ◆ Deterministic: ROM, Algorithm, Counter
 - ◆ **Pseudo Random**
 - * Linear Feedback Shift Register, LFSR (1977)
 - * **Cellular Automata, CA (1984)**




Cellular Automata [Wolfram 84]

- F_{CA} is a linear function of its two immediate neighbors and itself

$$F_{CA,i} = C_{i-1}S_{i-1} \oplus C_i S_i \oplus C_{i+1}S_{i+1}$$

$C_i=1$ means connection exists

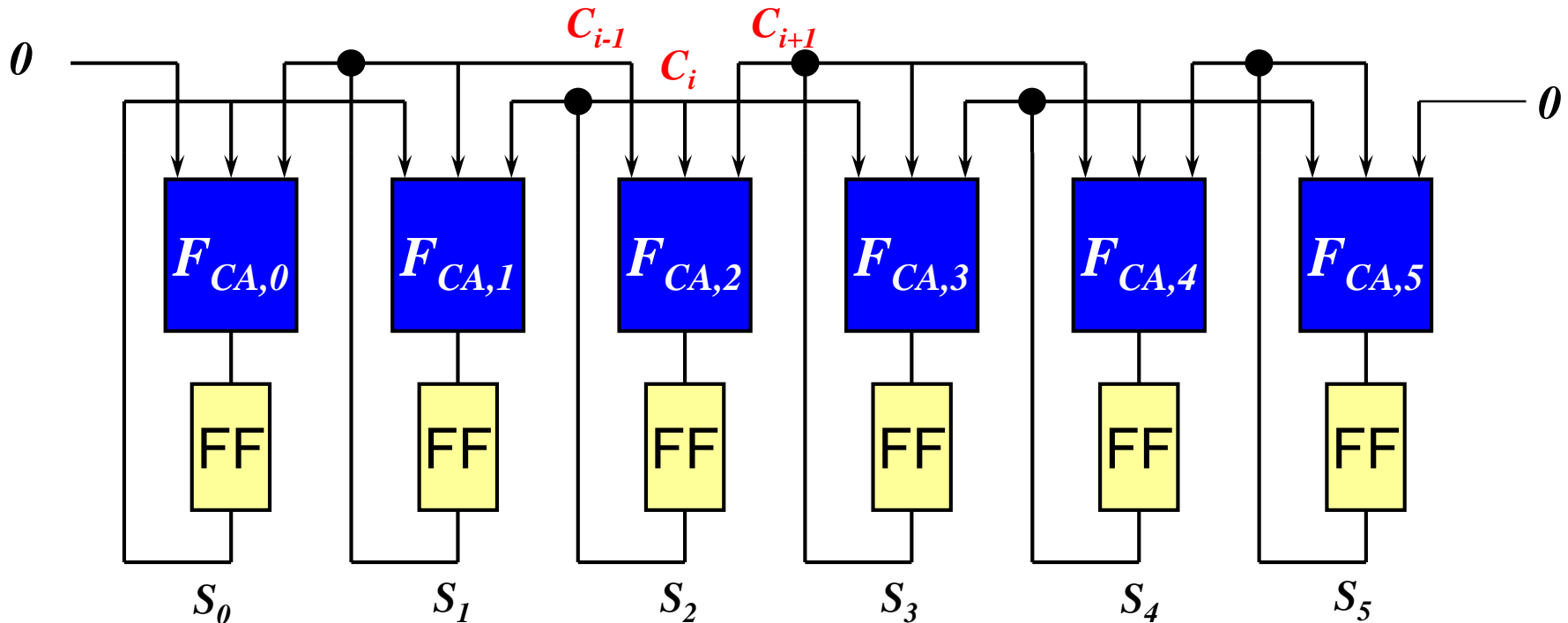- **Null Boundary Condition** = both ends tied to zero
- **Degree** = number of FF = 6



CA Has No Long Global Wires

Name of CA Cell

- CA cell is named by F_{CA} function

K map of F_{CA}

$S_i S_{i-1}$ S_{i+1}		00	01	11	10
		0	1	1	0
0		A_0	A_1	A_3	A_2
1		A_4	A_5	A_7	A_6

$$Name = \sum_{i=0}^7 A_i 2^i$$

- Example: $F_{CA,i} = S_{i-1} \oplus S_i$

$S_i S_{i-1}$ S_{i+1}		00	01	11	10
		0	1	1	0
0		0	1	0	1
1		0	1	0	1

Name = $2^6 + 2^5 + 2^2 + 2^1 = 102$
 This is called a **rule-102 cell**

Quiz

Q1: Given a CA cell $F_{CA,i} = S_{i-1} \oplus S_{i+1}$. What is rule number?


ANS:

K map of F_{CA}

$S_i S_{i-1}$		00	01	11	10
S_{i+1}	0	A_0	A_1	A_3	A_2
	1	A_4	A_5	A_7	A_6


Linear Hybrid CA, LHCA

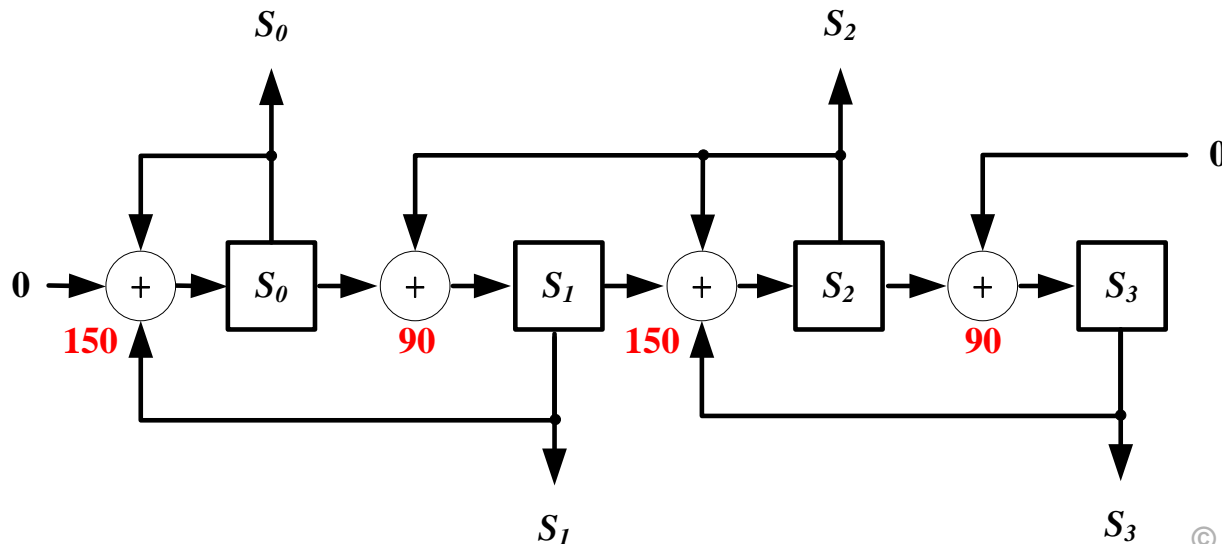- Rule-90 CA cell
 - ♦ $F_{CA,i} = S_{i-1} \oplus S_{i+1}$
- Rule-150 CA cell
 - ♦ $F_{CA,i} = S_{i-1} \oplus S_i \oplus S_{i+1}$
- **90/150 LHCA** with null boundary condition
 - ♦ Consist of only rule-90 and rule-150 cells
 - ♦ Very popular CA, math model well studied
- Example: 4-degree 90/150 LHCA



State Transition

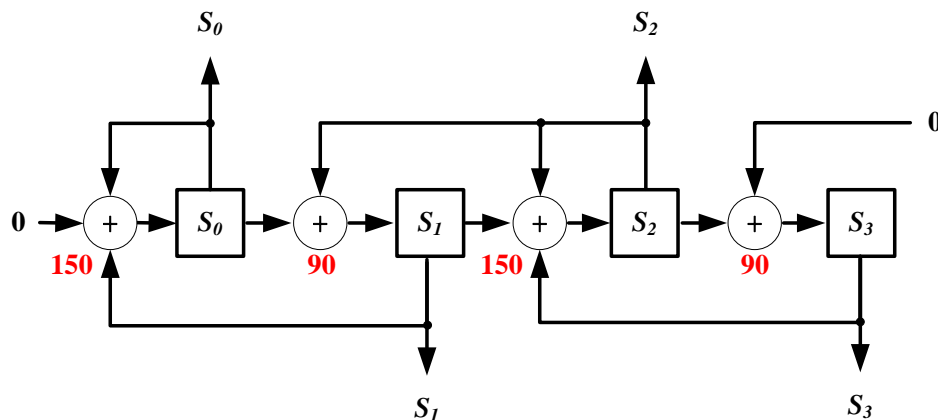- Given **seed = 1000**
- CA generates **pseudo random patterns**
 - ♦ **m-sequence** of phase difference
 - ♦ **Periodic**
- Why this CA generates m-sequence?
 - ♦ to be proved later



state	S_0	S_1	S_2	S_3
0	1	0	0	0
1	1	1	0	0
2	0	1	1	0
3	1	1	0	1
4	0	1	0	0
5	1	0	1	0
6	1	0	1	1
7	1	0	0	1
8	1	1	1	0
9	0	0	0	1
10	0	0	1	0
11	0	1	1	1
12	1	1	1	1
13	0	0	1	1
14	0	1	0	1
15				

Phase diff. $\begin{matrix} \longleftrightarrow & \longleftrightarrow & \longleftrightarrow \\ 11 & 9 & 1 \end{matrix}$


Quiz

Q1: What is state 15?

ANS:

Q2: What is cycle length of this CA?


ANS:

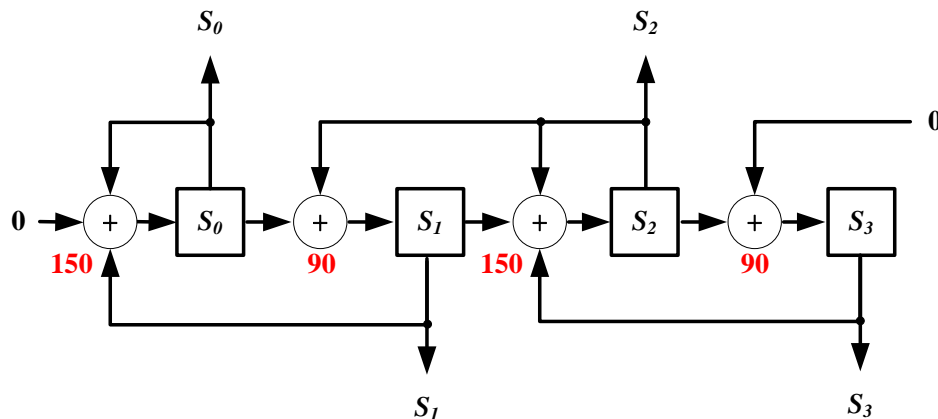

state	S_0	S_1	S_2	S_3
0	1	0	0	0
1	1	1	0	0
2	0	1	1	0
3	1	1	0	1
4	0	1	0	0
5	1	0	1	0
6	1	0	1	1
7	1	0	0	1
8	1	1	1	0
9	0	0	0	1
10	0	0	1	0
11	0	1	1	1
12	1	1	1	1
13	0	0	1	1
14	0	1	0	1
15				

N-degree 90/150 LHCA

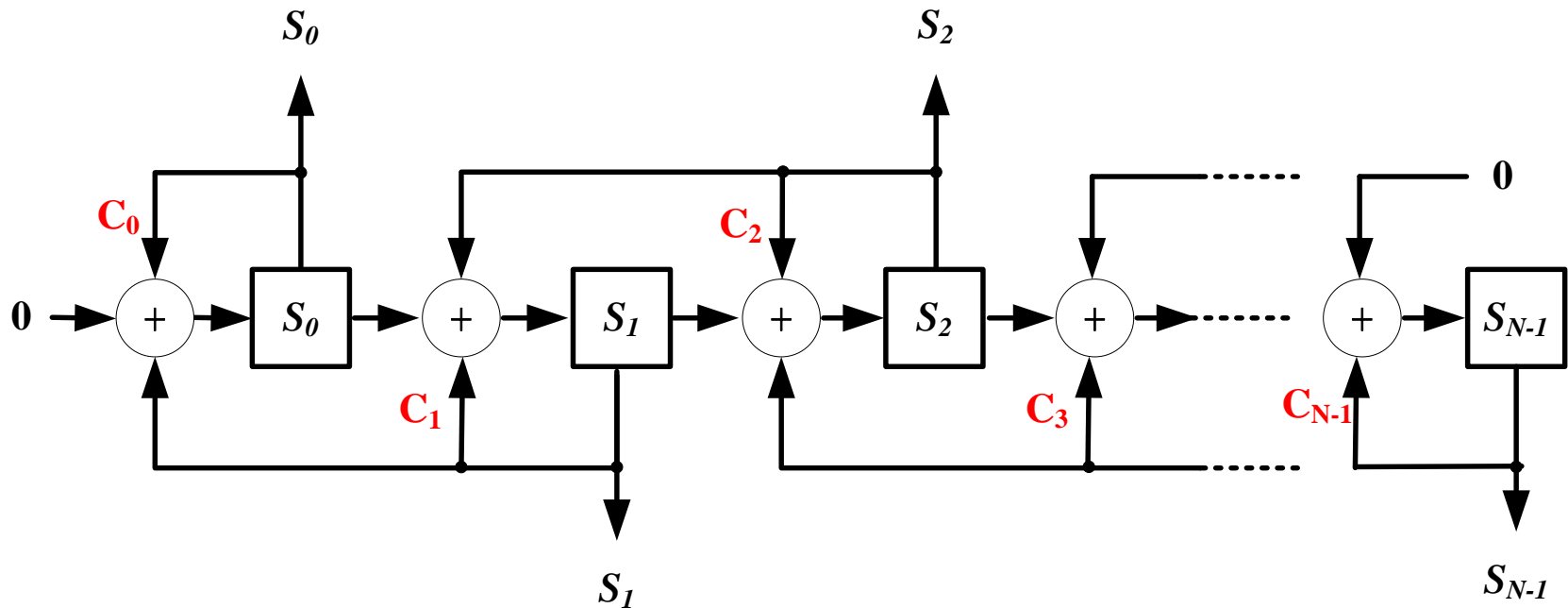- C_i are coefficients
 - ♦ 1 = feedback exists; **rule-150 cell**
 - ♦ 0 = no feedback; **rule-90 cell**



$$F_{CA,i} = S_{i-1} \oplus C_i S_i \oplus S_{i+1}$$

Matrix Representation (90/150 LHCA)

$$\begin{bmatrix} S_0^+ \\ S_1^+ \\ \vdots \\ S_{N-3}^+ \\ S_{N-2}^+ \\ S_{N-1}^+ \end{bmatrix} = \begin{bmatrix} C_0 & 1 & 0 & \dots & 0 & 0 & 0 \\ 1 & C_1 & 1 & \dots & 0 & 0 & 0 \\ \vdots & 1 & C_2 & 1 & \vdots & \vdots & \vdots \\ 0 & 0 & 0 & \dots & C_{n-3} & 1 & 0 \\ 0 & 0 & 0 & \dots & 1 & C_{n-2} & 1 \\ 0 & 0 & 0 & \dots & 0 & 1 & C_{n-1} \end{bmatrix} \begin{bmatrix} S_0 \\ S_1 \\ \vdots \\ S_{N-3} \\ S_{N-2} \\ S_{N-1} \end{bmatrix}$$


$S^+ = C S \quad (\text{mod-2 addition})$

S = current state

S^+ = next state

Characteristic polynomial:

$$f(\lambda) = \det (C - \lambda I)$$

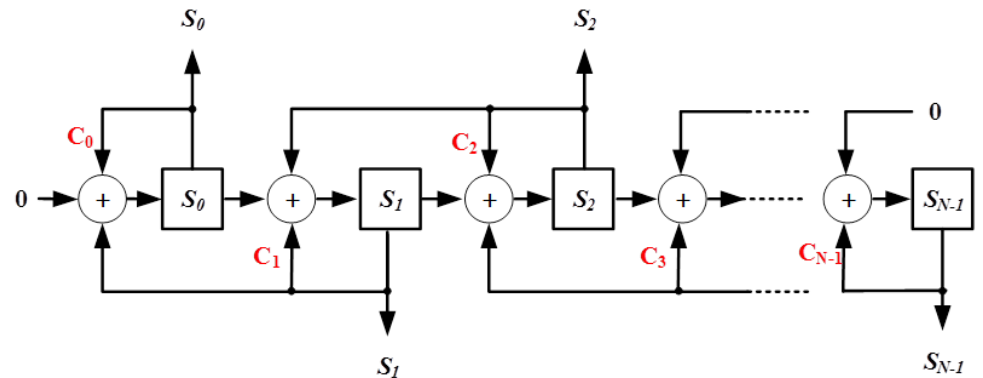

Quiz


Q1: Given this LHCA, what is matrix C ?

ANS:

Q2: What is characteristic polynomial?

NOTE : please use mod-2 addition

ANS:

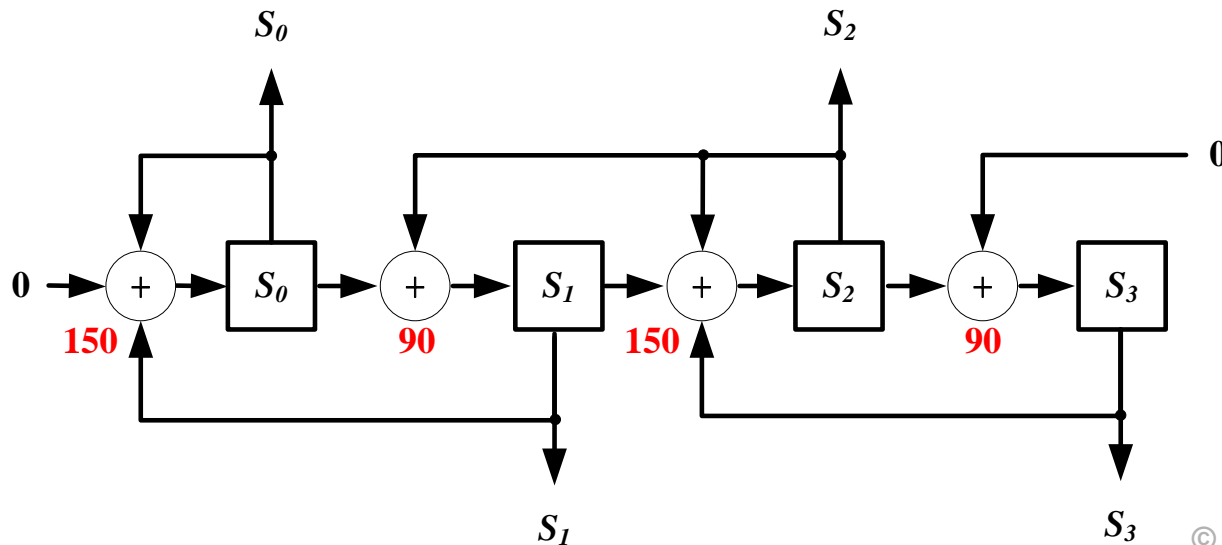

Determinant

$$\det \begin{bmatrix} a & b \\ c & d \end{bmatrix} = ad - bc$$

$$\det \begin{bmatrix} a & b & c \\ d & e & f \\ g & h & i \end{bmatrix} = \begin{vmatrix} a & b & c & a & b \\ d & e & f & d & e \\ g & h & i & g & h \end{vmatrix}$$

$$\text{Determinant} = [aei + bfg + cdh] - [g e c + h f a + i d b]$$

Determinant (column expansion)

- **Column expansion** (with respect to the j^{th} column)

$$\det(A) = |A| = \sum_{i=1}^n a_{ij} C_{ij} = a_{1j} C_{1j} + a_{2j} C_{2j} + \cdots + a_{nj} C_{nj}$$

- **Cofactor of a_{ij}** $= C_{ij} = (-1)^{i+j} \times M_{ij}$
 - ♦ M_{ij} is determinant of A by removing i^{th} row and j^{th} column

- **Example: $j=1$**



$$\begin{aligned} \det(A) &= \begin{vmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{vmatrix} = a_{11} C_{11} + a_{21} C_{21} + a_{31} C_{31} = a_{11} (-1)^{1+1} M_{11} + a_{21} (-1)^{2+1} M_{21} + a_{31} (-1)^{3+1} M_{31} \\ &= a_{11} \begin{vmatrix} a_{22} & a_{23} \\ a_{32} & a_{33} \end{vmatrix} - a_{21} \begin{vmatrix} a_{12} & a_{13} \\ a_{32} & a_{33} \end{vmatrix} + a_{31} \begin{vmatrix} a_{12} & a_{13} \\ a_{22} & a_{23} \end{vmatrix} \end{aligned}$$

Characteristic Polynomial of CA

$$\det(C - \lambda I) = \det \begin{pmatrix} 1-\lambda & 1 & 0 & 0 \\ 1 & -\lambda & 1 & 0 \\ 0 & 1 & 1-\lambda & 1 \\ 0 & 0 & 1 & -\lambda \end{pmatrix}$$

$$C = \begin{pmatrix} 1 & 1 & 0 & 0 \\ 1 & 0 & 1 & 0 \\ 0 & 1 & 1 & 1 \\ 0 & 0 & 1 & 0 \end{pmatrix}$$

$$= (-1)^{1+1}(1-\lambda) \begin{vmatrix} -\lambda & 1 & 0 \\ 1 & 1-\lambda & 1 \\ 0 & 1 & -\lambda \end{vmatrix} + (-1)^{1+2}(1) \begin{vmatrix} 1 & 0 & 0 \\ 1 & 1-\lambda & 1 \\ 0 & 1 & -\lambda \end{vmatrix}$$

$$= (1-\lambda)[\lambda^2(1-\lambda) + \lambda + \lambda] + (-1)[- \lambda(1-\lambda) - 1]$$

$$= \lambda^2(1-\lambda)^2 + 2\lambda(1-\lambda) + \lambda(1-\lambda) + 1$$


$$= \lambda^4 - 2\lambda^3 - 2\lambda^2 + 3\lambda + 1$$

$$= \lambda^4 + \lambda + 1 \quad (\text{mod-2 arithmetic})$$

This CA has a primitive polynomial


LFSR \leftrightarrow CA *not in exam

- If irreducible characteristic polynomial are equal: $f_{CA}(x) = f_{LFSR}(x)$
 - ♦ Then their matrices are **similar**: $T_{CA} \leftrightarrow T_{LFSR}$
 - ♦ i.e. $T_{CA} = V^{-1}T_{LFSR}V$ (aka. *isomorphism transformation*)
 - ♦ [Serra 88][Bardell 90]
- Implications:
- 1. If characteristic polynomial $f_{CA}(x)$ is **primitive polynomial**
 - ♦ It generates **m-sequence** of length $2^N - 1$
- 2. CA and LFSR of same polynomial generate same sequence
 - ♦ Just **phase difference**

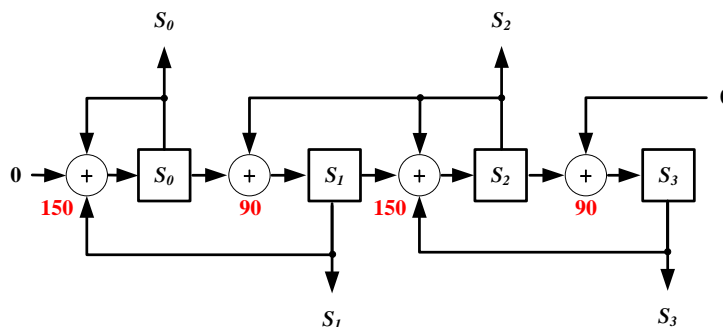

$f_{CA}(x) = x^4 + x + 1$
is primitive polynomial
so it generates m-sequence

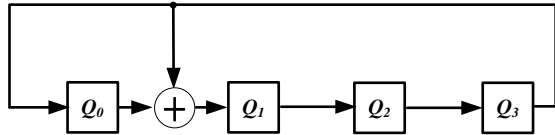
LFSR \leftrightarrow CA, same $f(x)=x^4+x+1$



state	Q_0	Q_1	Q_2	Q_3
0	1	0	0	0
1	0	1	0	0
2	0	0	1	0
3	0	0	0	1
4	1	1	0	0
5	0	1	1	0
6	0	0	1	1
7	1	1	0	1
8	1	0	1	0
9	0	1	0	1
10	1	1	1	0
11	0	1	1	1
12	1	1	1	1
13	1	0	1	1
14	1	0	0	1

same
m-sequence

Phase diff. 12 1 1

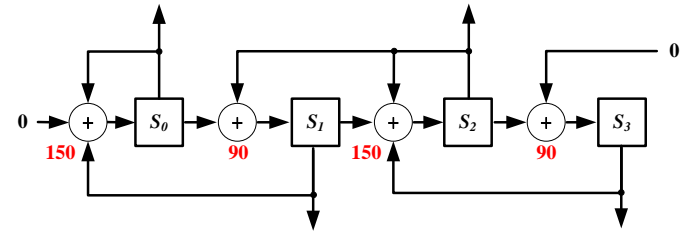

state	S_0	S_1	S_2	S_3
0	1	0	0	0
1	1	1	0	0
2	0	1	1	0
3	1	1	0	1
4	0	1	0	0
5	1	0	1	0
6	1	0	1	1
7	1	0	0	1
8	1	1	1	0
9	0	0	0	1
10	0	0	1	0
11	0	1	1	1
12	1	1	1	1
13	0	0	1	1
14	0	1	0	1

same
m-sequence

Phase diff. 11 9 1


Pros and Cons of CA

- Advantages of CA (over LFSR)
 - + **More randomness** than LFSR
 - ⇒ Large phase shift
 - + Potentially **faster** than LFSR
 - ⇒ short feedback loop
 - + **Small XOR**
 - ⇒ no more than 3-input XOR
- Disadvantages of CA (over LFSR)
 - **No easy design methodology**
 - ⇒ No good method to construct LHCA from polynomial



Summary - CA

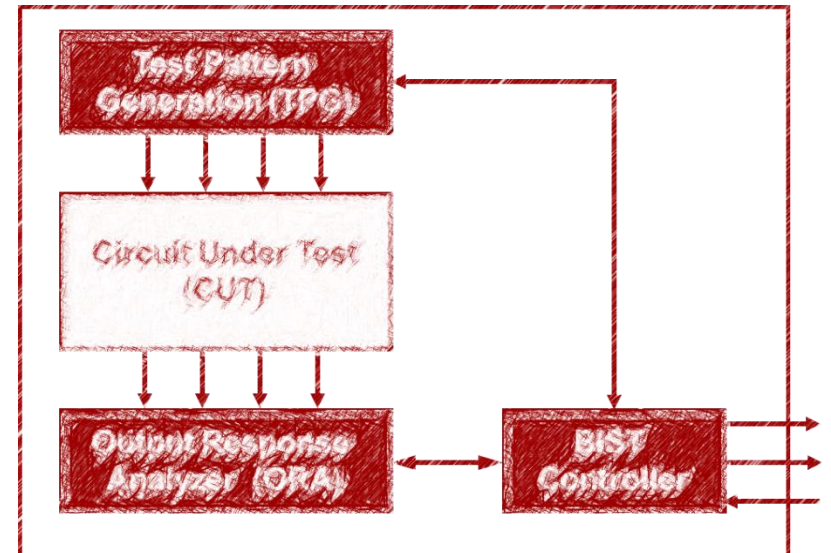- CA are named by its **function**
- **90/150 LHCA** very popular
- Polynomial of CA is $f(\lambda) = \det (C-\lambda I)$
- CA are good **but hard to design**



Reference

- (BMS 87) P.H. Bardell, W.H. McAnney, J. Savior, *Built-in Test for VLSI: Pseudorandom Techniques*, Wiley Interscience, 1987.
- [Könemann 91] B Könemann, “LFSR-coded test patterns for scan designs,” European Test Conference, 1991