 


DFT – Part 2

- Introduction
- Components of JTAG
- JTAG Instructions
 - ◆ Mandatory Instructions
 - ◆ Optional Instructions
- Conclusion




Mandatory Instructions

- EXTEST (000...0)
 - ◆ Selects Boundary-Scan Register, External Test
- BYPASS (111...1)
 - ◆ Selects Bypass Register
- SAMPLE/PRELOAD (instruction code decided by designer)
 - ◆ SAMPLE: Take [snapshot](#) of system I/O pins
 - ◆ PRELOAD: Control system I/O pins



SAMPLE (1/3)

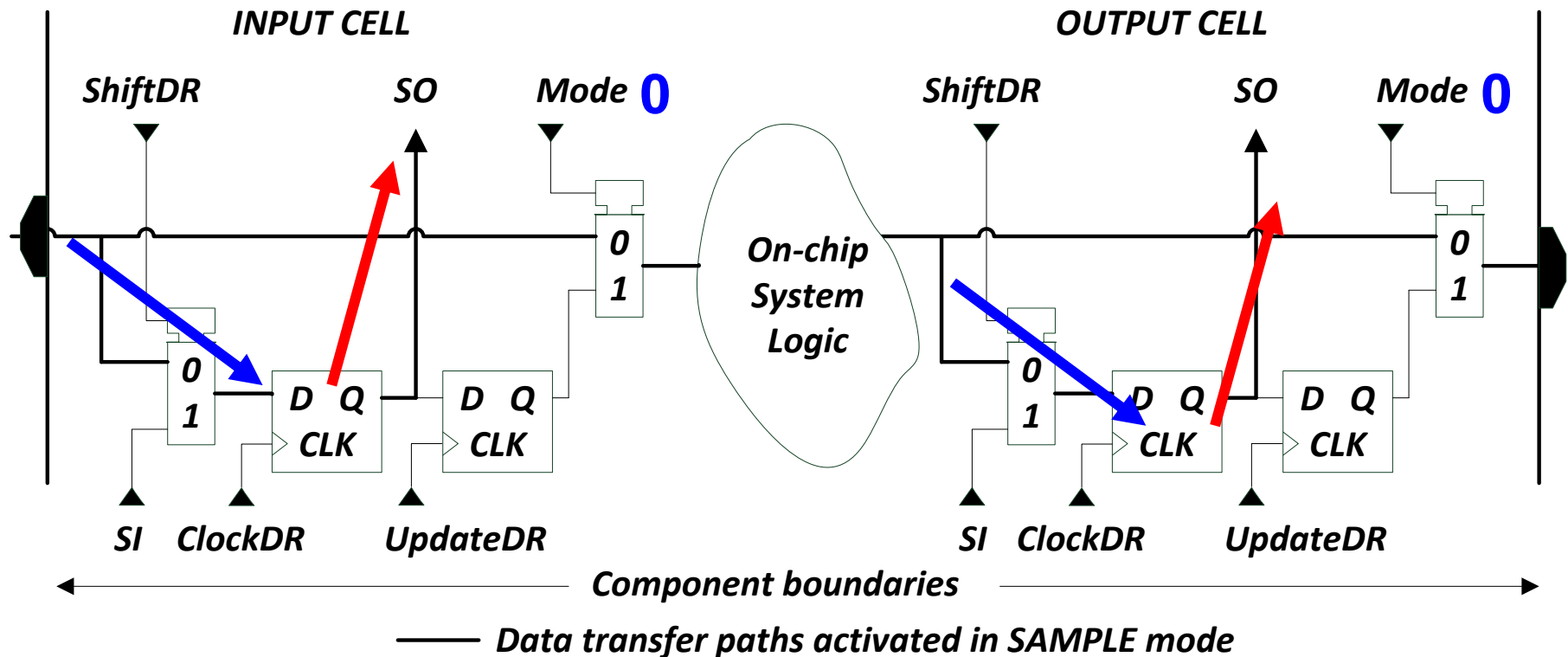- Step1: **Capture**: ShiftDR=0, ClockDR
- Step2: **Scan out**: ShiftDR=1, ClockDR ...
- **Mode = 0** to isolate system logic
 - ◆ Does not interfere with normal operation of system logic



SAMPLE (2/3)


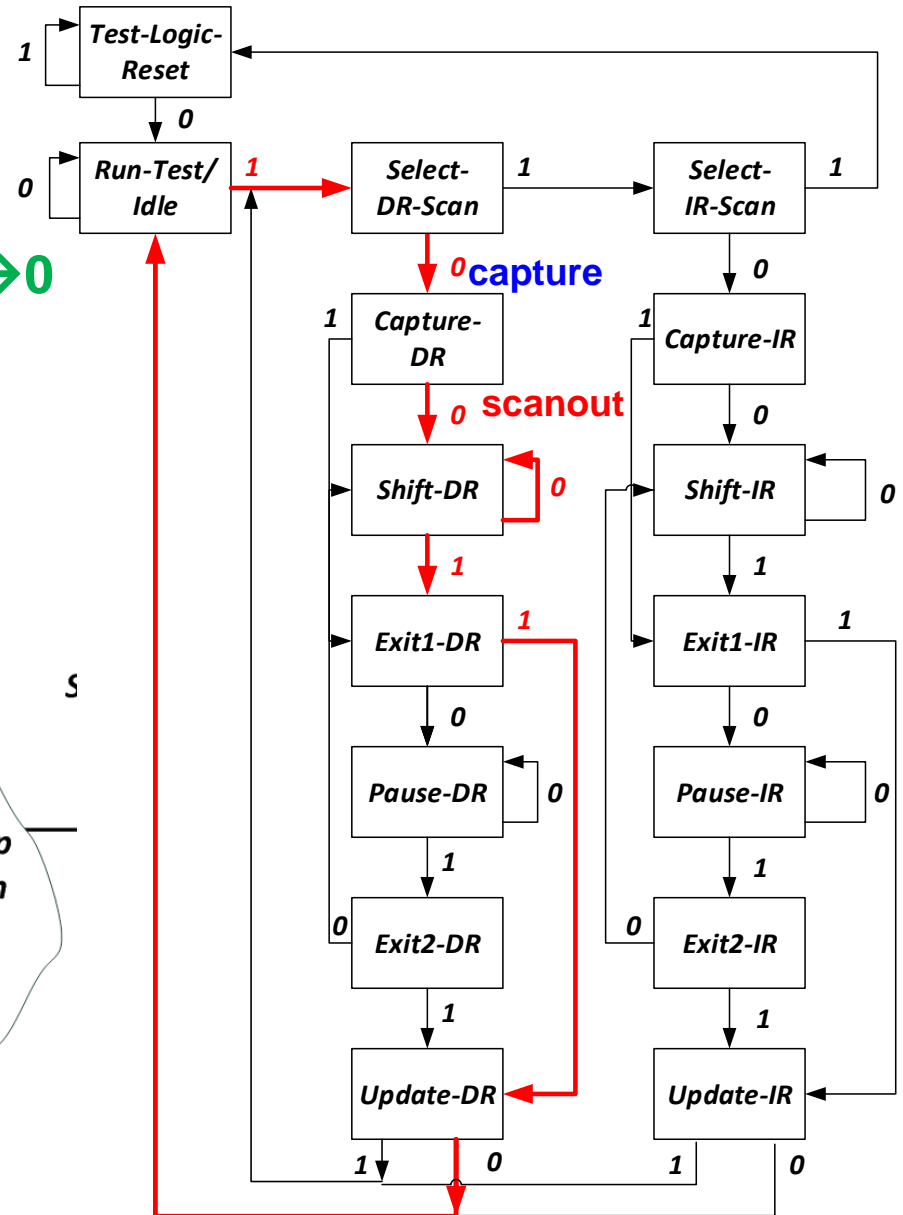
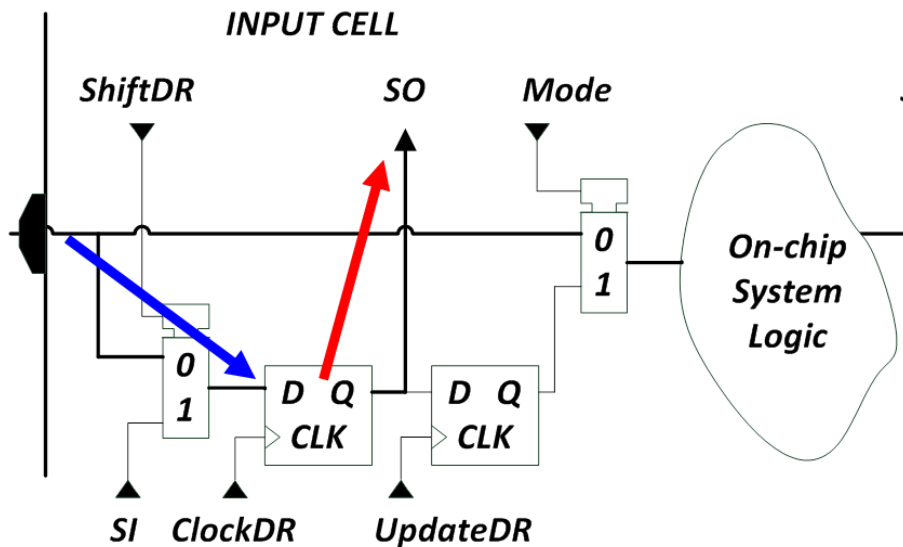
- After instruction loaded
 - ◆ Start from Run-test/Idle
- TMS = 1-→0-→0-→0.....0→1→1→0
 - ◆ Ends at Run-test/Idle



SAMPLE (3/3)

	Capture		Scan out	
TMS	10	0	0000 0000 0000 0000	110
TDI				
TDO			XXXX HLH X XXXX XXXX	
Final state	Capture-DR		Shift-DR	run-test/Idle

(assume instruction code already loaded)

  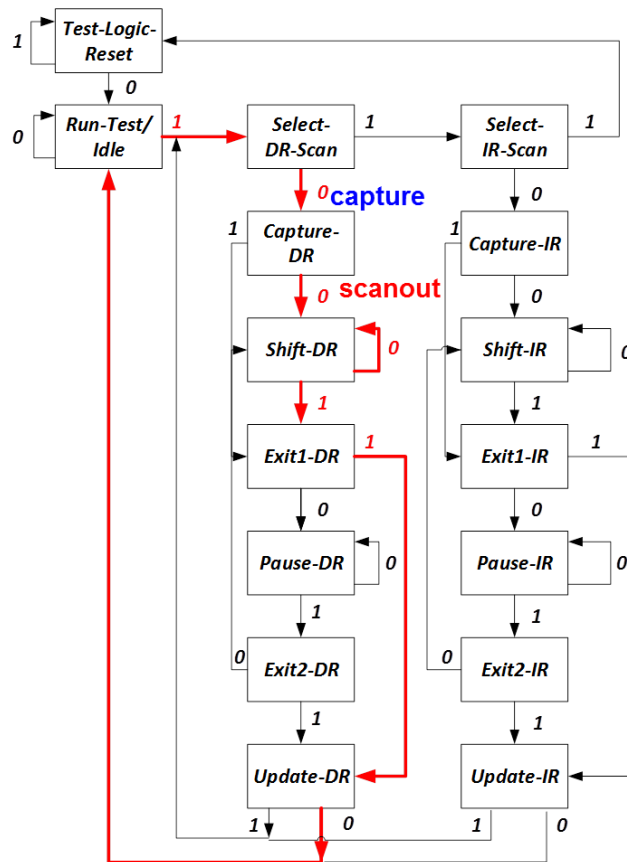


Mandatory Instructions

- EXTEST (000...0)*
 - ◆ Selects Boundary-Scan Register, External Test
- BYPASS (111...1)
 - ◆ Selects Bypass Register
- SAMPLE/PRELOAD (instruction code decided by designer)
 - ◆ SAMPLE: Take snapshot of system I/O pins
 - ◆ PRELOAD: Control system I/O pins (by output FF of BSC)



PRELOAD (1/2)

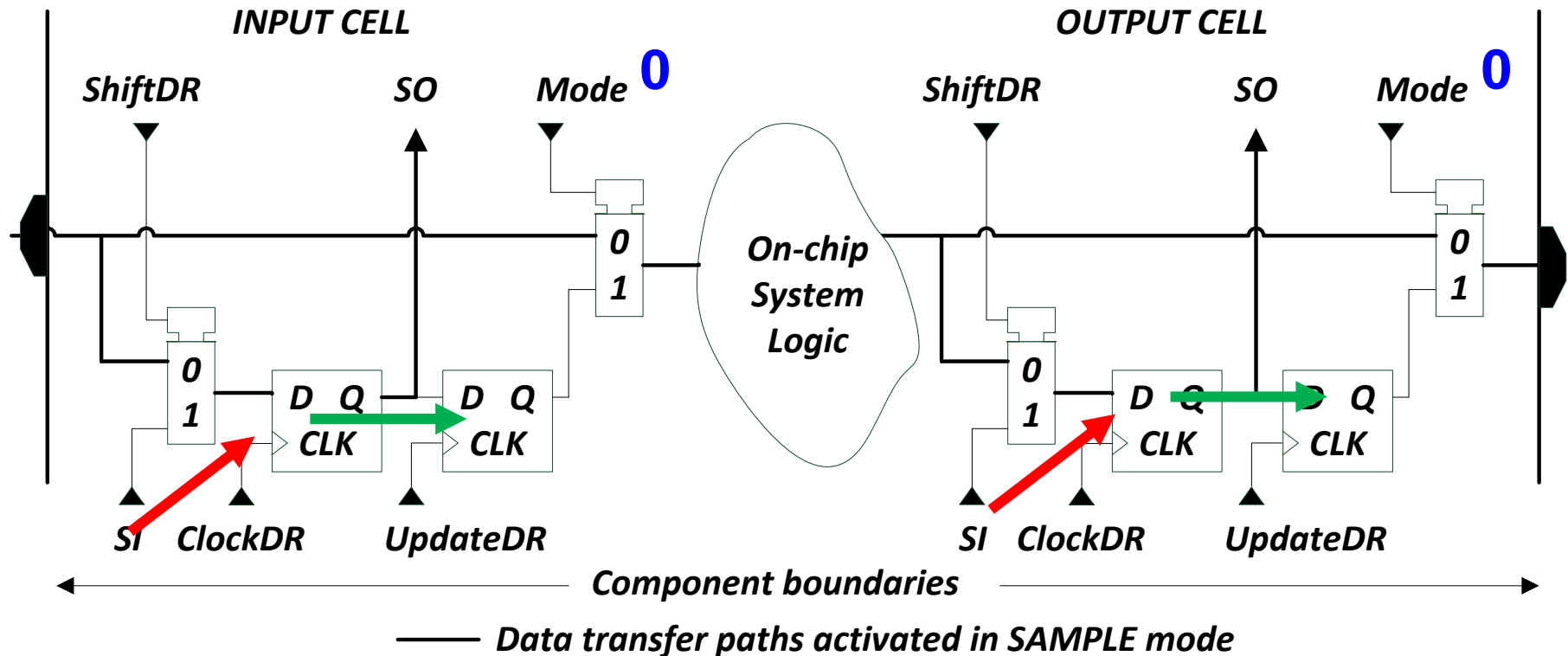- Step1: **Scan in**: ShiftDR=1, ClockDR...
- Step2: **Update**: UpdateDR
- **Mode = 0** to isolate system logic




PRELOAD (2/2)

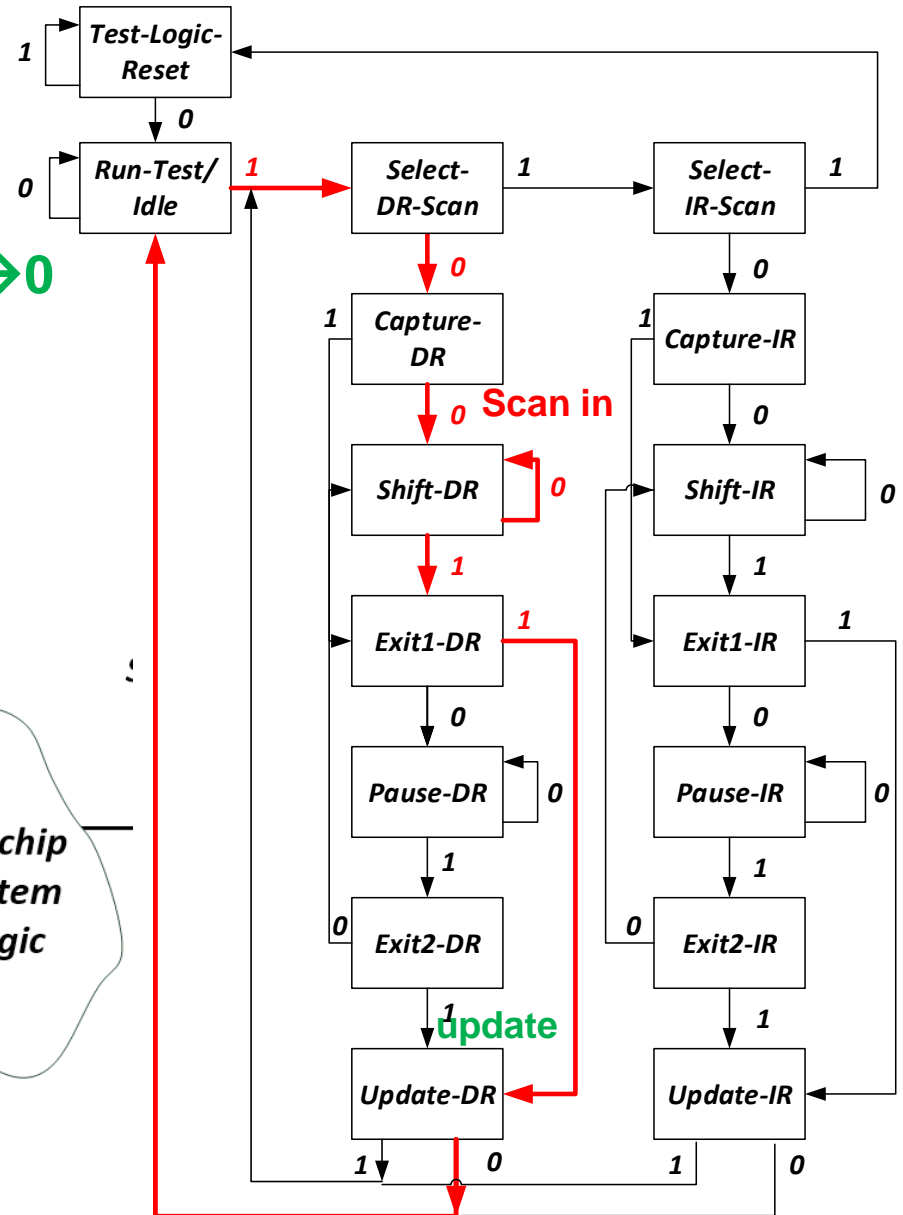 - After instruction loaded
 - ◆ Start from Run-test Idle
- TMS = 1-→0-→0-→0.....0→1→1→0
 - Ends at Run-test/Idle





Quiz

			Scan in	Update
TMS				
TDI				
TDO				
Final state	Capture-DR		Shift-DR	run-test/Idle

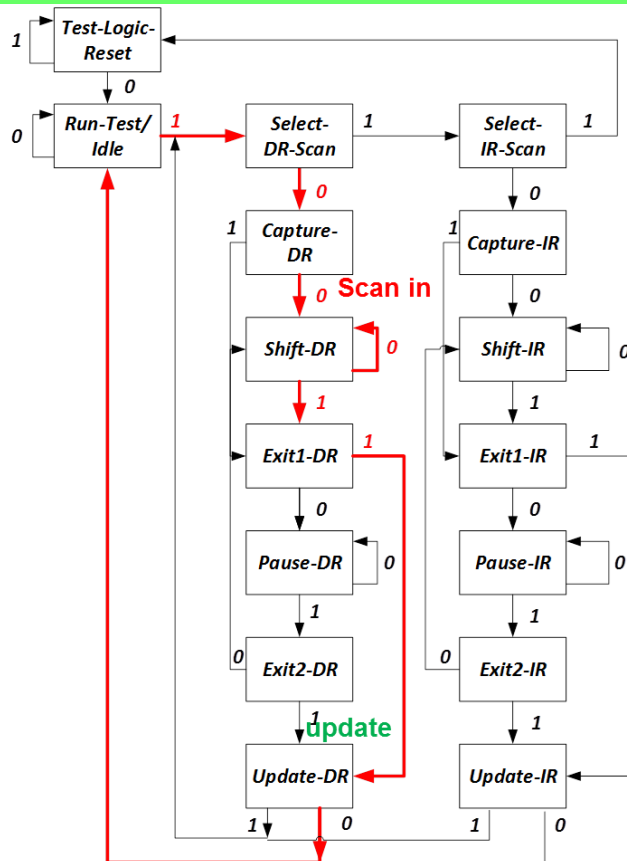


  Q: Suppose we want to preload chip #2 by '1011'. Please fill in blanks. (assume instruction code already loaded)



DFT – Part 2

 - Introduction
- Components of JTAG
- JTAG Instructions
 - ◆ Mandatory Instructions
 - ◆ Optional Instructions
- Conclusion




Optional Instructions

- **INTEST**
 - ◆ Selects Boundary scan register. Internal test of system logic
- **RUNBIST**
 - ◆ Runs built-in self-test (BIST)
- **IDCODE**
 - ◆ Selects device identification register
- **Design Specific**
 - ◆ Designer's Choice


INTEST (1/4)

- Purpose: Test on-chip system logic

 



INTEST (2/4)

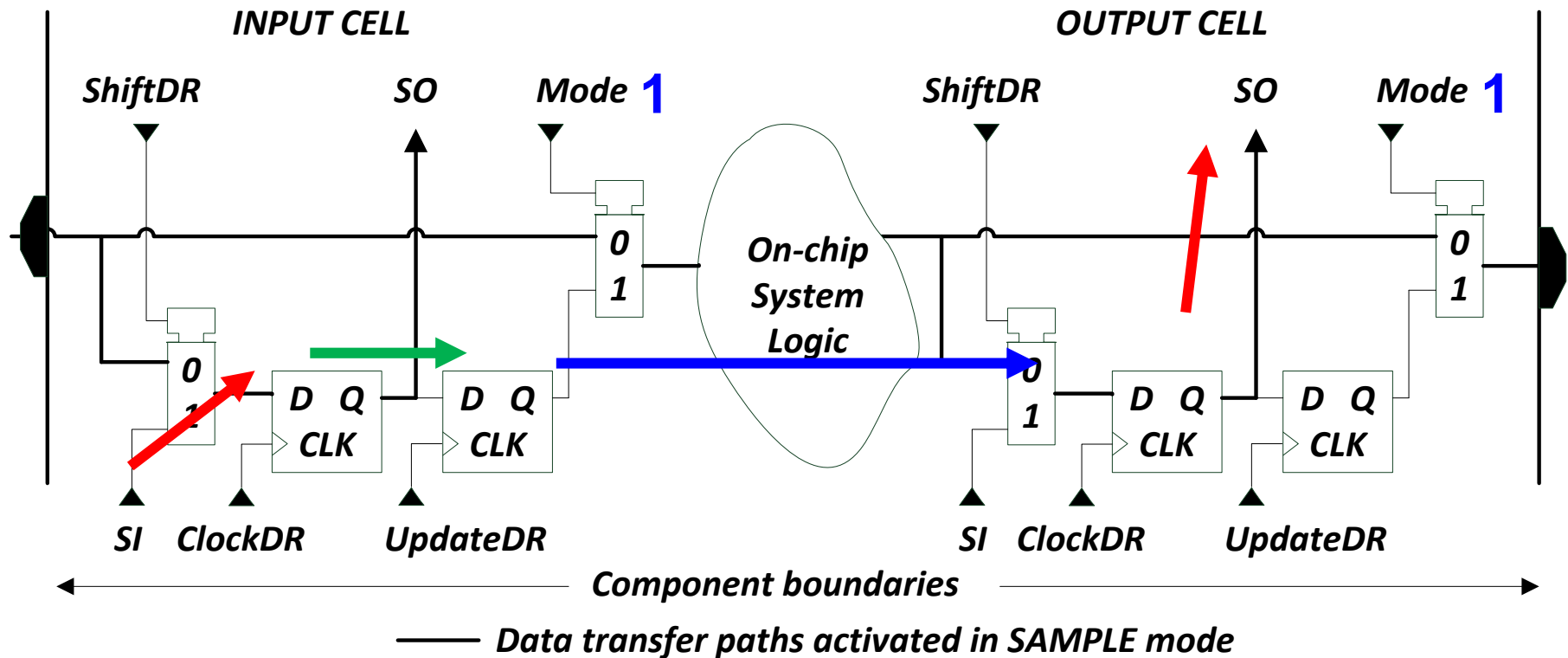- Step 1: **Scan in**: ShiftDR=1 ClockDR ...
- Step 2: **Update Input BSR**: UpdateDR
- Step 3: **Capture Output BSR**: ShiftDR=0 ClockDR
- Step 4: **Scan out**: ShiftDR=1 ClockDR ...
- **Mode = 1**





INTEST (3/4)

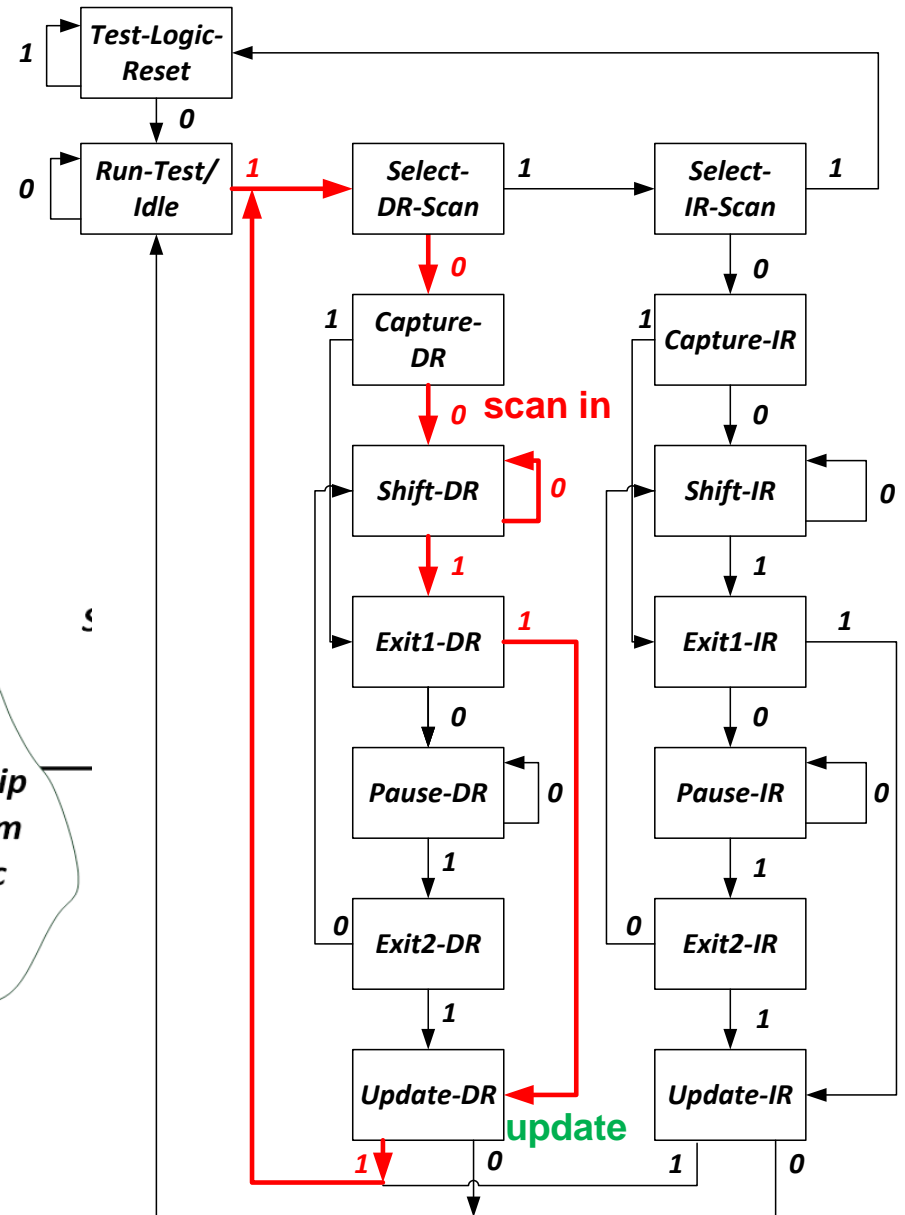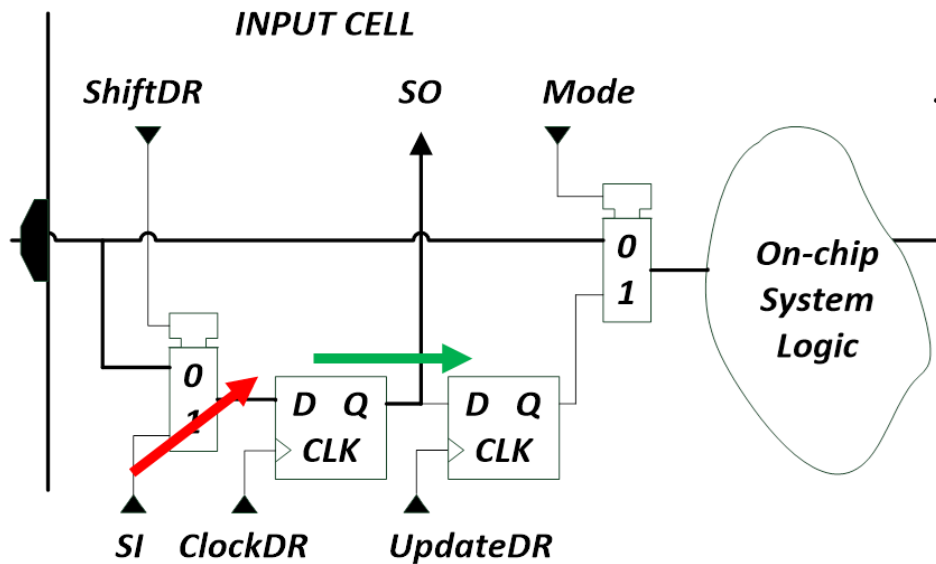- After instruction loaded
 - ◆ Start from Run-test/Idle
- TMS = 1→0→0→0...0→1→1→1



INTEST (4/4)

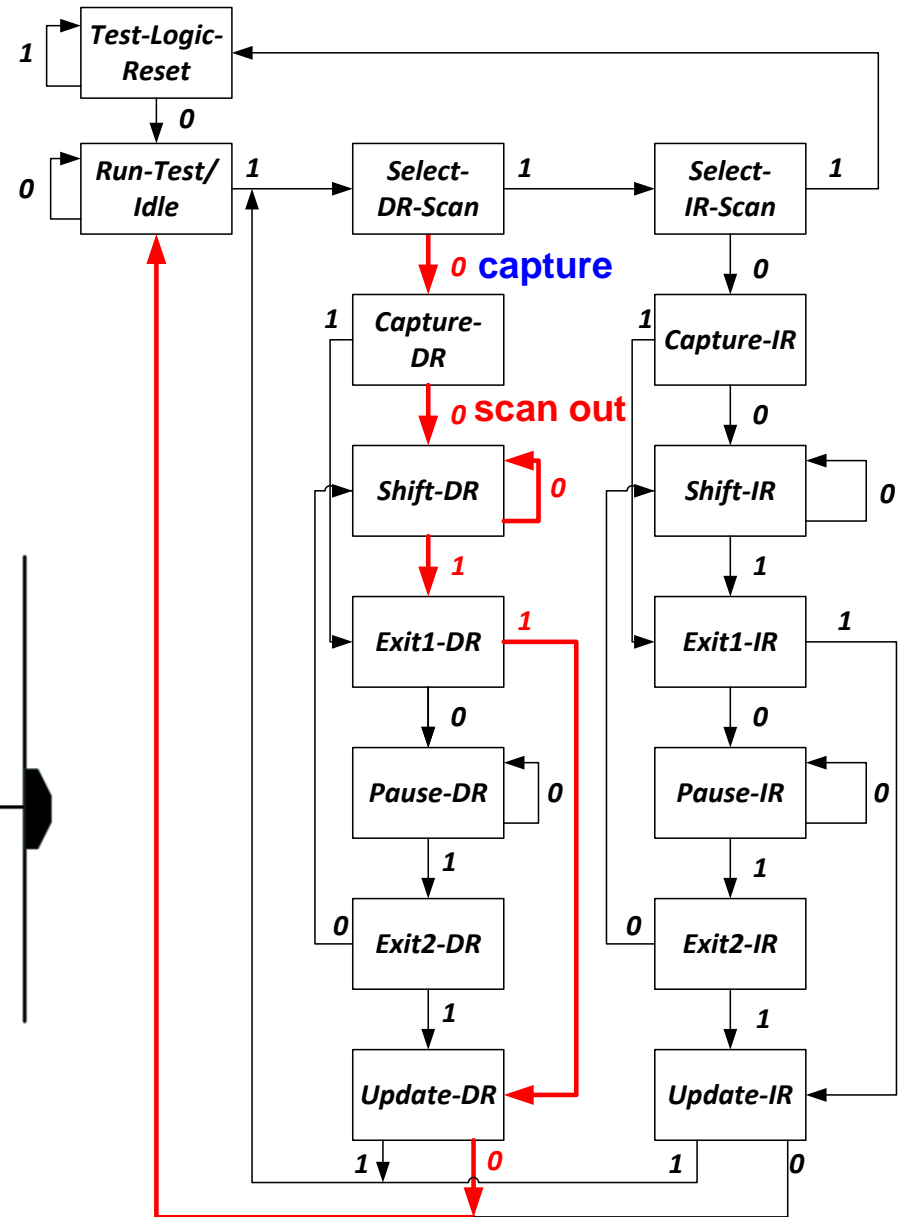
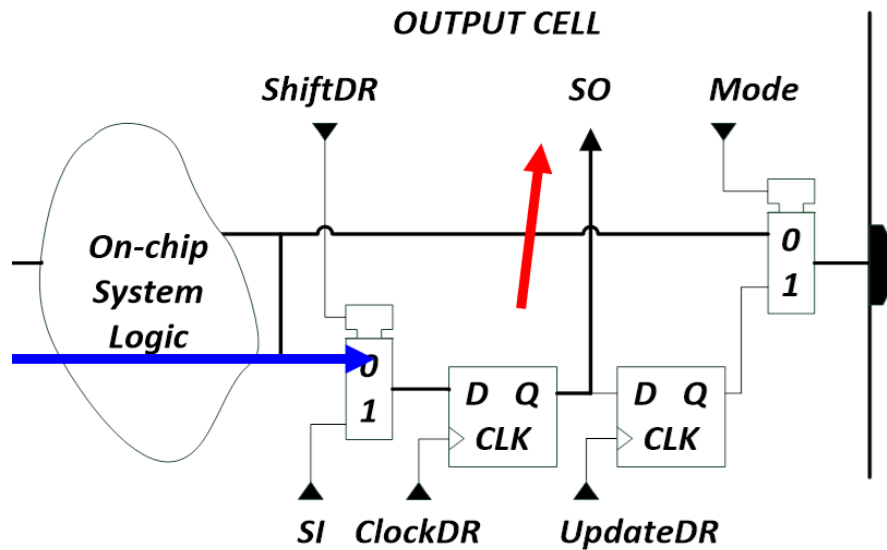
- TMS = 0 → 0 → 0...0 → 1 → 1 → 0
- Ends at Run-test/Idle



Quiz


			Scan in	Update Capture	Scan-out
TMS					
TDI					
TDO					
Final state	Capture-DR		Shift-DR		Run-test Idle

  Q: Suppose we want to test AND gate by '10'. Please fill in blanks. (assume instruction code already loaded)




RUNBIST Instruction* not in exam

 - Purpose: Run BIST commands
- To avoid random system logic outputs during BIST
 - ◆ (1) BSR controls system output pins. (PRELOAD), or
 - ◆ (2) Put all output BSR to high-impedance (Z)
- BIST results (PASS or FAIL) can be left in BSR or internal cell
 - ◆ Shift out through boundary scan chain



IDCODE Instruction* not in exam

 - Purpose: Connects **chip ID register** serially between TDI and TDO
 - ♦ Read out chip ID
- Device ID standard by JEDEC (Joint Electron Device Engineering Council)




Conclusion

- JTAG IEEE 1149.1 standard
 - ◆ Boundary scan for board-level testing
- Components
 - ◆ TAP ports, TAP controller
 - ◆ Registers (BSR/BR/IR), Instruction decoder
- Instructions
 - ◆ Mandatory: EXTEST, BYPASS, SAMPLE/PRELOAD
 - ◆ Optional: INTEST, RUNBIST, IDCODE ...
- JTAG area overhead is small
 - ◆ Has been widely adopted by industry
 - ◆ Automatic compiler is widely available

FFT

 
- Q1: INTEST is exactly the same as EXTEST, why?
- Q2: During PROLOAD, Why do we need to control system output?



Reference


- **JTAG Verilog Code Example**
 - ◆ **M. D. Ciletti, “Advance Digital Design with the Verilog HDL,” Prentice Hall, 2002, Ch11.**
- **K.P. Parker, *The Boundary Scan Handbook*, Springer.**

Appendix: TAP controller timing

 


INTEST Instruction Clocks

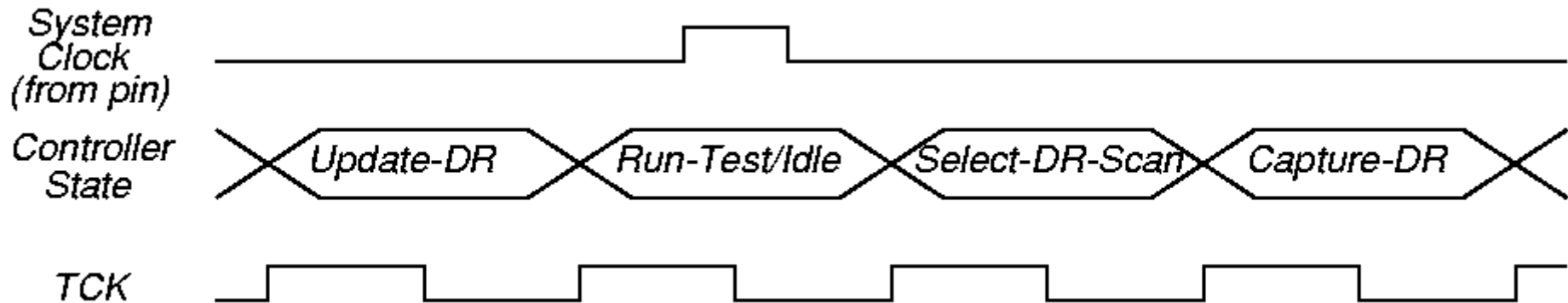Control of applied system clock during **INTEST**



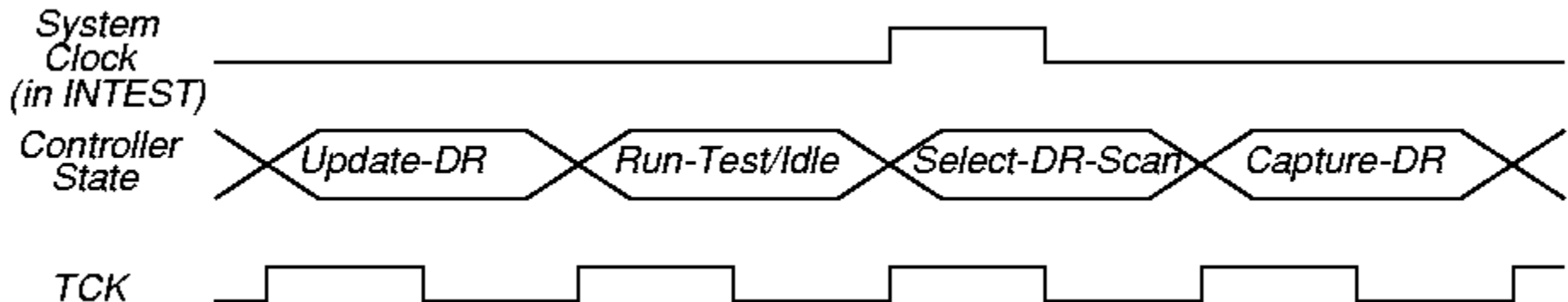Use of **TCK** for on-chip system logic clock



CLAMP Instruction

- Purpose: Forces chip outputs to be driven by BSR
- Can bypass boundary scan chain by using one-bit Bypass Register
- May have to add RESET hardware to control on-chip system logic
 - ♦ so that it does not get damaged (by shorting 0's and 1's onto an internal bus, etc.)

